

Design Kit

Class D Audio Amplifier Using IRS2092

Contents

	Slide #
1. Specification.....	3
• Efficiency.....	4-5
• THD.....	6-7
• Frequency Response.....	8-9
• Note: $P_o[W]$ vs. $V_{in}[V_{PEAK}]$	10
2. Waveforms Evaluations.....	11
3. Simulated vs. Measured Waveforms.....	12-14
4. Voltage Gain – G_V	15-16
5. Self Oscillation Frequency.....	17-18
6. Dead time.....	19-21
7. Turn on transient.....	22-25
8. Components stress.....	26-27
9. Power loss in the MOSFETs.....	28
• Standard Model.....	29-30
• Professional Model.....	31-33
• Standard vs. Professional Model.....	34-35
10. Short circuit vs. switching output shutdown.....	36-38
11. Short Circuit Response.....	39-41
12. Capacitor Models.....	42-44
13. Simulated Performance of the circuit with different FETs.....	45-47
14. Simulation Index	48



1. Specifications

General Test Conditions

Supply Voltage	$\pm 15V$
Load Impedance	8-4 Ω
Self-Oscillating Frequency	400kHz
Gain Setting	24dB

[Simulation folder](#)

Electrical Data

Output Power	25W	(1kHz, 4 Ω)
Efficiency	93%	(25W, 4 Ω)

[\[Efficiency\]](#)


Audio Performance

Distortion	Less than 0.015%THD	(1kHz, 4 Ω , 10W)
Frequency Response : 20Hz~20kHz	$\pm 1dB$	(20 ~ 20000 Hz, 4 Ω , 2V Output)

[\[THD\]](#)

[\[FrqRsp\]](#)

 Specifications : Efficiency Evaluation Circuit



Condition :
 $P_o = 25[W], 4\Omega$ Load

Analysis

Time Domain (Transient)

Run to time: 3ms

Start saving data after: 1ms

Maximum step size: 100n

Skip the initial transient bias point calculation (SKIPBP)

.Options

RELTOL: 0.01

VNTOL: 1.0u

ABSTOL: 1.0n

CHGTOL: 0.01p

GMIN: 1.0E-12


ITL1: 500

ITL2: 200


ITL4: 10



 Specifications : Efficiency Simulation Result



Specifications : THD Evaluation Circuit

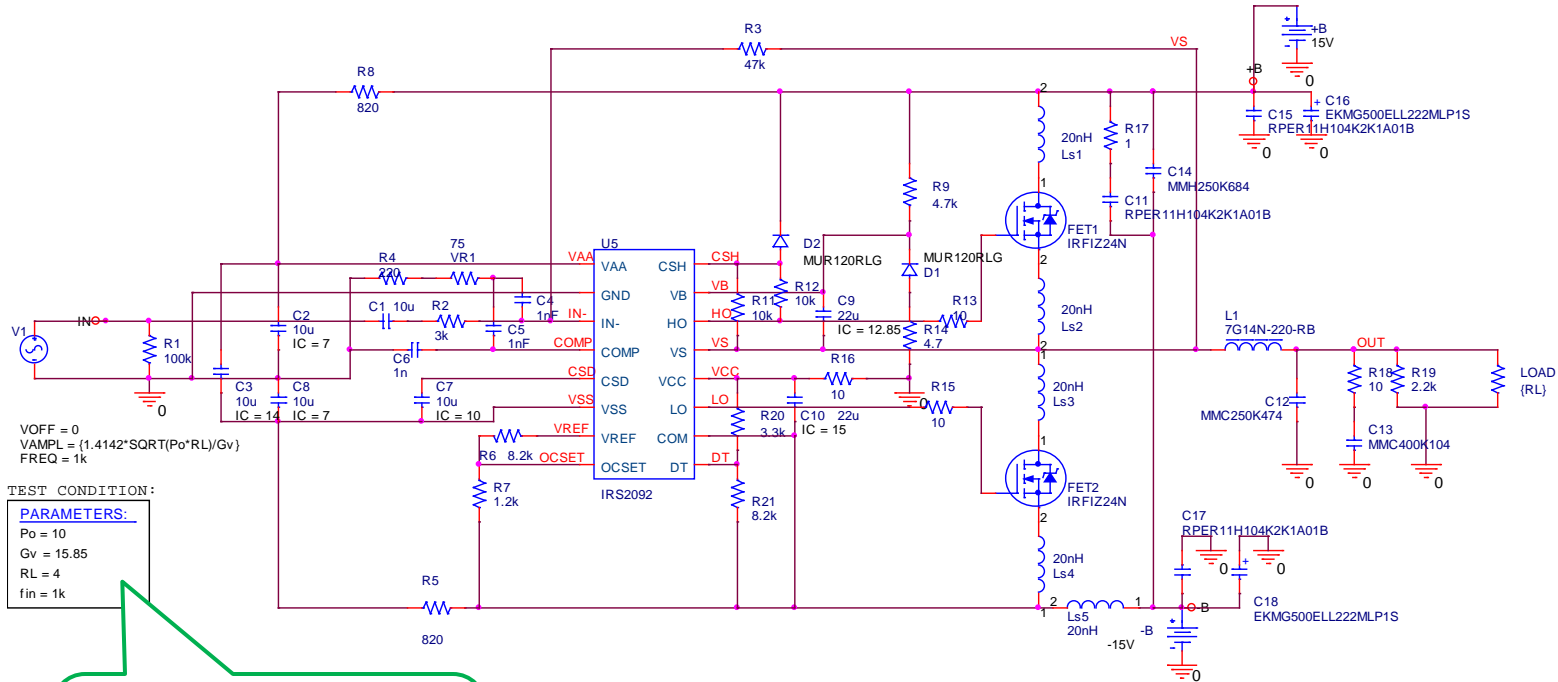

VOFF = 0
 VAMPL = (1.4142*SQRT(Po*RL)/Gv)
 FREQ = 1k

TEST CONDITION:

PARAMETERS:

Po = 10
 Gv = 15.85
 RL = 4
 fin = 1k

Condition :
 $f_{in} = 1\text{kHz}$, $P_o = 10\text{[W]}$,
 4Ω Load

Analysis

Time Domain (Transient)

Run to time: 3ms

Start saving data after: 0s

Maximum step size: 100n

Skip the initial transient bias point calculation (SKIPBP)

Output File Options...

Perform Fourier Analysis

Center Frequency: 1kHz

Output Variables: V(OUT)

.Options

RELTOL: 0.01

VNTOL: 1.0u

ABSTOL: 1.0n

CHGTOL: 0.01p

GMIN: 1.0E-12


ITL1: 500

ITL2: 200

ITL4: 10




Specifications : THD Simulation Result

 

HARMONIC NO	FREQUENCY (HZ)	FOURIER COMPONENT	NORMALIZED COMPONENT	PHASE (DEG)	NORMALIZED PHASE
1	1.00E+03	8.81E+00	1.00E+00	1.79E+02	0.00E+00
2	2.00E+03	4.62E-04	5.25E-05	4.18E+01	-3.15E+02
3	3.00E+03	2.78E-04	3.16E-05	8.49E+01	-4.51E+02
4	4.00E+03	3.23E-04	3.67E-05	6.91E+01	-6.45E+02
5	5.00E+03	3.73E-04	4.23E-05	8.66E+01	-8.06E+02
6	6.00E+03	6.69E-04	7.60E-05	6.10E+01	-1.01E+03
7	7.00E+03	2.85E-04	3.24E-05	8.09E+01	-1.17E+03
8	8.00E+03	4.32E-04	4.91E-05	7.17E+01	-1.36E+03
9	9.00E+03	5.95E-04	6.76E-05	2.70E+01	-1.58E+03

TOTAL HARMONIC DISTORTION = 1.438206E-02 PERCENT

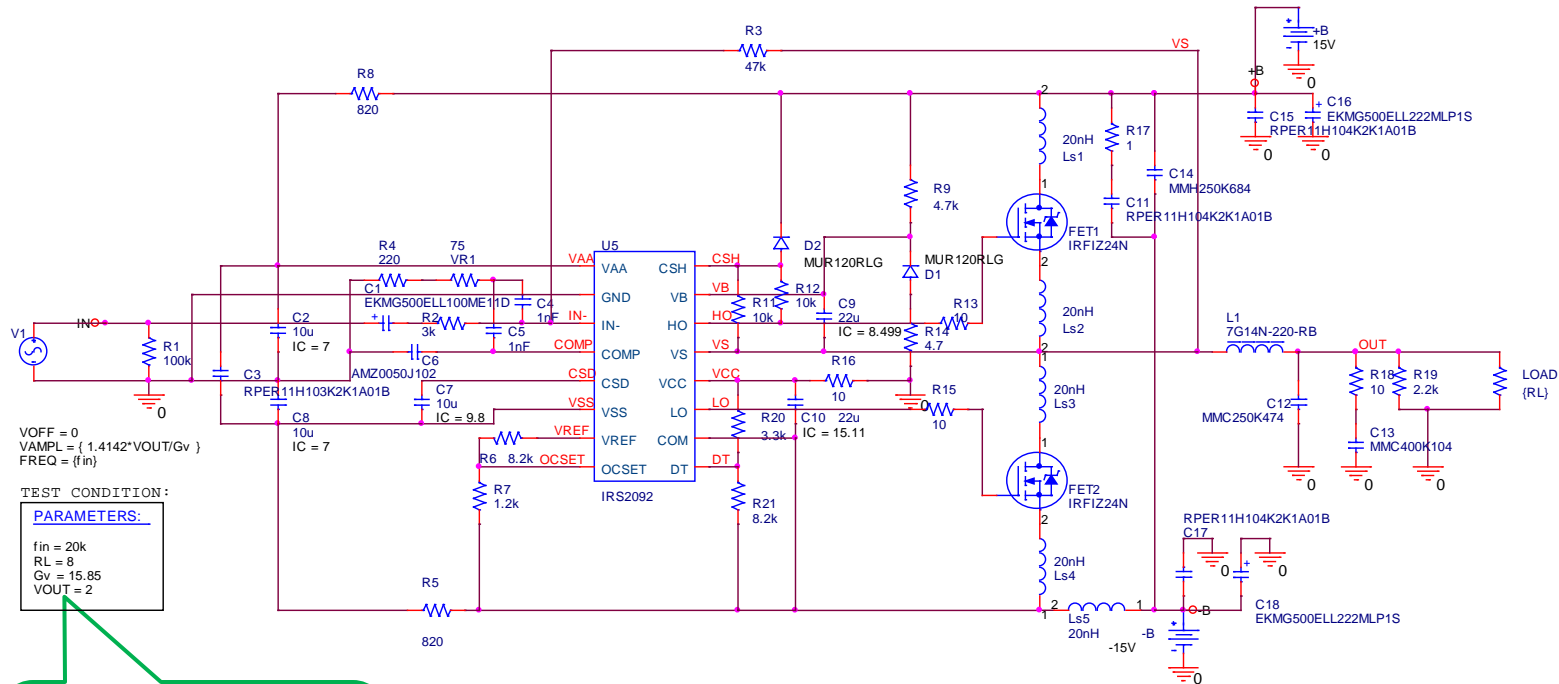Specifications : Frequency Response Evaluation Circuit



Condition :
20 ~ 20000 Hz, 4Ω
Load, 2V Output

Analysis

Time Domain (Transient)

Run to time: 2ms

Start saving data after: 0ms

Maximum step size: 100n

Skip the initial transient bias point calculation (SKIPBP)

Parametric Sweep

Global parameter

Parameter name: RL

Value list: 4, 8

.Options

RELTOL: 0.01

VNTOL: 1.0u

ABSTOL: 1.0n

CHGTOL: 0.01p


GMIN: 1.0E-12

ITL1: 500

ITL2: 200

ITL4: 10

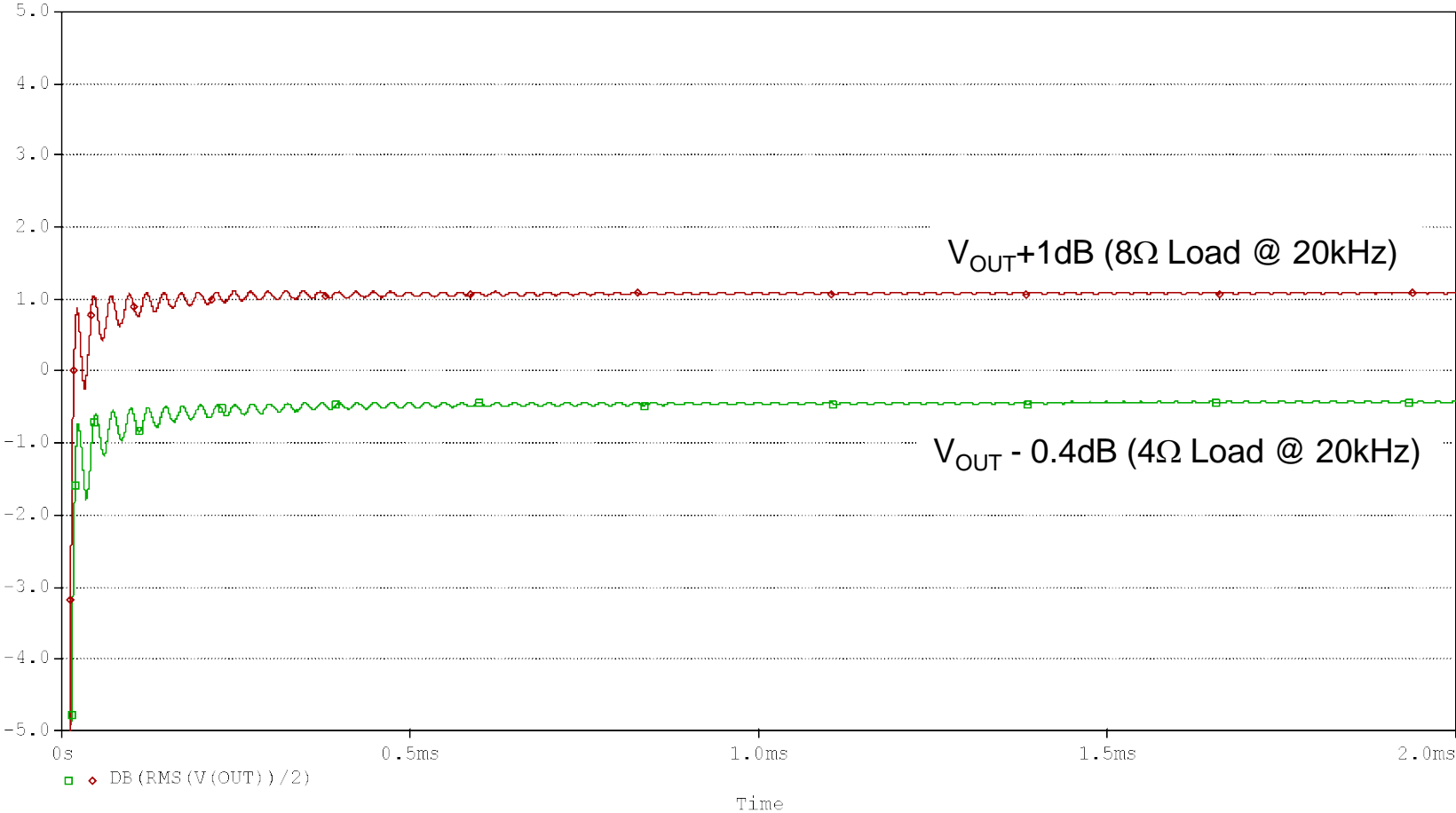Specifications : Frequency Response Simulation Result



Note : P_O [W] vs. V_{IN} [V_{PEAK}]


$$V_{in} [V_{peak}] = \frac{1.4142 \times \sqrt{P_o \times R_{load}}}{G_v}$$

- ▶ P_o [W] = power output
- ▶ R_{load} [Ω] = Load resistance
- ▶ G_v = Amplifier voltage gain







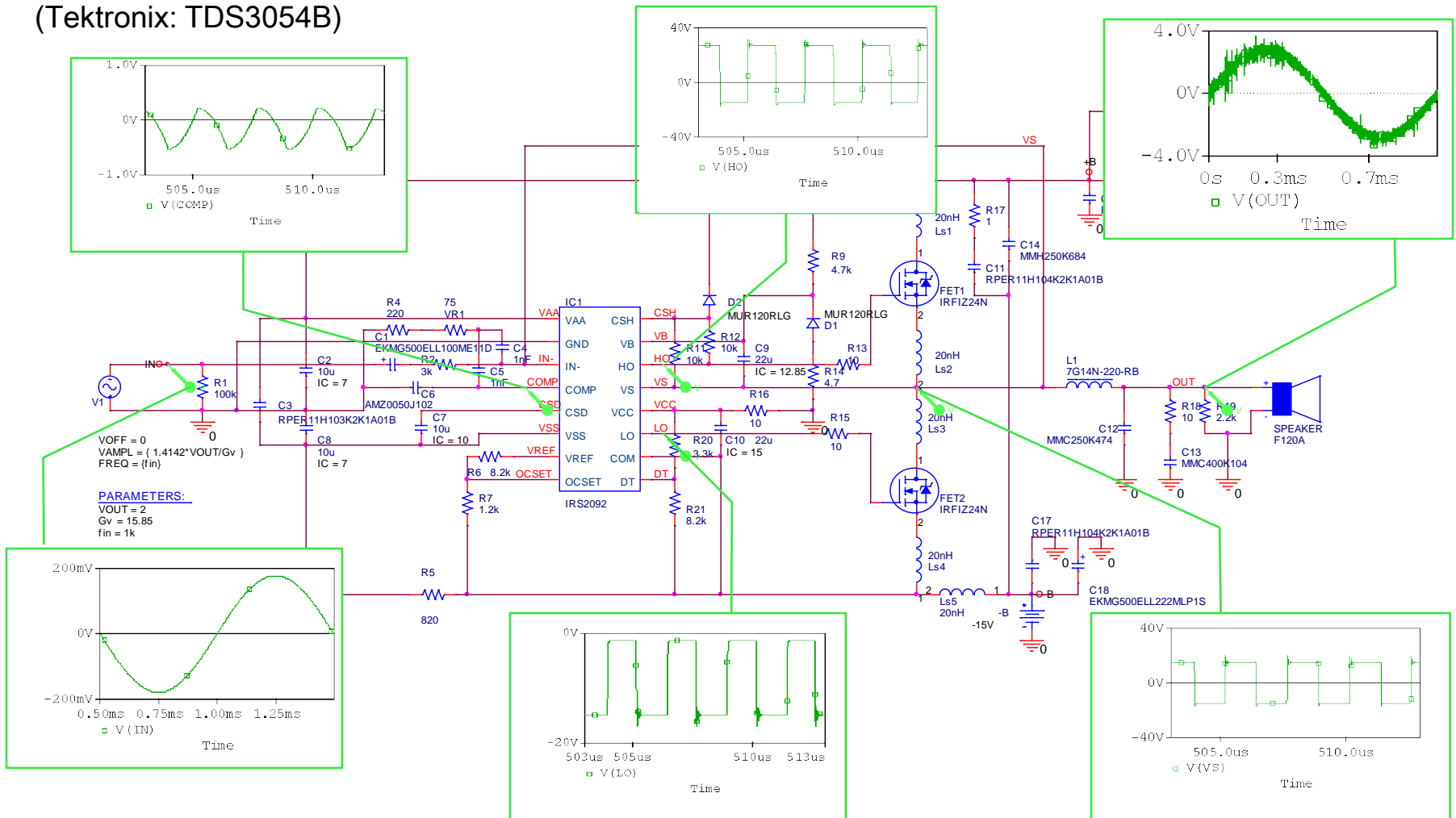2. Waveforms Evaluation





Class D amplifier circuit are simulated and compared with measured waveforms from oscilloscope (Tektronix: TDS3054B)




3. Simulated vs. Measured Waveform (1/3)

  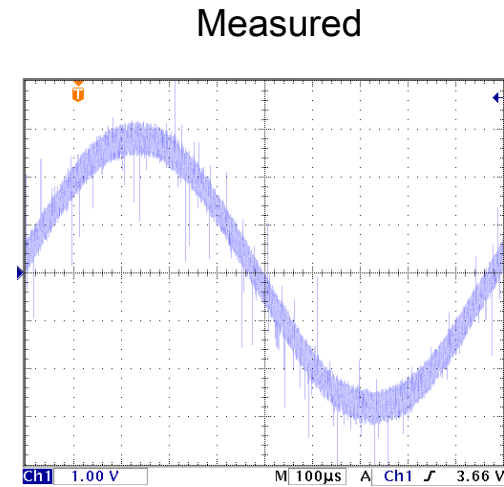 

3. Simulated vs. Measured Waveform (2/3)

  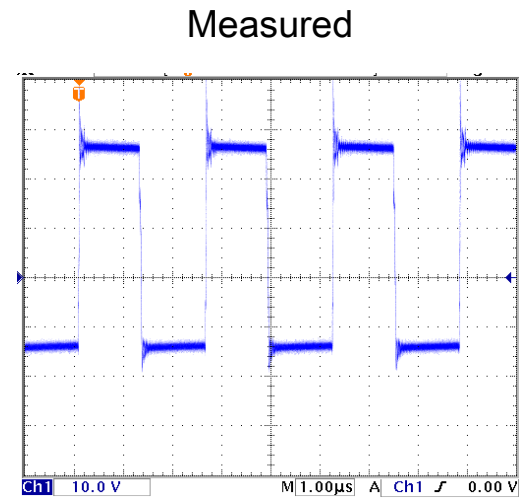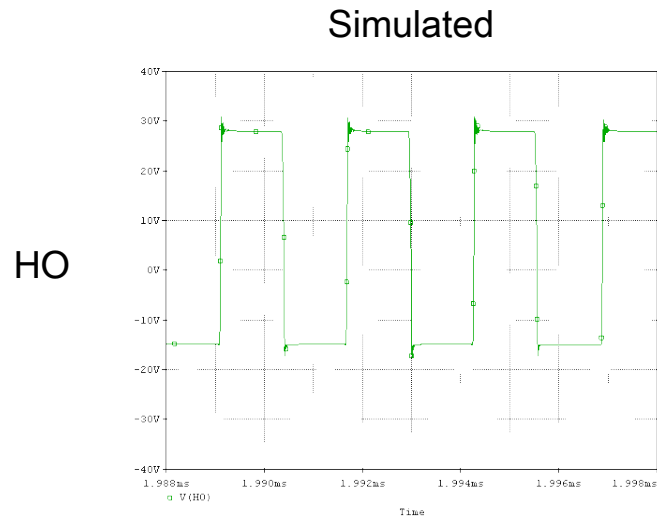


3. Simulated vs. Measured Waveform (3/3)

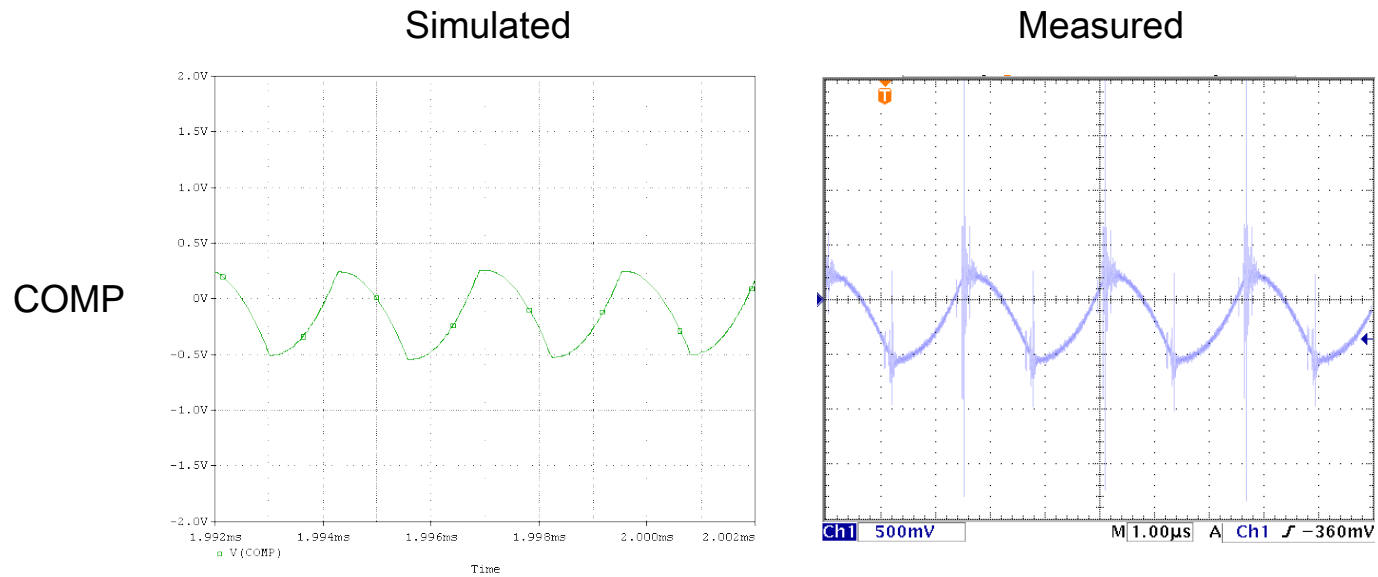

4. Voltage gain of the amplifier – G_V

$$G_V = \frac{R_{FB}}{R_{IN}}$$

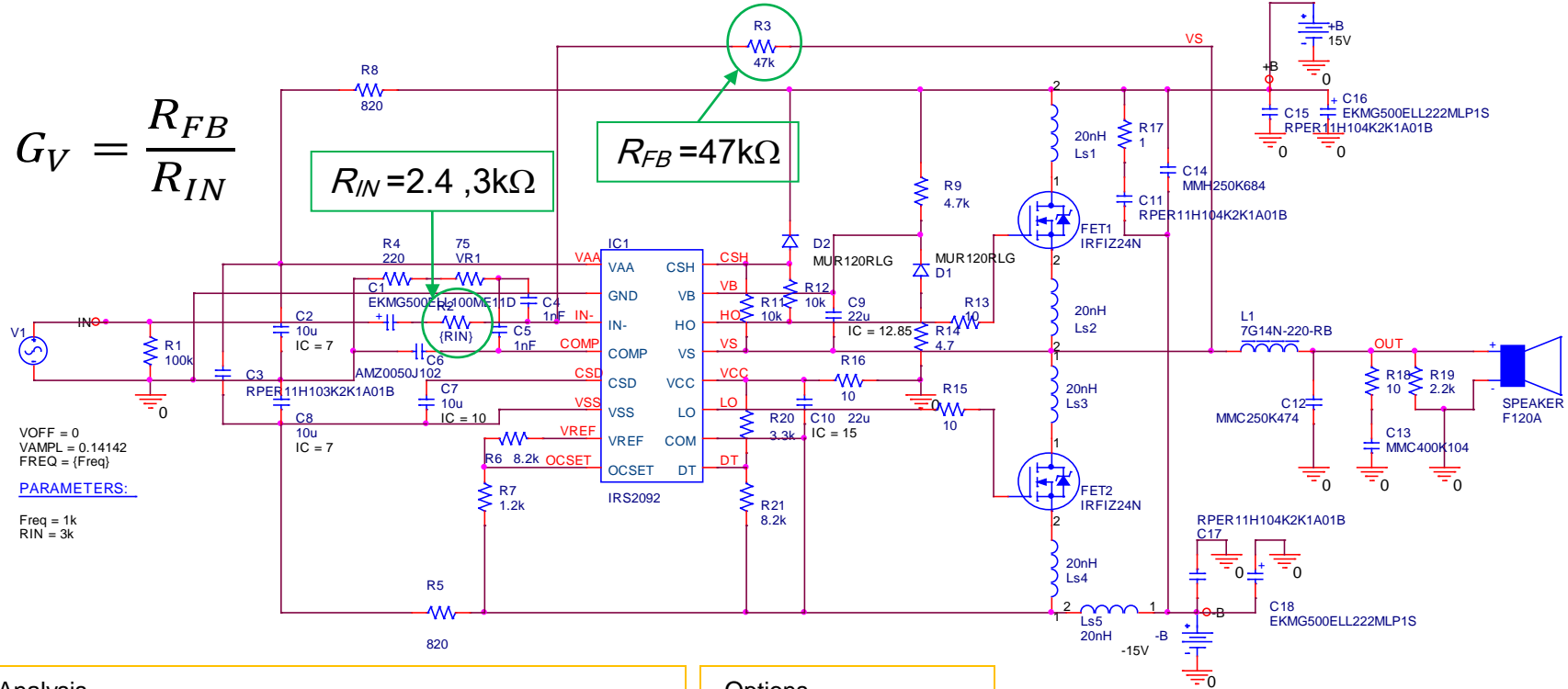


Analysis
 Time Domain (Transient)
 Run to time: 1ms
 Start saving data after: 100n
 Maximum step size: 100n
 Skip the initial transient bias point calculation (SKIPBP)

Sweep variable
 Global parameter: RIN
 Value list: 2.4k, 3k

.Options
 RELTOL: 0.01
 VNTOL: 1.0u
 ABSTOL: 1.0n
 CHGTOL: 0.01p
 GMIN: 1.0E-12
 ITL1: 500
 ITL2: 200
 ITL4: 10


4. Voltage gain of the amplifier – G_V

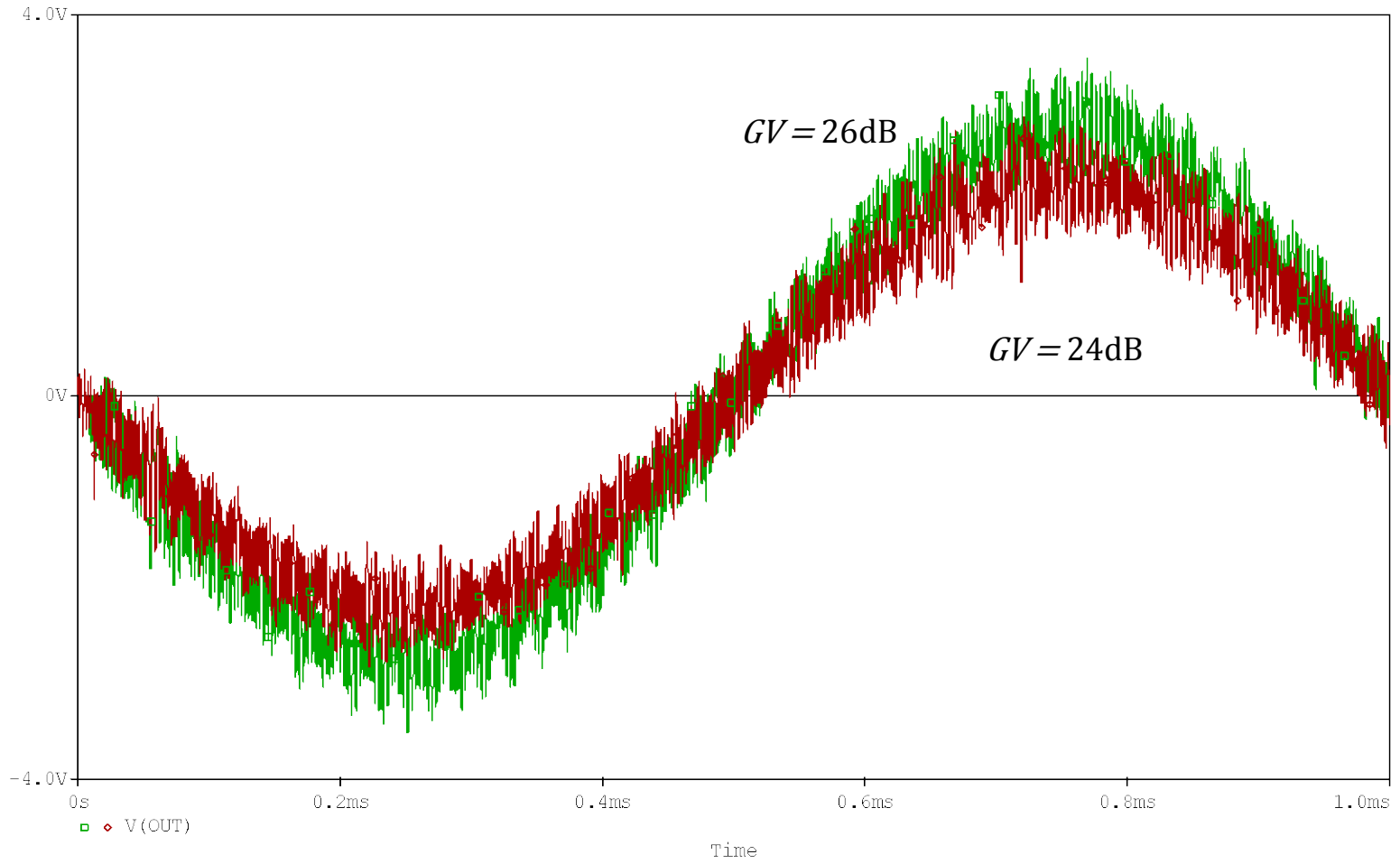

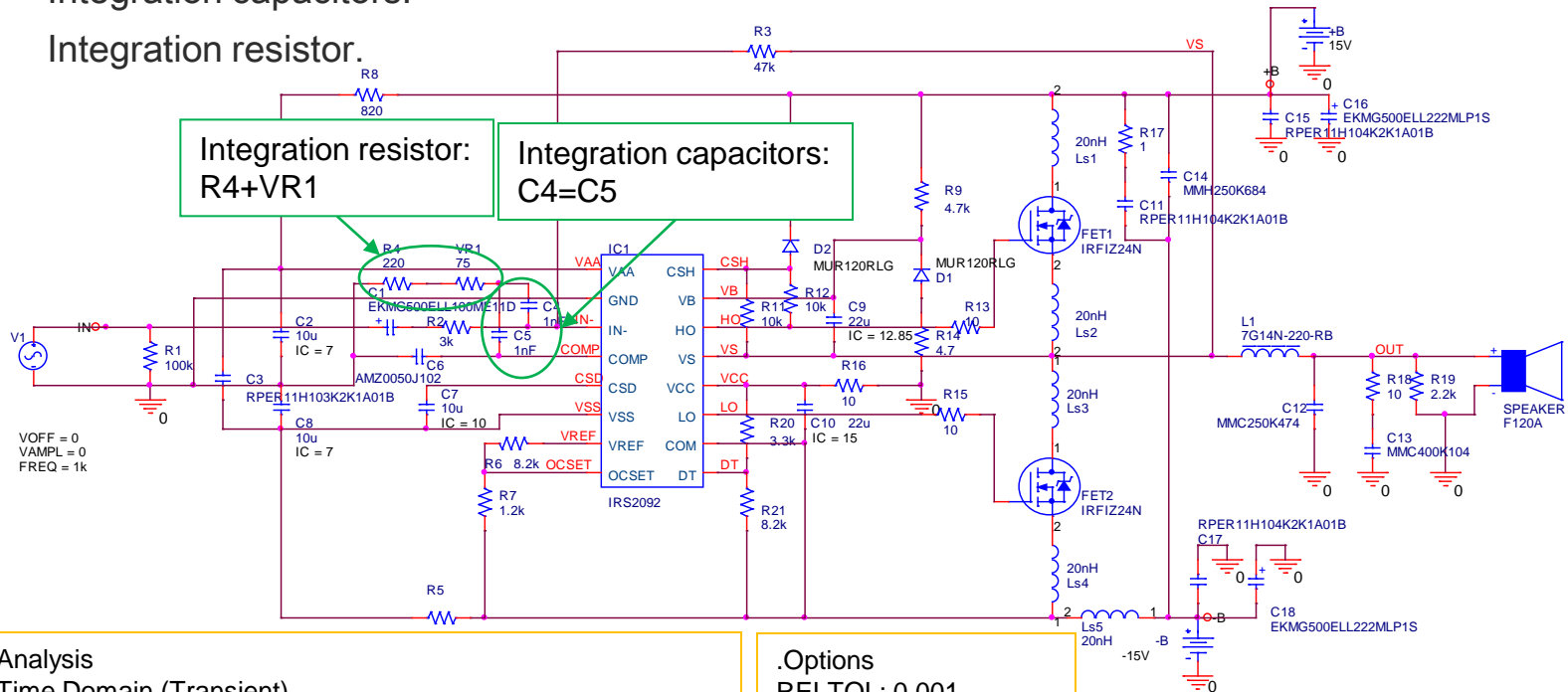5. Self-Oscillating Frequency


Self oscillating frequency is design by setting the following items

- Integration capacitors.
- Integration resistor.




5. Self-Oscillating Frequency

Simulated

 

Measured

 


6. Dead-time


Dead-time Mode	R20	R21
DT1 (25ns)	3.3k	8.2k
DT2 (40ns)	5.6k	4.7k
DT3 (65ns)	8.2k	3.3k
DT4 (105ns)	-	< 10k

Analysis
 Time Domain (Transient)
 Run to time: 1ms
 Start saving data after: 0.5ms
 Maximum step size: 40ns
 Skip the initial transient bias point calculation (SKIPBP)

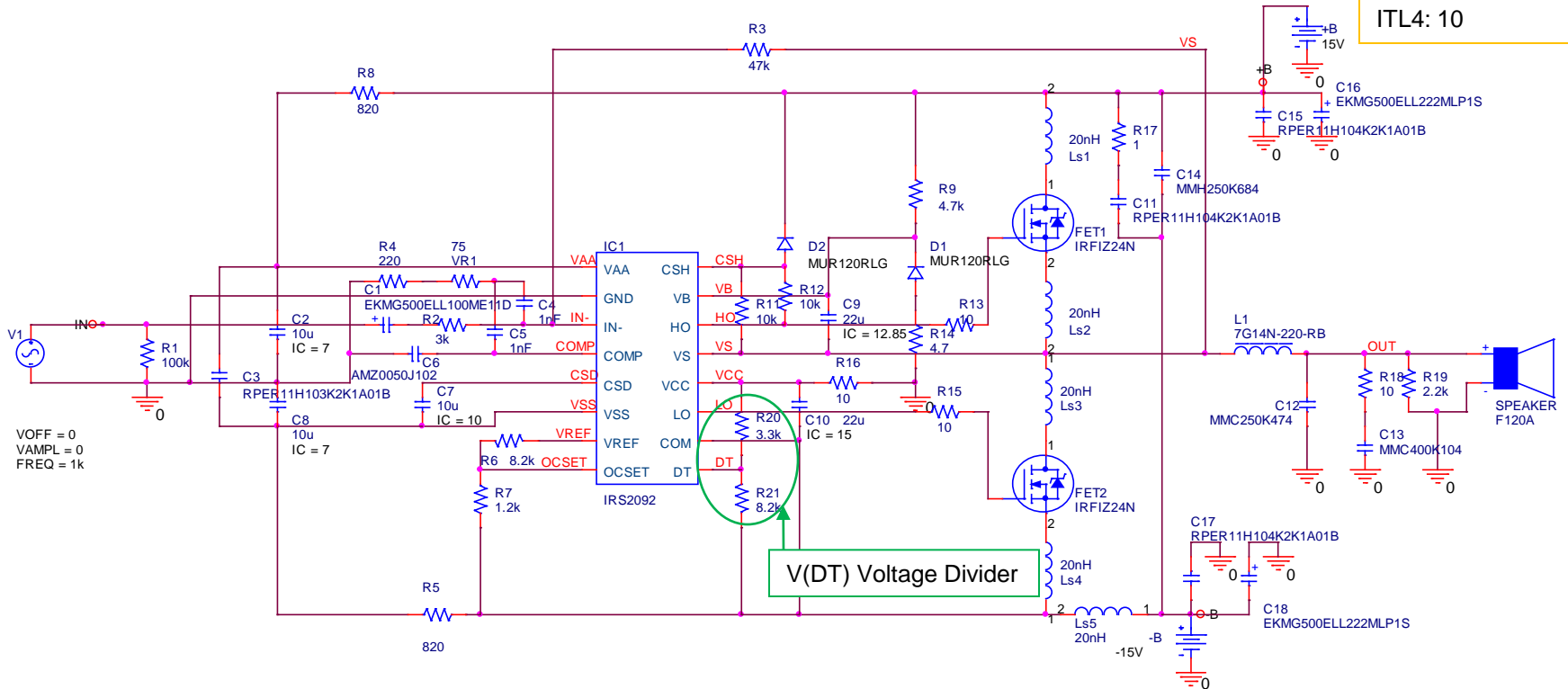
.Options
 RELTOL: 0.001
 VNTOL: 1.0u
 ABSTOL: 1.0n
 CHGTOL: 0.01p
 GMIN: 1.0E-12
 ITL1: 500
 ITL2: 200
 ITL4: 10




Dead-time DT1(25ns)

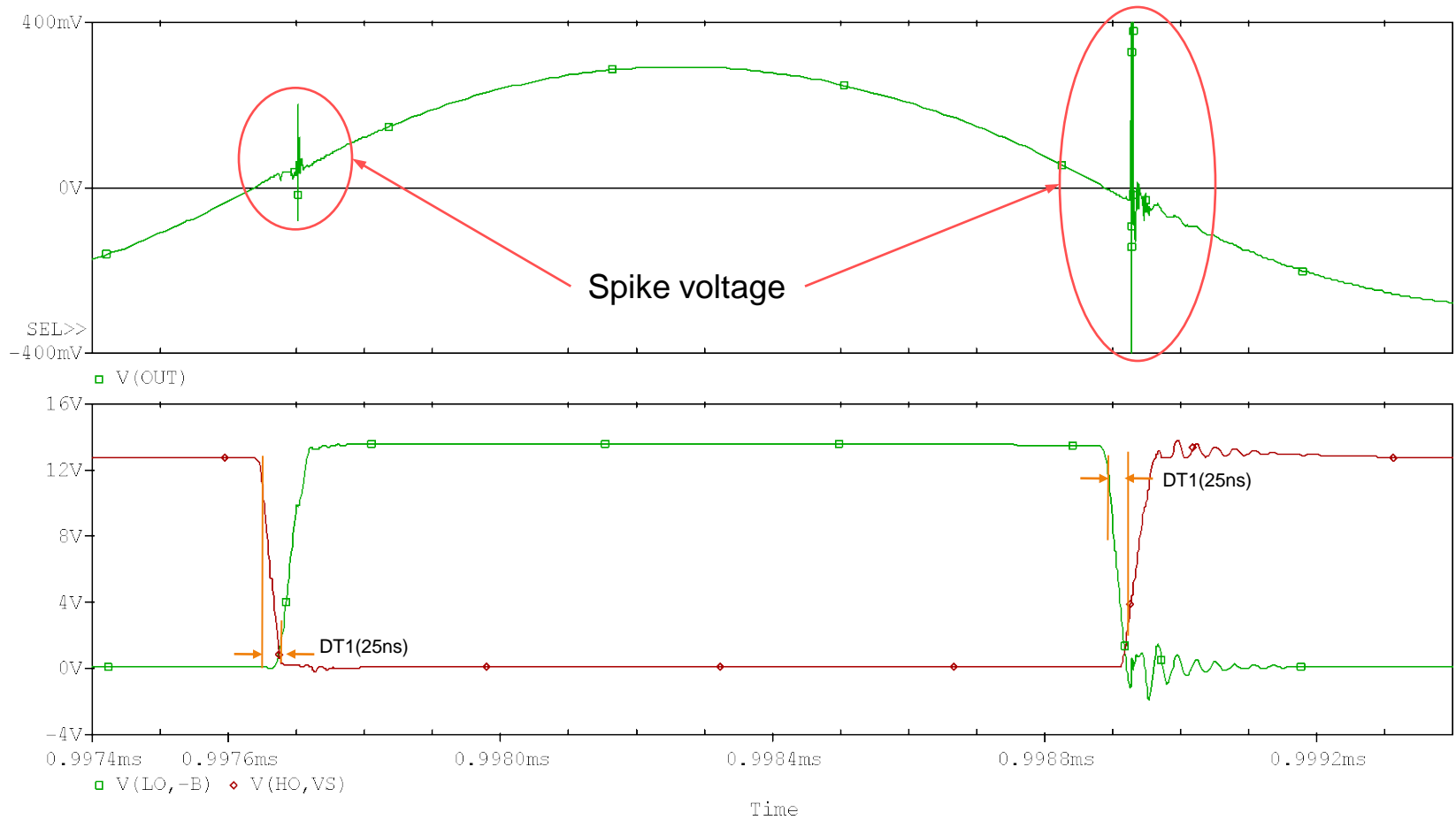


Dead-time DT3(65ns)

 

Turn-on transient: C7 = 10uF

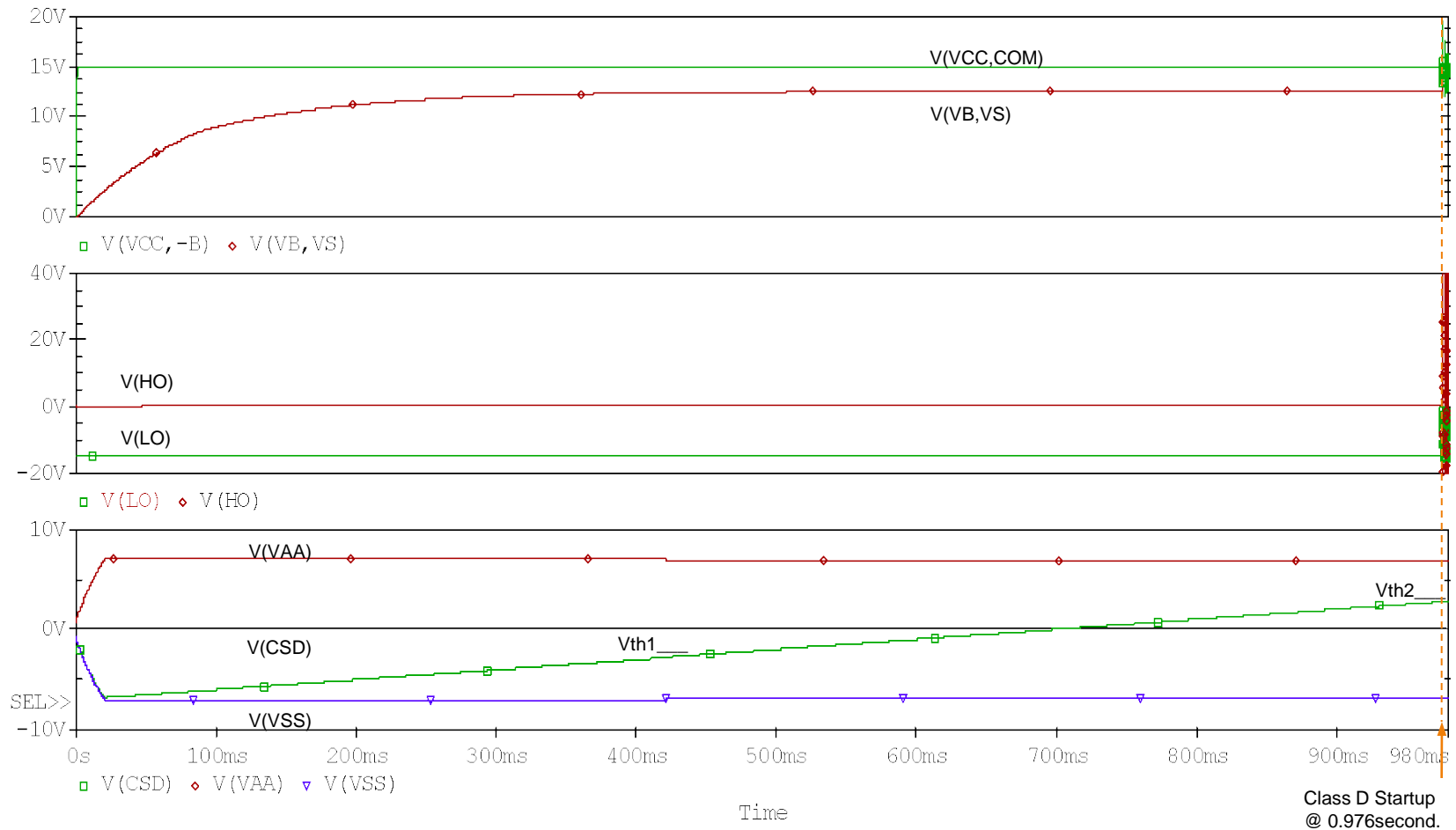


Turn-on transient: C7 = 5uF

 

Class D Startup
@ 0.488second.


Turn-on transient: C7 = 3.3uF

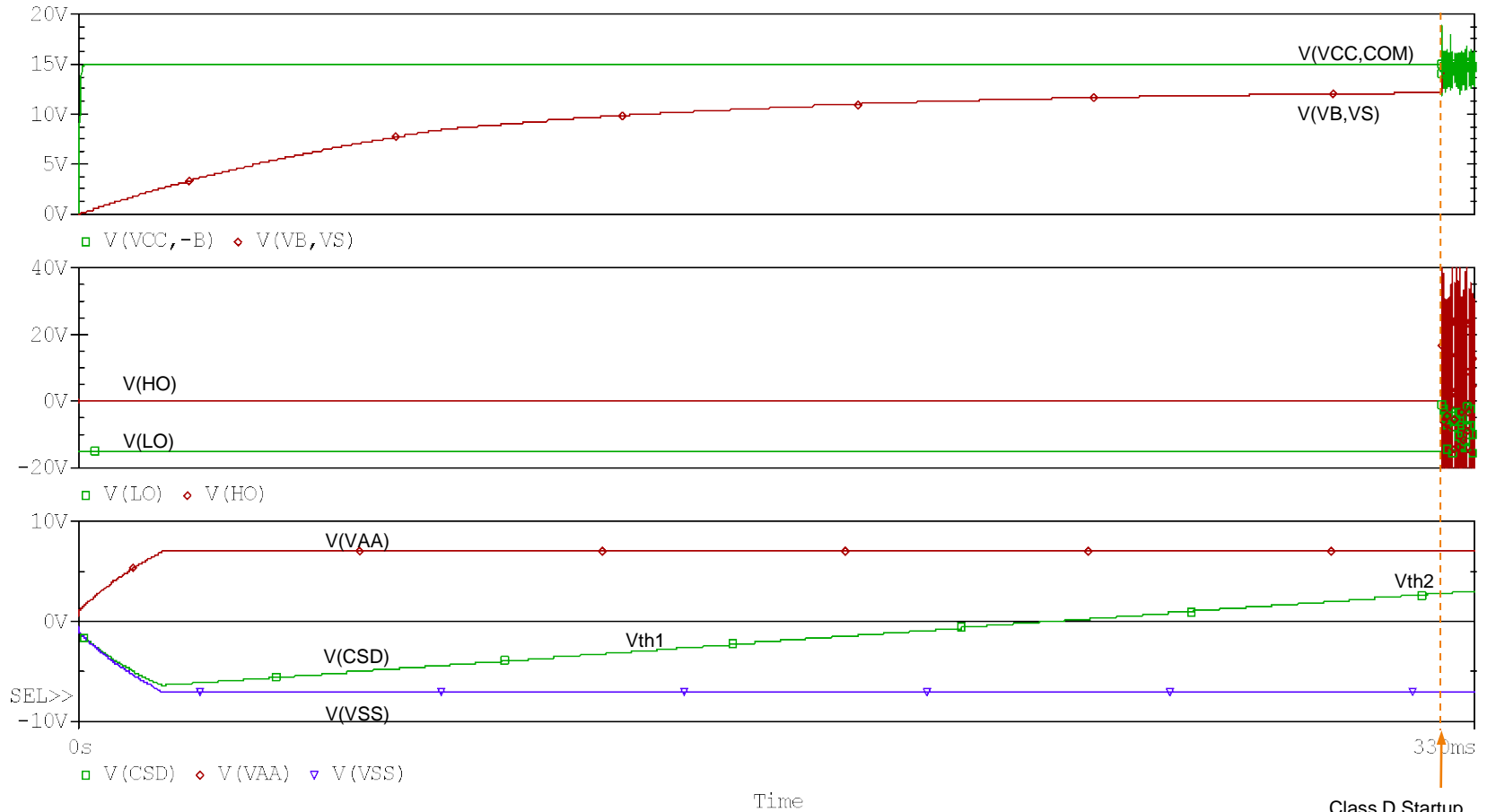


Class D Startup
@ 0.320second.

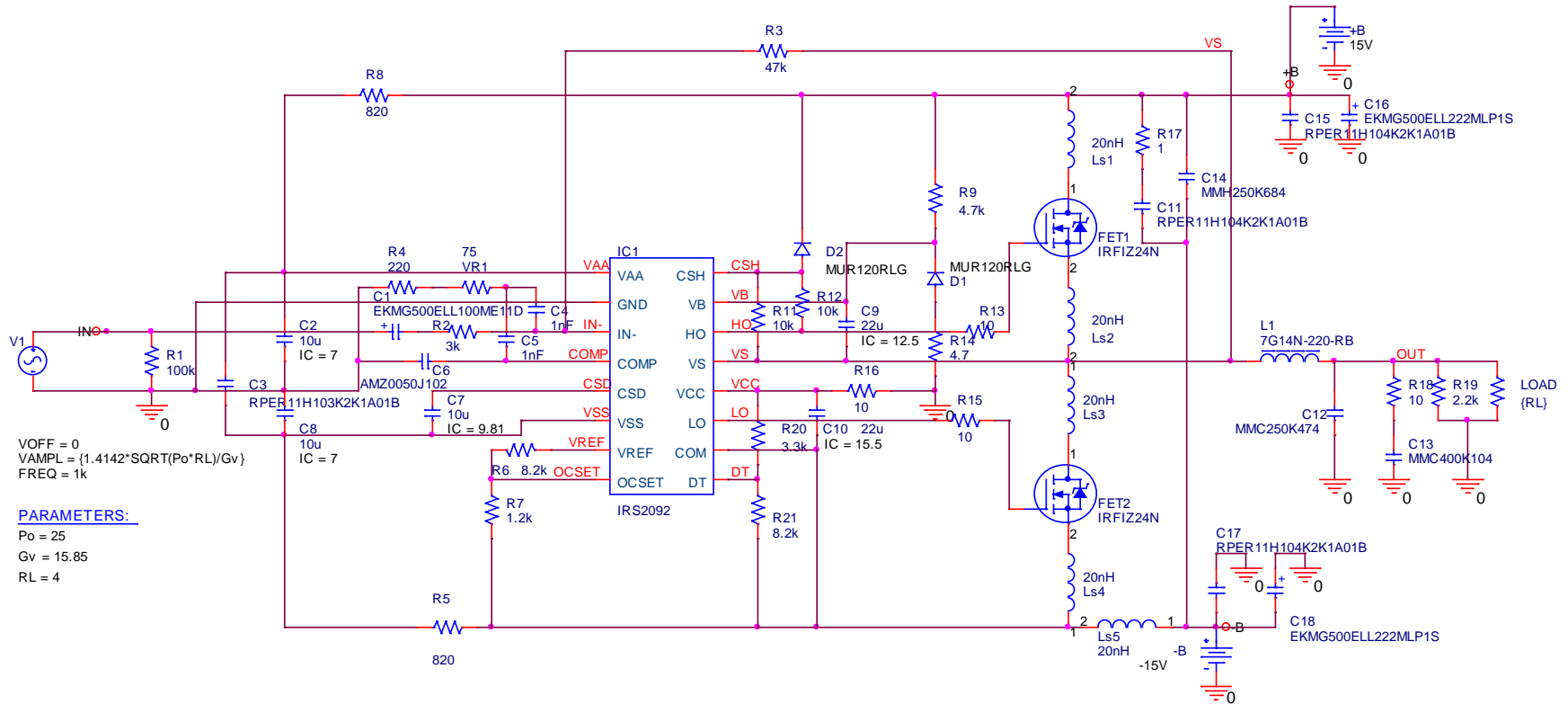8. Components stress

- This simulation shows how voltage and current are applied to each components at the maximum load condition (25W,4ohm).



 
Components Stress Simulated Result for Diodes, FETs, Inductor, and 4ΩLoad



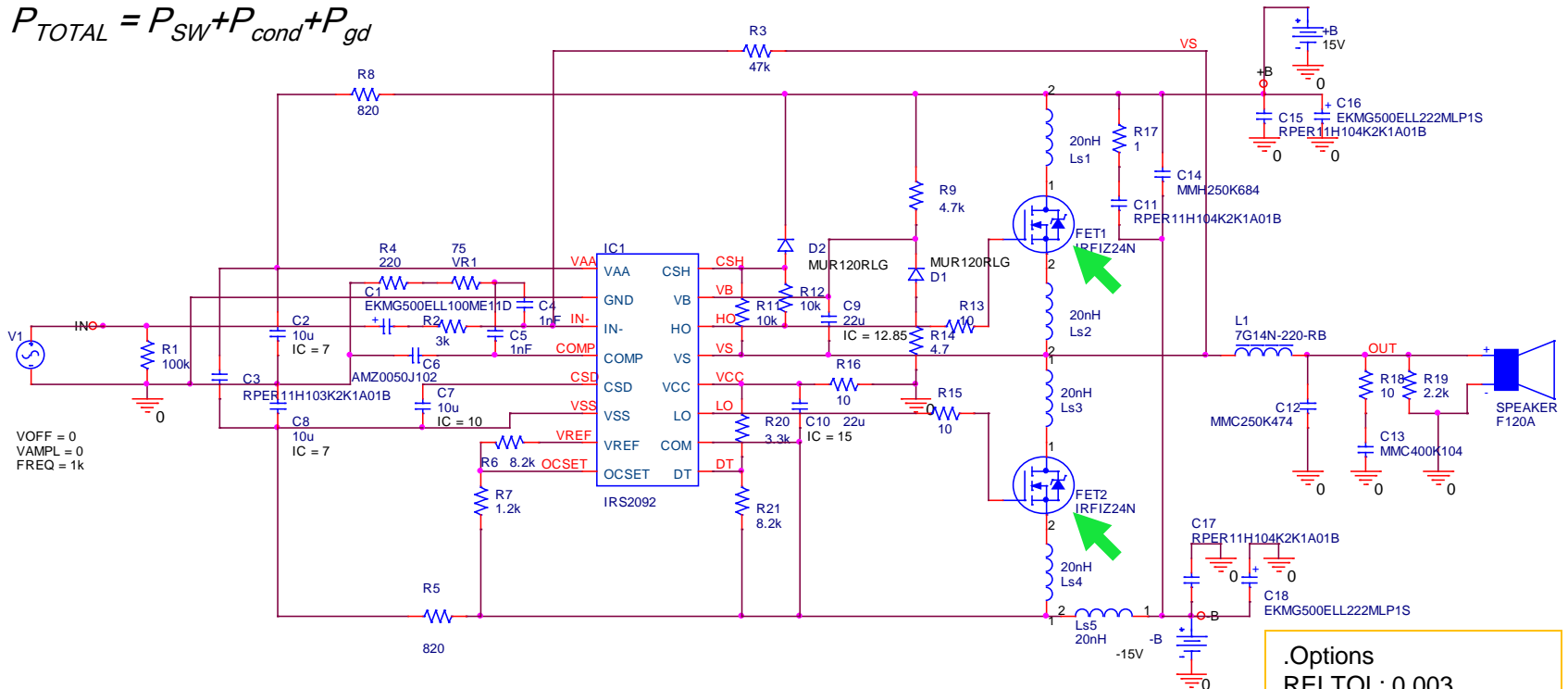9. Power losses in the MOSFETs

The total power loss in MOSFET are given by:

$$P_{TOTAL} = P_{SW} + P_{cond} + P_{gd}$$



Analysis

Time Domain (Transient)

Run to time: 500us

Start saving data after: 100n

Maximum step size: 2n

Skip the initial transient bias point calculation (SKIPBP)

.Options

RELTOL: 0.003

VNTOL: 1.0m

ABSTOL: 100n

CHGTOL: 0.01p

GMIN: 1.0E-12

ITL1: 500



ITL2: 200

ITL4: 20

Power losses FET1(Standard Model)

FET1: ID and VDS are simulated and compared with scope (Tektronix: TDS3054B) waveforms

 
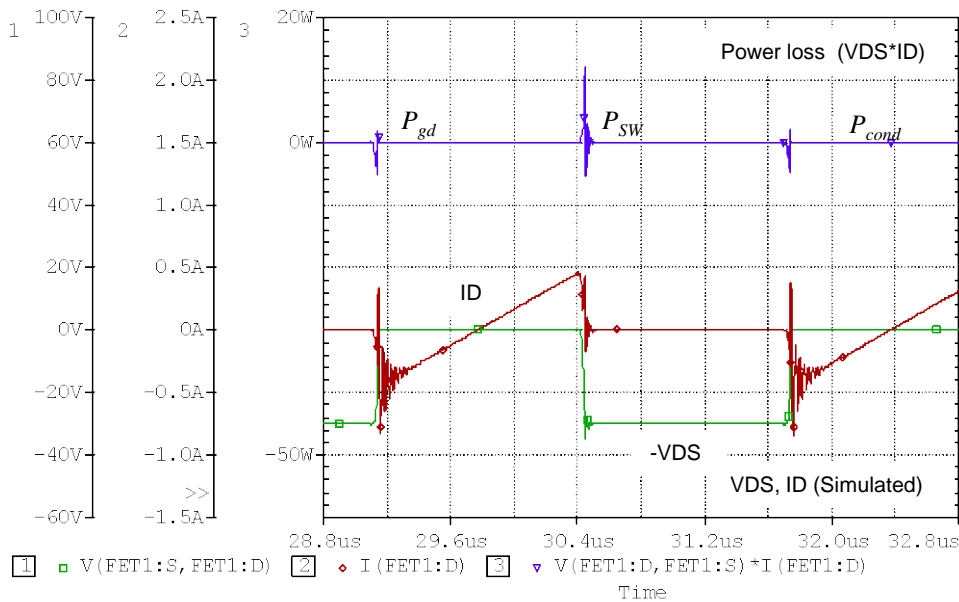
P_{SW} , P_{cond} , and P_{gd} are calculated by PSpice.



Power losses FET2(Standard Model)

FET2: ID and VDS are simulated and compared with scope (Tektronix: TDS3054B) waveforms

  
P_{SW} , P_{cond} , and P_{gd} are calculated by PSpice.



Power losses in the MOSFETs (Professional model)

The total power loss in MOSFET are given by:
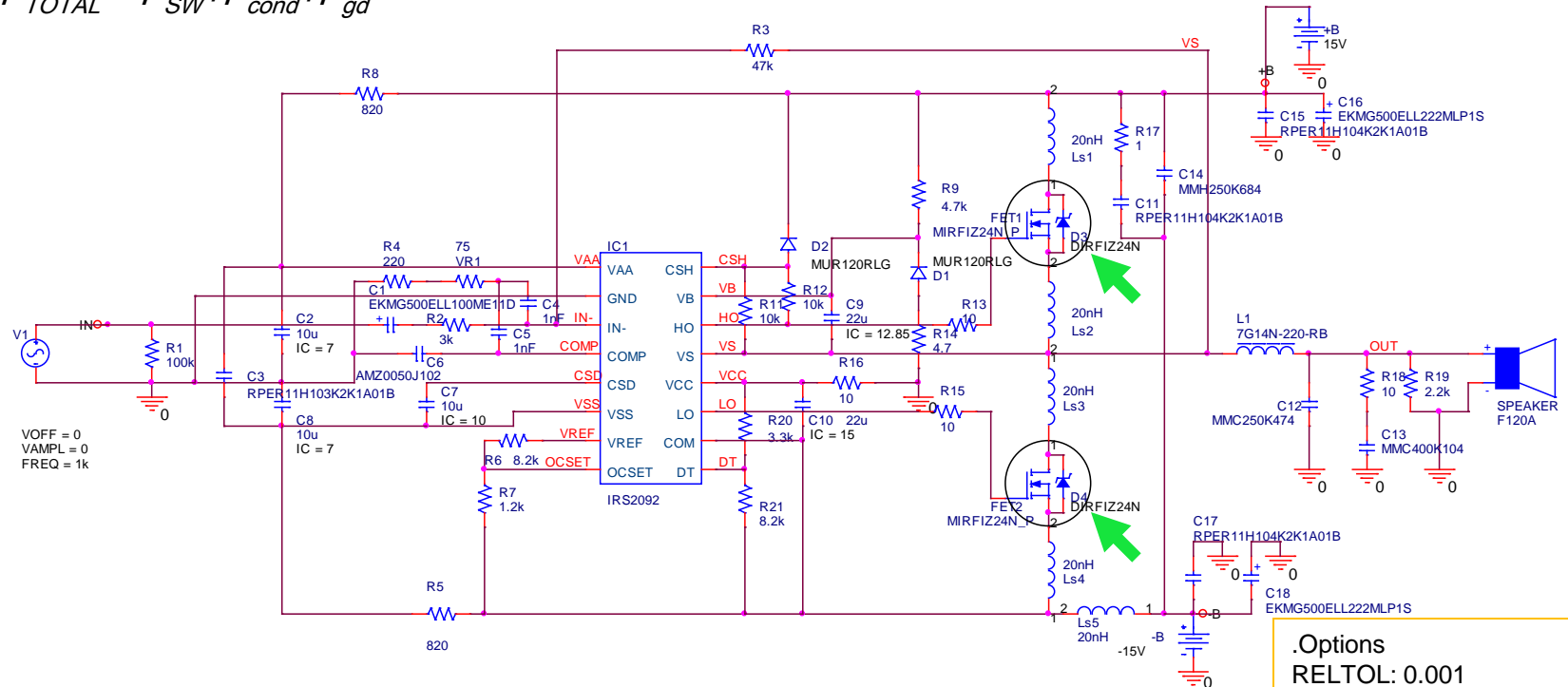
$$P_{TOTAL} = P_{SW} + P_{cond} + P_{gd}$$





Analysis
 Time Domain (Transient)
 Run to time: 500us
 Start saving data after: 100n
 Maximum step size: 2n
 Skip the initial transient bias point calculation (SKIPBP)

.Options
 RELTOL: 0.001
 VNTOL: 1.0m
 ABSTOL: 100n
 CHGTOL: 0.01p
 GMIN: 1.0E-12
 ITL1: 500
 ITL2: 200
 ITL4: 10

Power losses FET1(Professional Model)

FET1: ID and VDS are simulated and compared with scope (Tektronix: TDS3054B) waveforms

 
 
P_{SW} , P_{cond} , and P_{gd} are calculated by PSpice.



Power losses FET2(Professional Model)



FET2: ID and VDS are simulated and compared with scope (Tektronix: TDS3054B) waveforms

  P_{SW} , P_{cond} , and P_{gd} are calculated by PSpice.



FET: IRFIZ24N Qg Standard vs. Professional Model

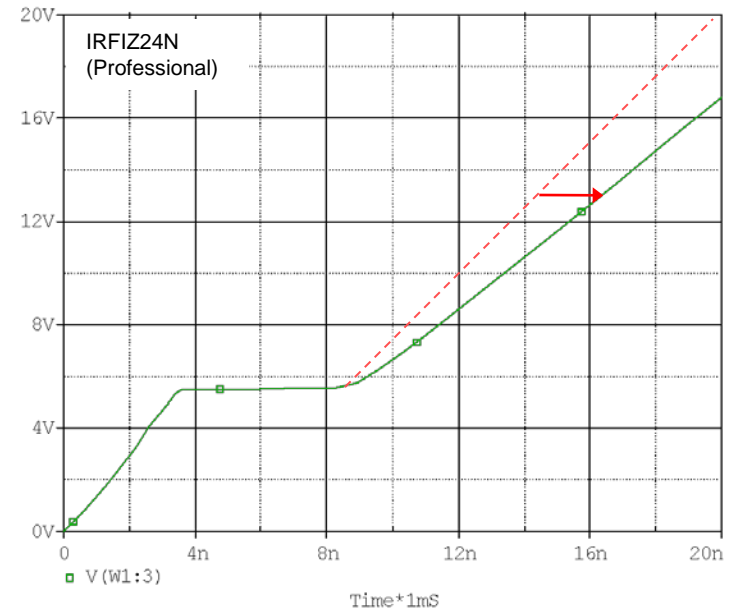
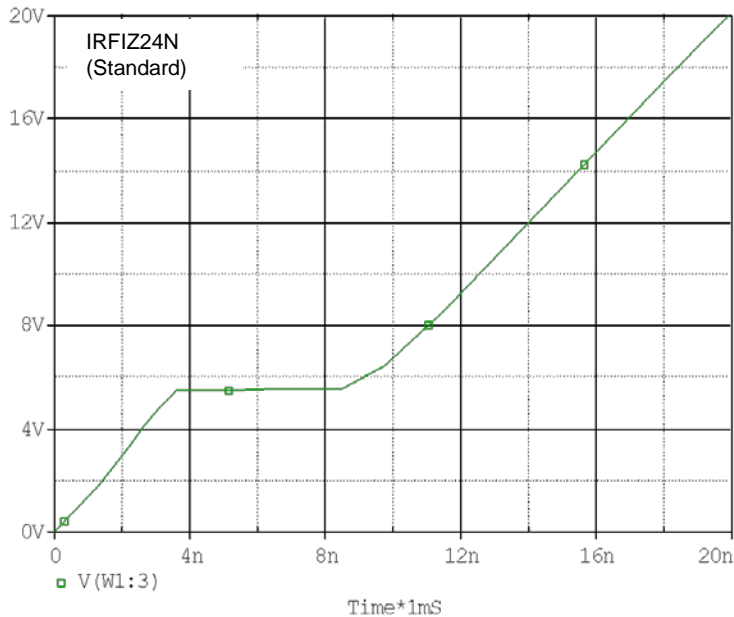
- Gate charge characteristics in Professional model has more accurate results than standard model.



$V_{DD}=44V, I_D=10A$ $, V_{GS}=10V$	Measurement	Simulation	Error (%)
Standard Model: Qg(nc)	13.400	12.543	-6.396
Professional Model: Qg(nc)	13.400	13.409	0.067

FET: IRFIZ24N P_{gd} Standard vs. Professional Model

  
- ▶ Simulated P_{gd} , Standard model compared to Professional model, shows some different result caused by different Qg characteristics of the models.



※ Professional model requires more simulation time and might cause some convergence error.

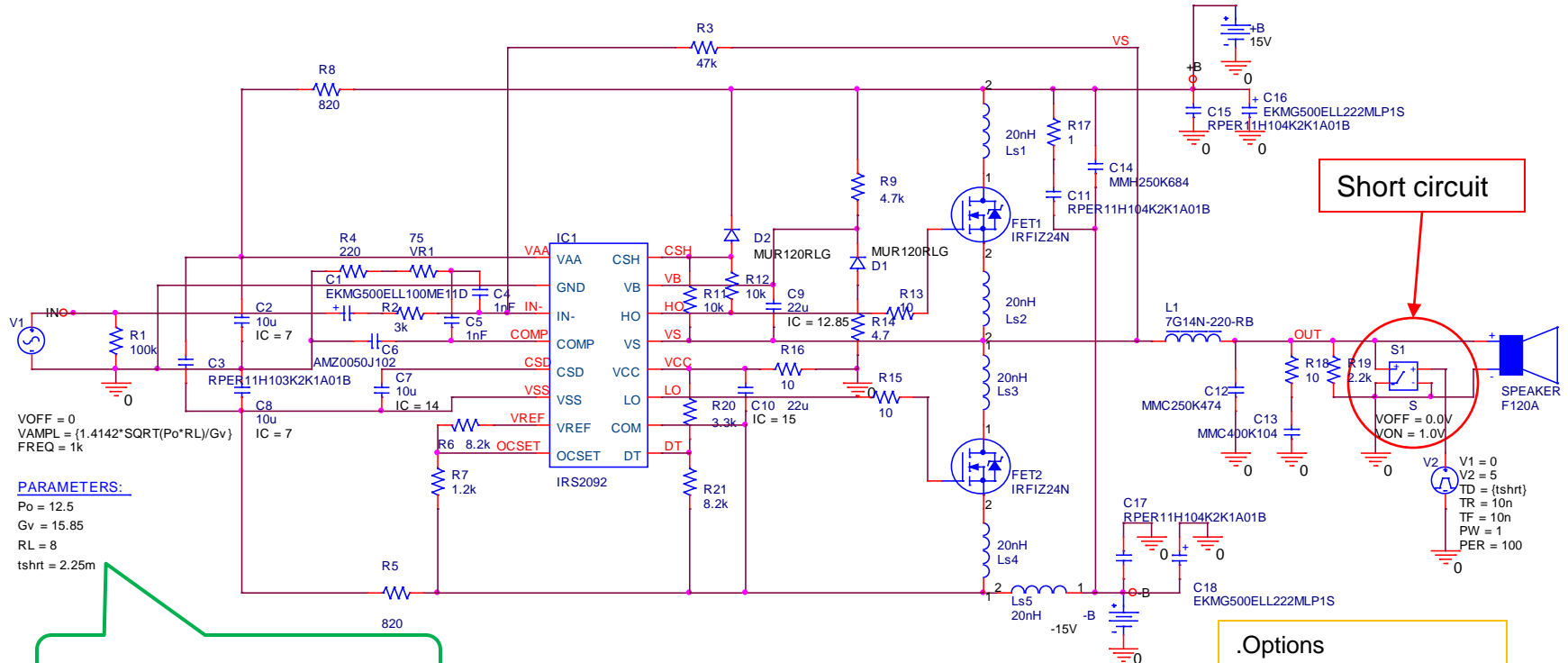10. Short circuit vs. switching output shutdown

- ▶ This simulation will show how the IRS2092 responds to a short circuit condition.



VOFF = 0
 VAMPL = $(1.4142 \cdot \sqrt{Po \cdot RL}) / Gv$
 FREQ = 1k

PARAMETERS:


Po = 12.5
 Gv = 15.85
 RL = 8
 tshrt = 2.25m

Short circuit at 2.25ms.


Analysis
 Time Domain (Transient)
 Run to time: 4ms
 Start saving data after: 100n
 Maximum step size: 100n
 Skip the initial transient bias point calculation (SKIPBP)

.Options
 RELTOL: 0.01
 VNTOL: 1.0u
 ABSTOL: 1n
 CHGTOL: 0.01p
 GMIN: 1.0E-12
 ITL1: 500
 ITL2: 200
 ITL4: 10

 Short Circuit vs. Switching Output Shutdown (Positive Side)




 Short Circuit vs. Switching Output Shutdown (Negative Side)



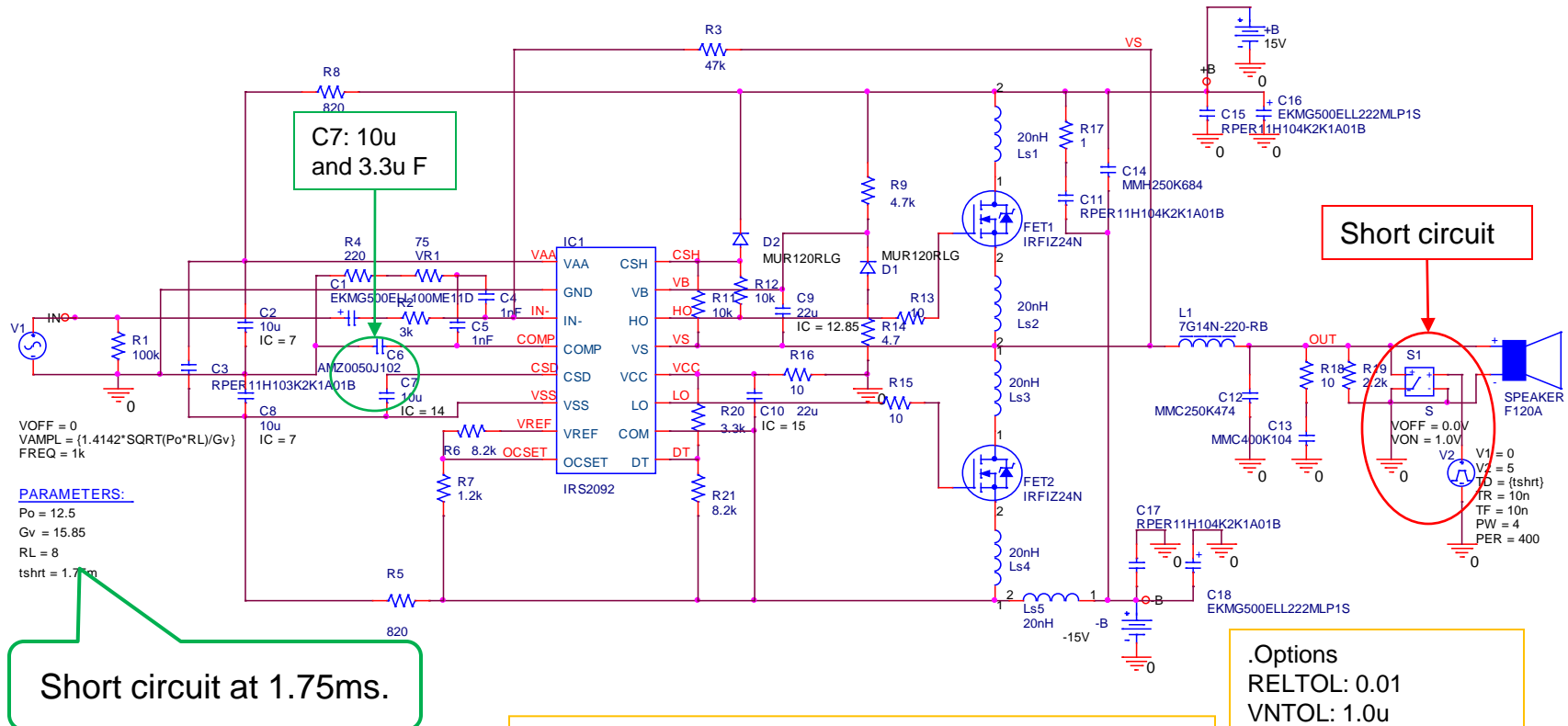
11. Short Circuit Response

- ▶ This simulation will show how the IRS2092 responds to a short circuit condition.




Analysis
 Time Domain (Transient)
 Run to time: 1.25s
 Start saving data after: 100n
 Maximum step size: 100u
 Skip the initial transient bias point calculation (SKIPBP)

Short Circuit Response: C7 = 10uF

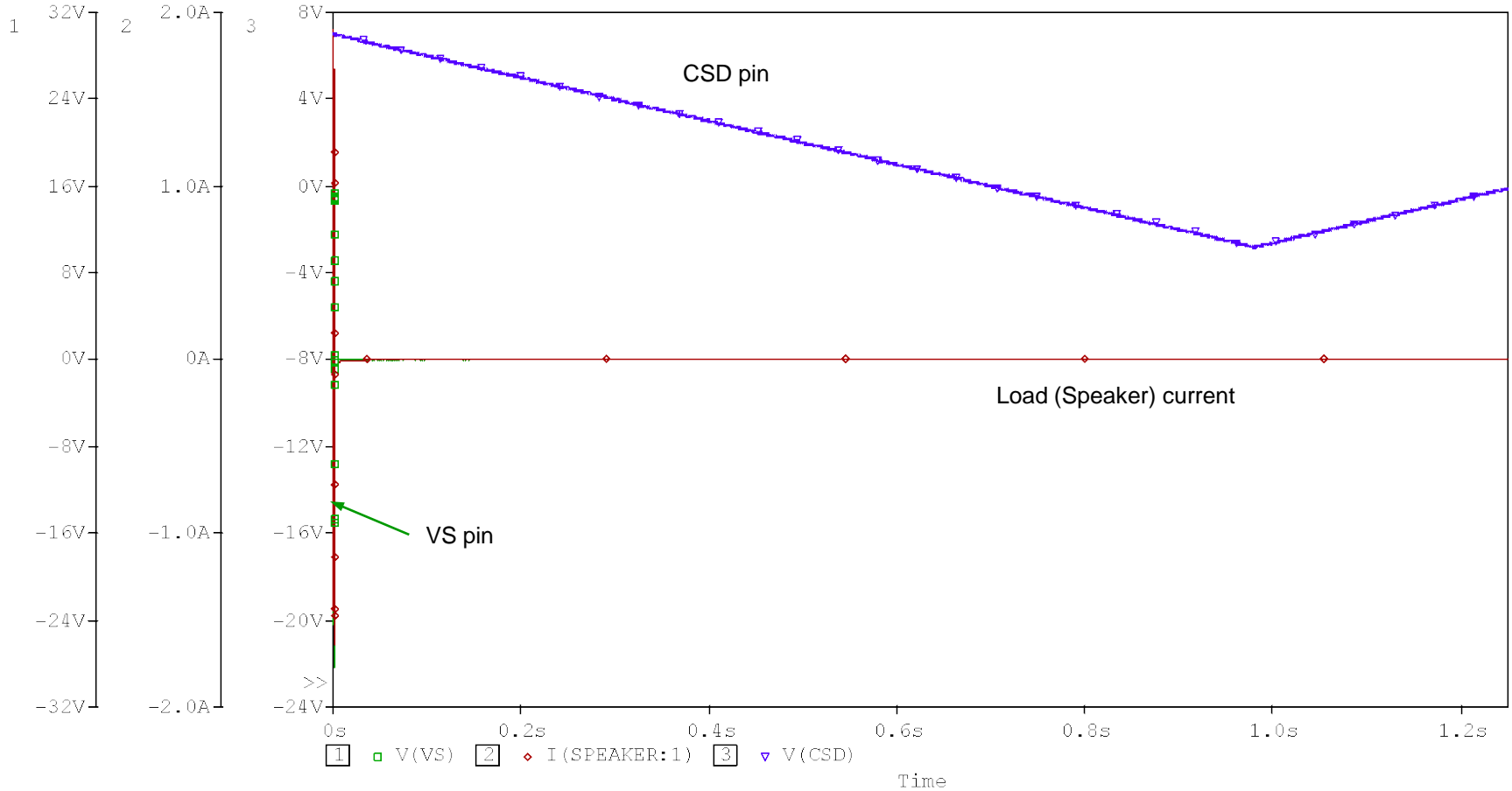


Short Circuit Response: C7 = 3.3uF

 

 12. Capacitor models

- ▶ Capacitor models are needed for the simulation to include spike voltage.




VOFF = 0
VAMPL = 0
FREQ = 1k

Analysis
Time Domain (Transient)
Run to time: 1ms
Start saving data after: 0.5m
Maximum step size: 40n
 Skip the initial transient bias point calculation (SKIPBP)


.Options
RELTOL: 0.001
VNTOL: 1.0u
ABSTOL: 1.0n
CHGTOL: 0.01p
GMIN: 1.0E-12
ITL1: 500
ITL2: 200
ITL4: 10

Simulation Result (without Capacitor Model)

 Simulated (without output capacitor models)




Measured

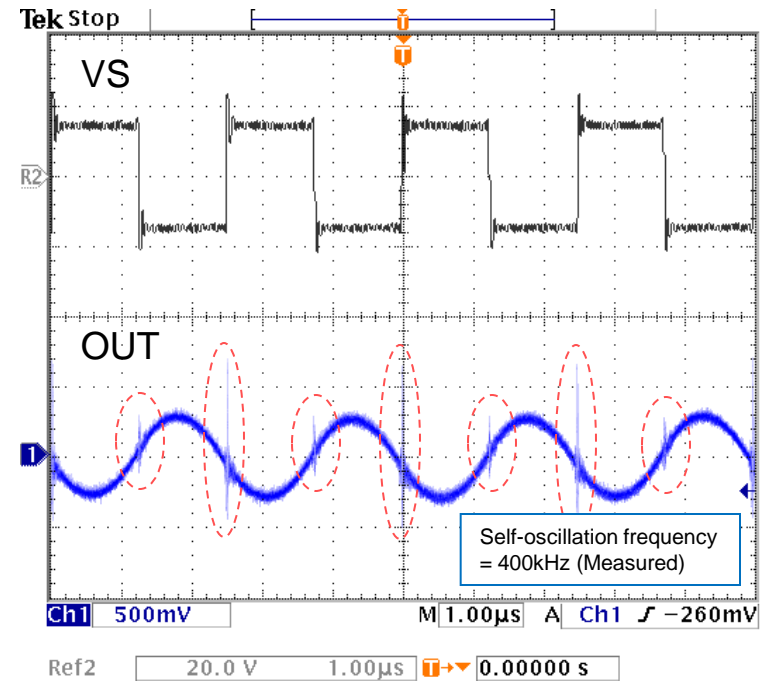


Simulation Result (with Capacitor Model)

Simulated (with output capacitor models)

 

Measured

 


13. Simulated Performance of the circuit with different FETs

IRFIZ24N Key Parameters		
V_{DS}	55	V
I_D	14	A
$R_{DS(ON)}$ typ. @ 10V	70	m Ω
Q_g typ.	13.4	nC
t_{ON} typ.	38.9	ns
t_{OFF} typ.	46	ns
Q_{rr} typ.	120	nC





IRFI4024H-117P Key Parameters		
V_{DS}	55	V
I_D	11	A
$R_{DS(ON)}$ typ. @ 10V	48	m Ω
Q_g typ.	8.9	nC
t_{ON} typ.	7.9	ns
t_{OFF} typ.	16.4	ns
Q_{rr} typ.	11	nC

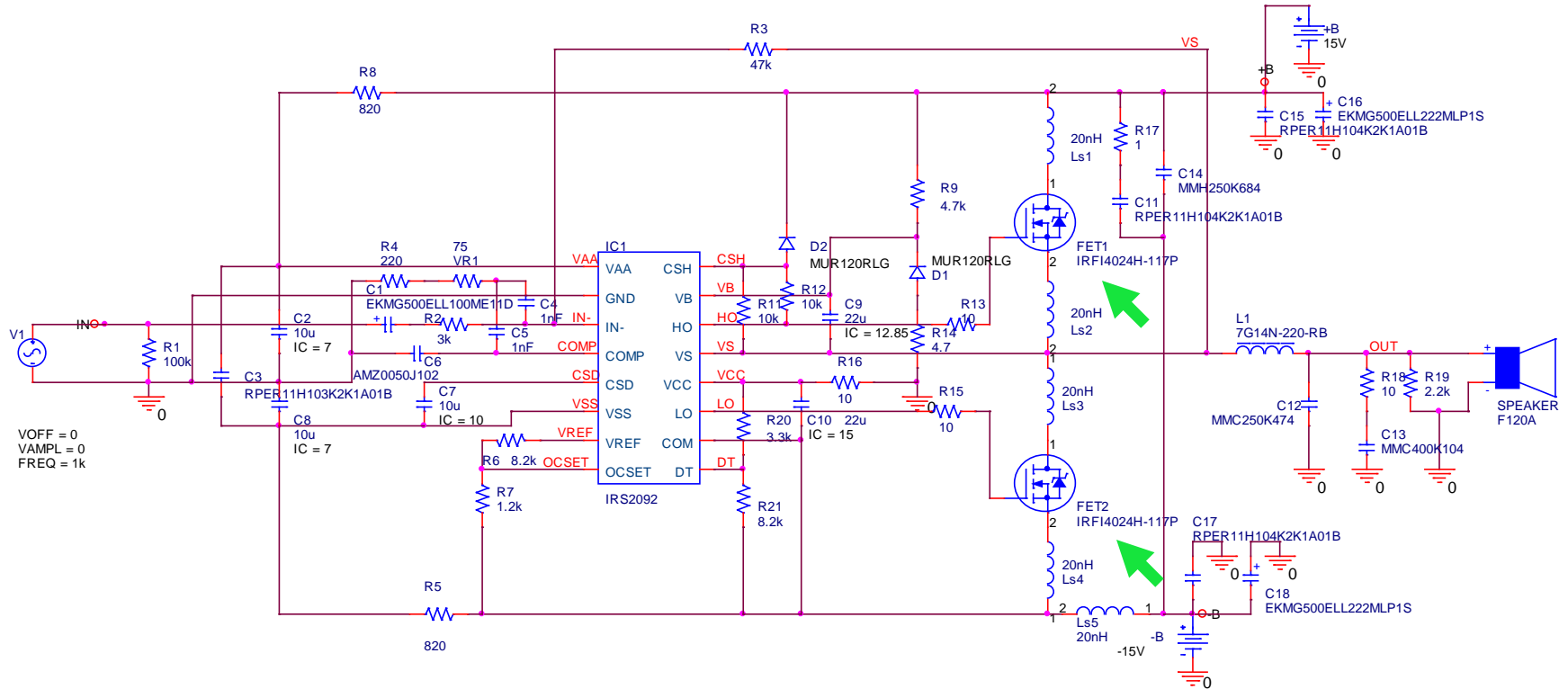Simulated Performance of the circuit with different FETs



	IRFIZ24N	IRFI4024H-117P
Efficiency (@ 25W, 4Ω)	93.505%	94.578%
Distortion (@ 1kHz, 4Ω, 10W)	0.0144 %THD	0.0201 %THD

    Simulated Performance of the circuit with different FETs



Simulations Index

Simulation	Folder Name
1. Efficiency Evaluation.....	Efficiency
2. THD Evaluation.....	THD
3. Frequency Response Evaluation.....	FrqRsp
4. Waveforms Evaluation.....	Waveforms
5. Voltage gain of the amplifier – G_v	Gv
6. Self-Oscillating Frequency.....	OSC
7. Dead-time Evaluation.....	DT
8. Turn-on transient.....	StartUp
9. Component stresses.....	Stress
10. Power losses in the MOSFETs (Standard model)	FET(STD)
11. Power loss in the MOSFETs (Professional Model)	FET(PRO)
12. Short Circuit vs. Switching Output Shutdown.....	Short
13. Short Circuit Response.....	ShrtRsp

