

# Get Started with DesignKit

Class D Audio Amplifier Using IRS2092


# Contents

---

	<b>Slide #</b>
1. DesignKit Simulations folders.....	3
2. How the initial condition are set?.....	4-5
3. Example of Using Design Kit.....	6
4. How to Estimate Design %Efficiency?.....	7-8
5. How to Estimate Output THD?.....	9-11
6. How to Estimate Frequency Response?.....	12-13
7. How to Create Reference Waveforms?.....	14-15
8. Change $R_{IN}$ (R2) and simulate to see change in $G_V$ .....	16-17
9. Use Design Kit to select proper VR value.....	18-19
10. Use Design Kit to Predict Spike Voltage vs. Dead-time setting.....	20-21
11. Use Design Kit to Develop the Design (Change the FETs).....	22-23
12. MOSFET Professional Model.....	24

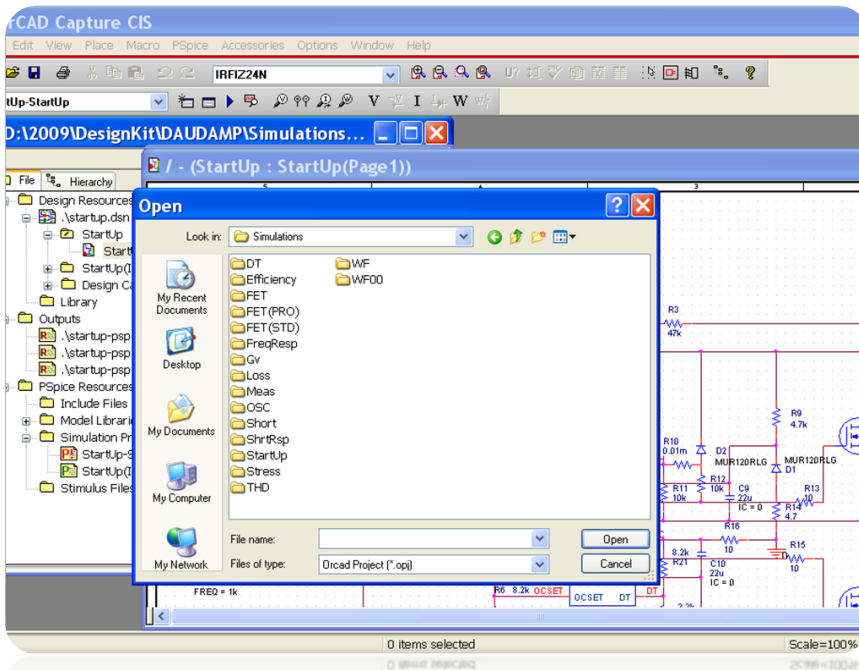
# 1. DesignKit Simulations folders

- ▶ Ready to use simulation projects
  - ✓ Test conditions are set and easily changeable.
  - ✓ Appropriate simulation settings and Initial Condition (.IC).
  - ✓ .Option setting is done without convergence problem.
  - ✓ Libraries are included and added.
  - ✓ Simulation results (ex. Power and %Efficiency) are calculated and displayed.




## 2. How the initial condition are set?

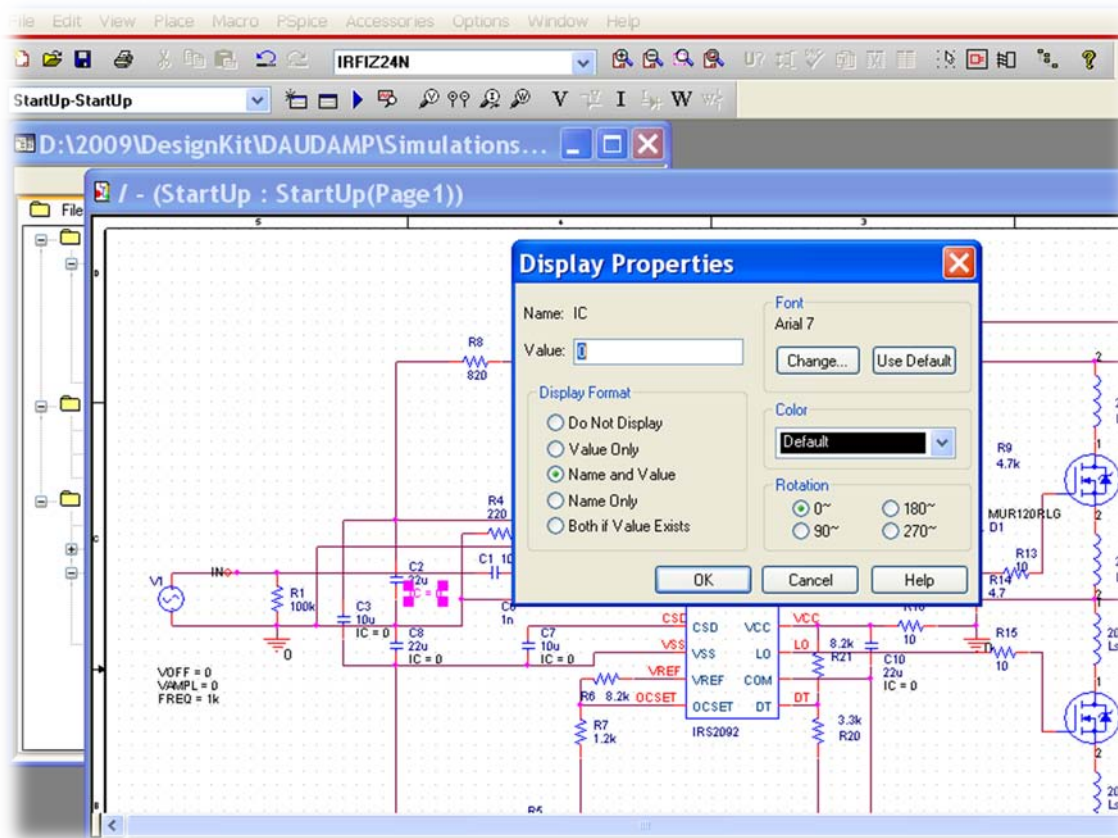1. Open Project: ...¥Simulations¥StartUp¥StartUp.opj .
2. Set initial value of charged-up capacitors (C2, C3, C7, C8, C9, and C10) to be zero (IC=0).
3. Run the simulation (0-1sec. or until circuit is startup).


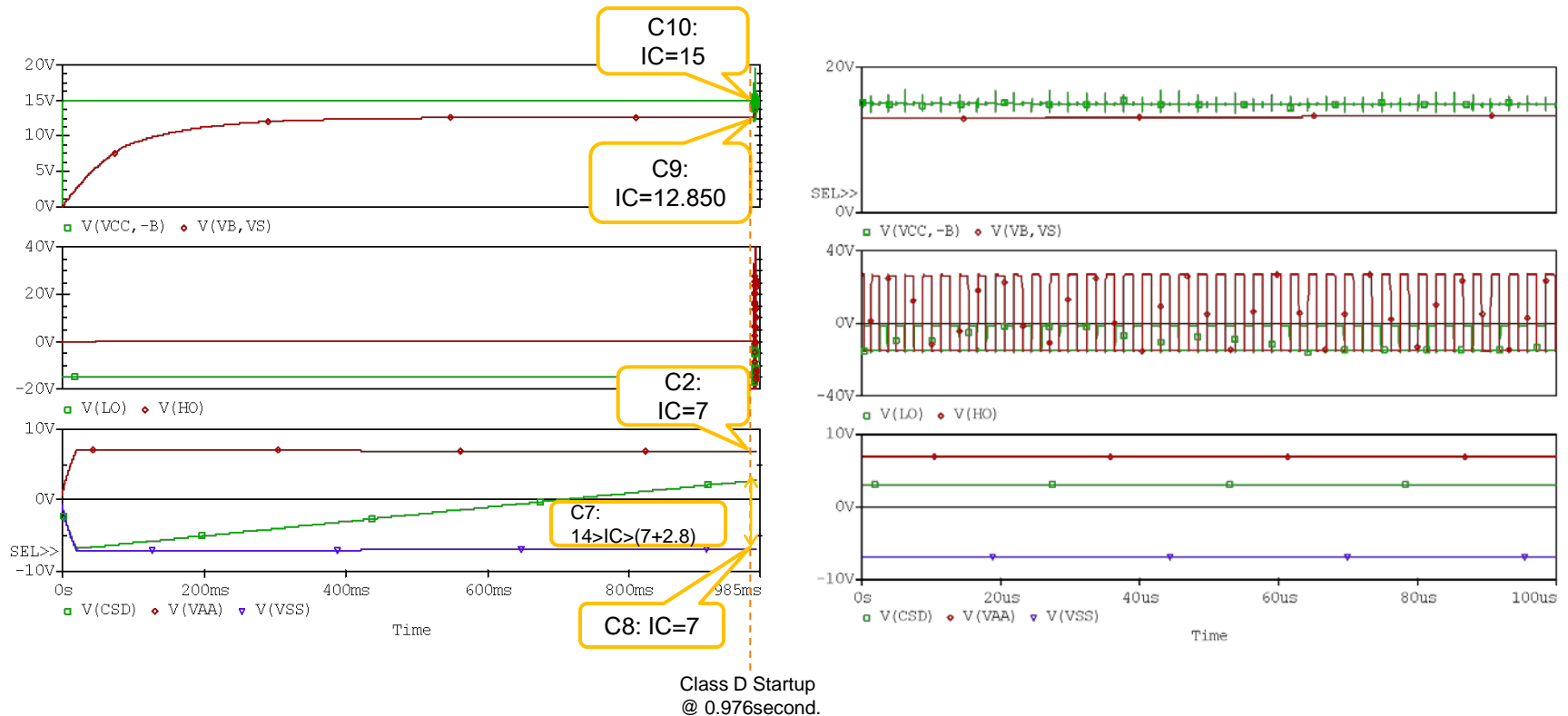
## 2. How the initial condition are set?

- Initial conditions are the startup voltage at each capacitor.
- Change the IC values ,then run the simulation (0-100usec. with maximum time step 10nsec.).




## 3. Example of Using Design Kit

---

- ▶ Estimate design specification.
  - ✓ %Efficiency.
  - ✓ %THD.
  - ✓ Frequency response.
- ▶ Create reference waveforms.
- ▶ Change the design parameters and simulate to see results.
- ▶ Component stress test.
- ▶ Simulate switching losses.
- ▶ Simulate Short-circuit scenarios.


# 4. How to Estimate Design %Efficiency?

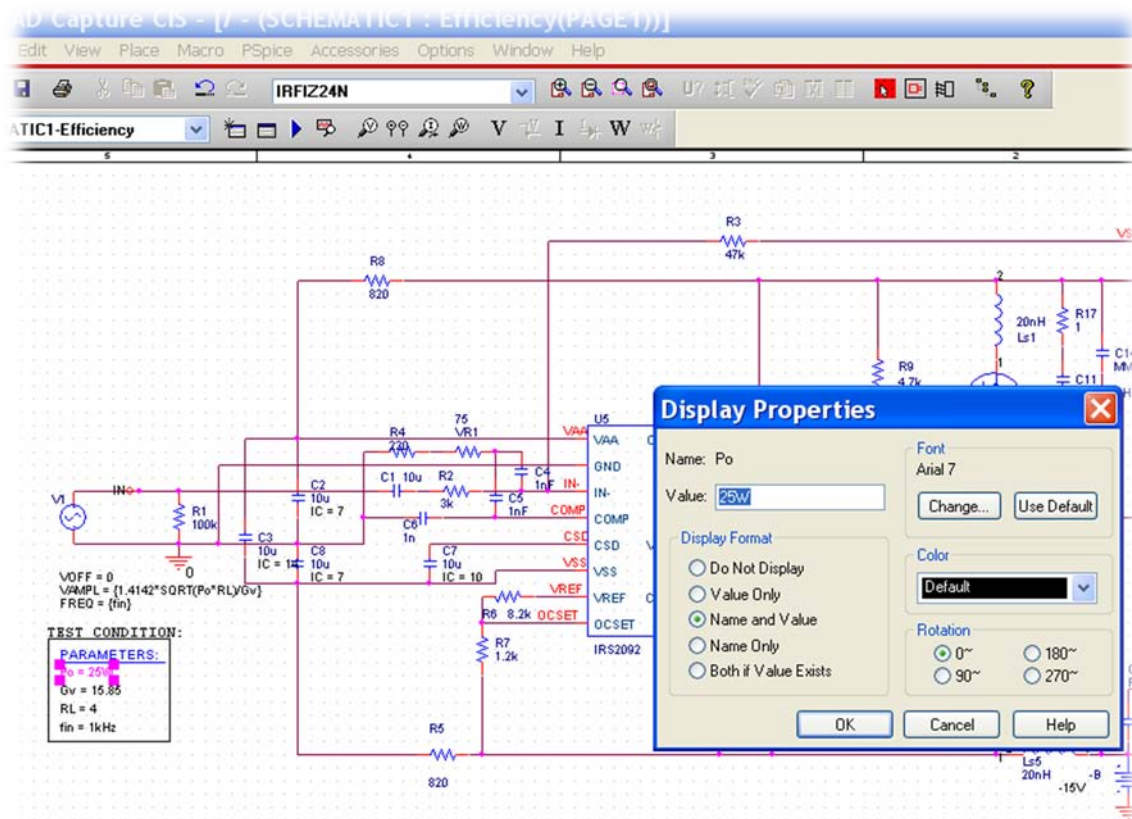1. Open Project: ...¥Simulations¥Efficiency¥Efficiency.opj .
2. Enter test condition parameters:  $P_O=25W$ ,  $G_V=15.85(24dB)$ ,  $R_L=4ohm$ , and  $f_{in}=1kHz$ .
3. Run the simulation from 1 to 3 ms. (about  $3\times 1kHz$  output cycles )



# 4. How to Estimate Design %Efficiency?

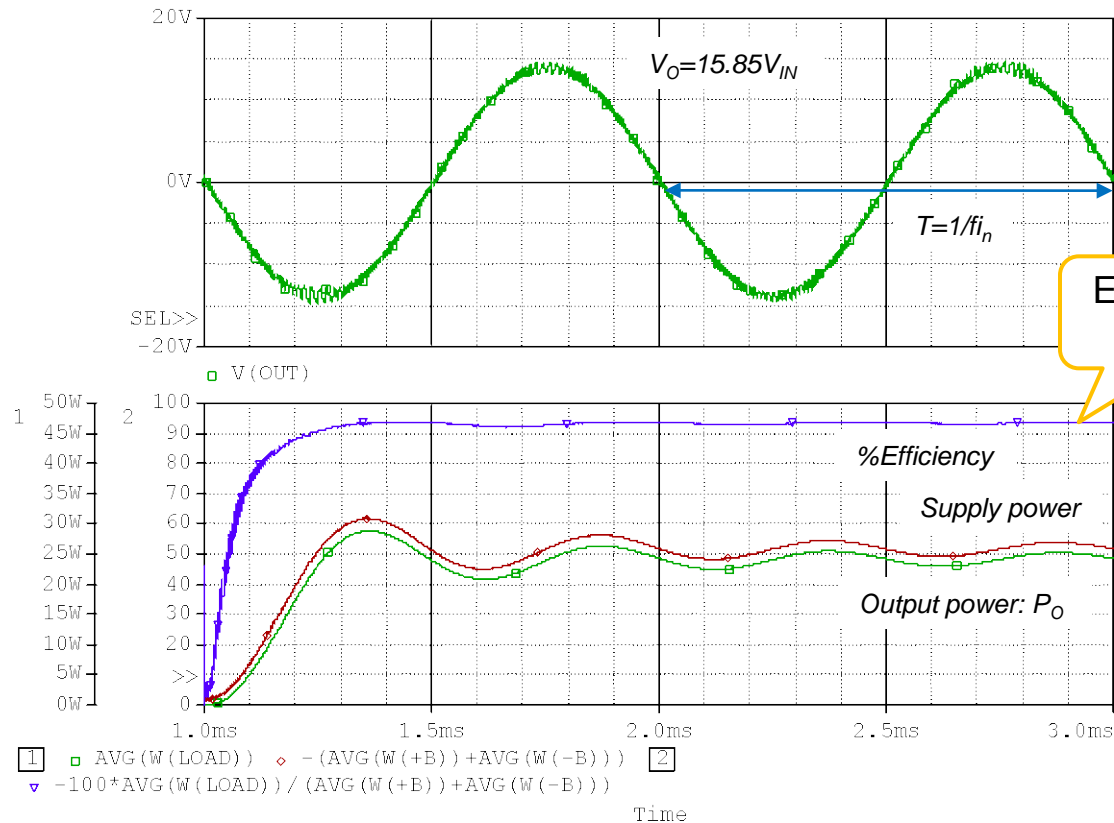4. Add traces: “AVG(W(LOAD))” for PO[W],  
“- (AVG(W(+B)) +AVG(W(-B)))” for Supply power [W], and  
“-100\*AVG(W(LOAD)) / (AVG(W(+B)) +AVG(W(-B)))” for %Efficiency




Efficiency ≈  
93%




# 5. How to Estimate Output THD?

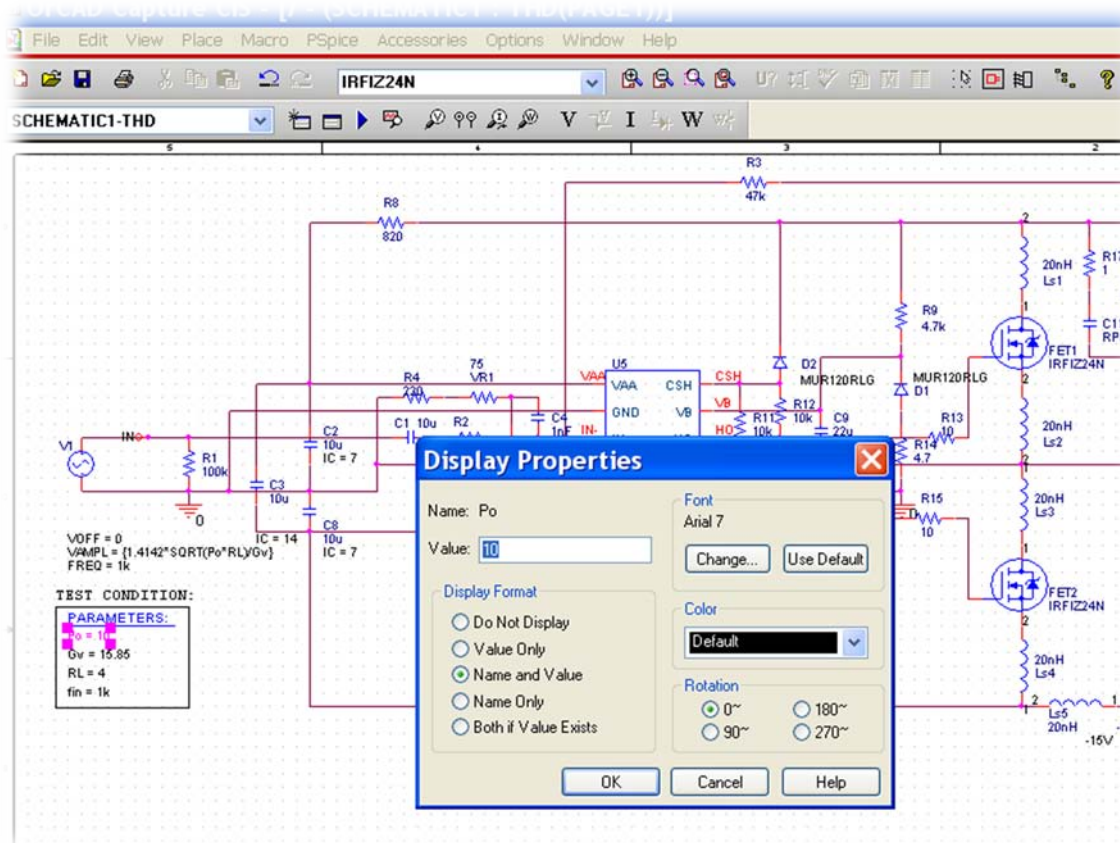1. Open Project: ...¥Simulations¥THD¥THD.opj .
2. Enter test condition parameters:  $P_O=10W$ ,  $G_V=15.85(24dB)$ ,  $R_L=4ohm$ , and  $f_{in}=1kHz$ .



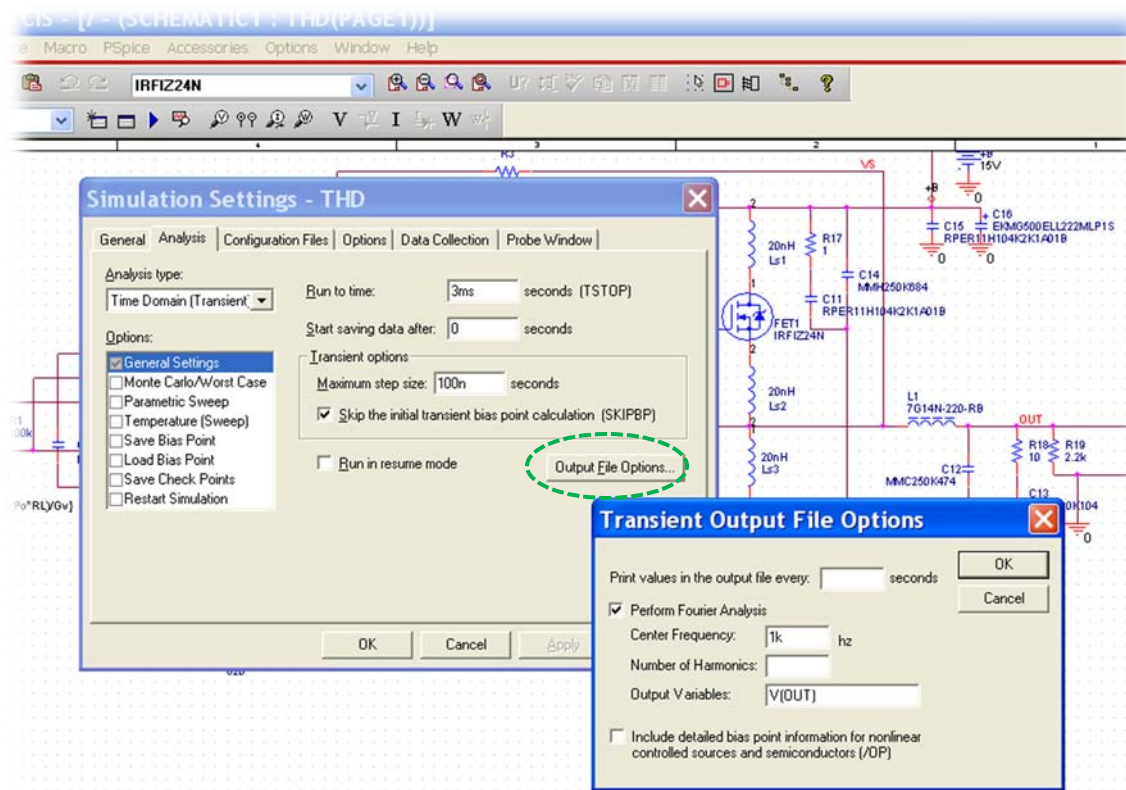
# 5. How to Estimate Output THD?

- THD is calculated by checking the box “Perform Fourier Analysis” in the Output File Options setting. Center Frequency is 1kHz same as  $f_{in}$  and “V(OUT)” is the Output Variable(s).



# 5. How to Estimate Output THD?

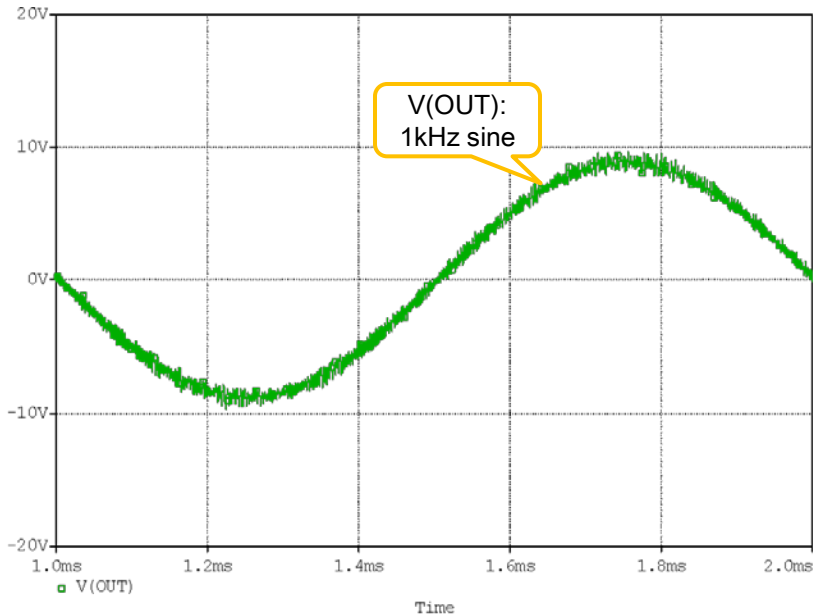4. Run the simulation 0 to 3ms. (maximum time step 100ns. ).
5. View Output File to see the simulated result THD(%)




HARMONIC NO	FREQUENCY (HZ)	FOURIER COMPONENT	NORMALIZED COMPONENT	PHASE (DEG)	NORMALIZED PHASE
1	1.00E+03	8.81E+00	1.00E+00	1.79E+02	0.00E+00
2	2.00E+03	4.62E-04	5.25E-05	4.18E+01	-3.15E+02
3	3.00E+03	2.78E-04	3.16E-05	8.49E+01	-4.51E+02
4	4.00E+03	3.23E-04	3.67E-05	6.91E+01	-6.45E+02
5	5.00E+03	3.73E-04	4.23E-05	8.66E+01	-8.06E+02
6	6.00E+03	6.69E-04	7.60E-05	6.10E+01	-1.01E+03
7	7.00E+03	2.85E-04	3.24E-05	8.09E+01	-1.17E+03
8	8.00E+03	4.32E-04	4.91E-05	7.17E+01	-1.36E+03
9	9.00E+03	5.95E-04	6.76E-05	2.70E+01	-1.58E+03

TOTAL HARMONIC DISTORTION = 1.438206E-02 PERCENT

※ Please note that the simulated result is only an estimate of %THD and the value is influenced by maximum step size.


# 6. How to Estimate Frequency Response?

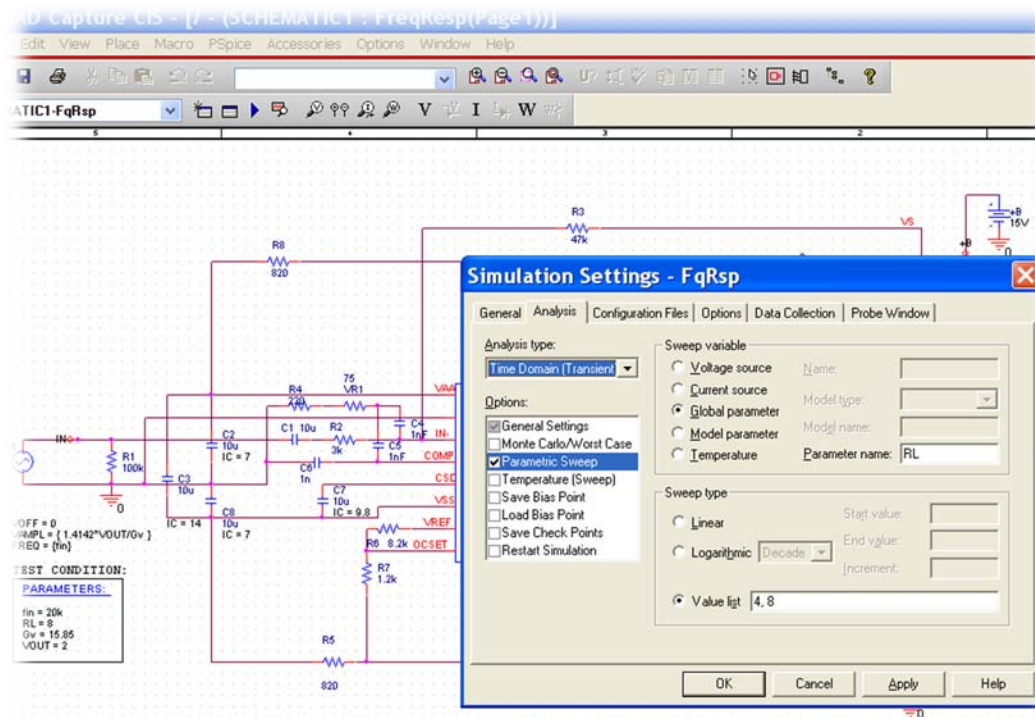1. Open Project: ...¥Simulations¥FrqRsp¥FreqResp.opj.
2. Enter test condition parameters:  $V_{OUT}=2V$ ,  $G_V=15.85(24dB)$ ,  $R_L=4/8$  ohm, and  $f_{in}=20kHz$ .
3. Run the simulation from 0 to 2 ms. (about  $40 \times 20kHz$  output cycles). Use Parametric Sweep (Global parameter: RL with value = 4 and 8)



# 6. How to Estimate Frequency Response?

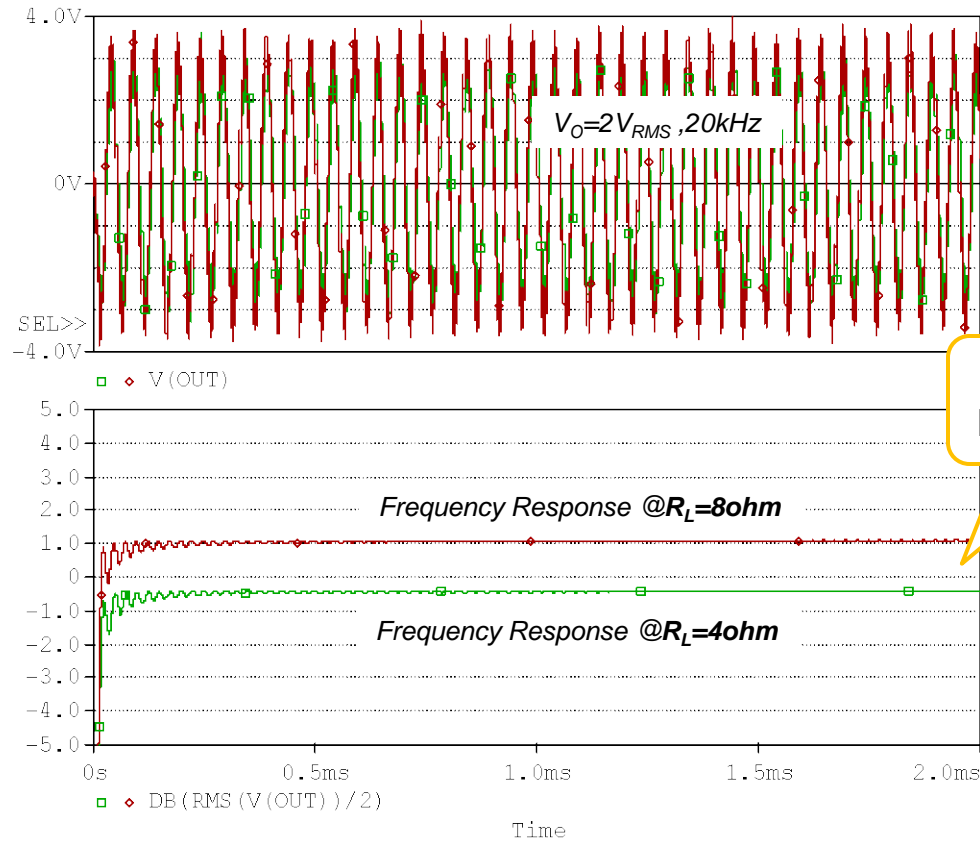4. Add traces: “ $\text{DB}(\text{RMS}(\text{V}(\text{OUT}))/2)$ ” for the frequency response of  $2V_{\text{RMS}}$  output in dB.




Frequency Response in dB





# 7. How to Create Reference Waveforms?

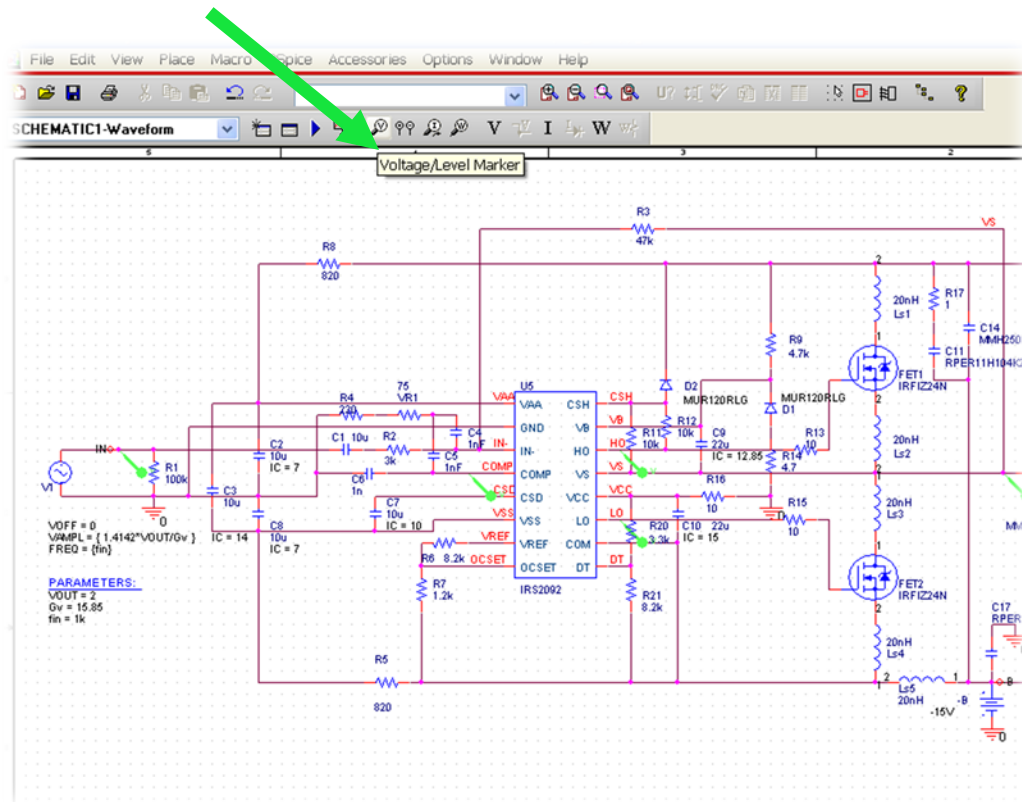1. Open Project: ...¥Simulations¥Waveforms¥Waveform.opj .
2. Enter test condition parameters:  $V_{OUT}=2V$ ,  $G_V=15.85(24dB)$ ,  $R_L=4ohm$ , and  $f_{in}=1kHz$ .
3. Run the simulation from 100n to 3 ms. (about  $3\times 1kHz$  output cycles )
4. Put the Voltage/Level Marker (or Current Marker) to see the waveform(s).





# 7. How to Create Reference Waveforms?

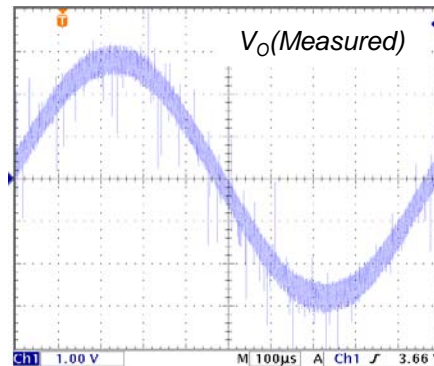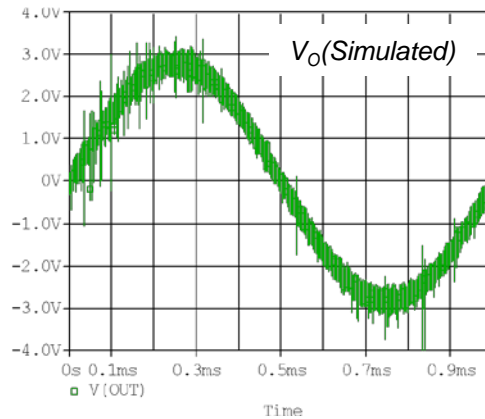4. Set X and Y Data Range in Axis Setting according to oscilloscope scale.
5. Use simulated waveforms as reference to compare with real circuit waveforms.



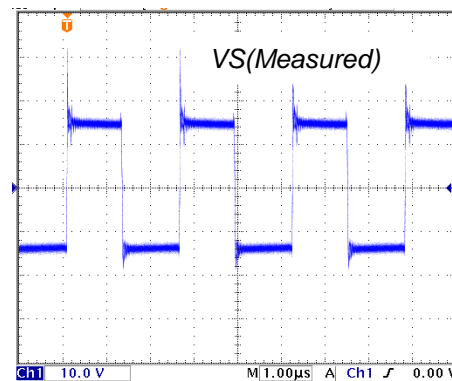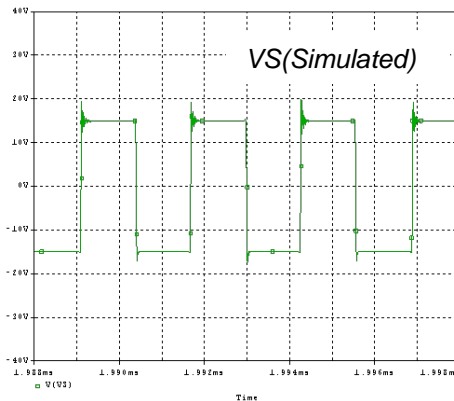
*Result are correlated according to simulated data.*





## 8. Change $R_{IN}$ (R2) and simulate to see change in $G_V$

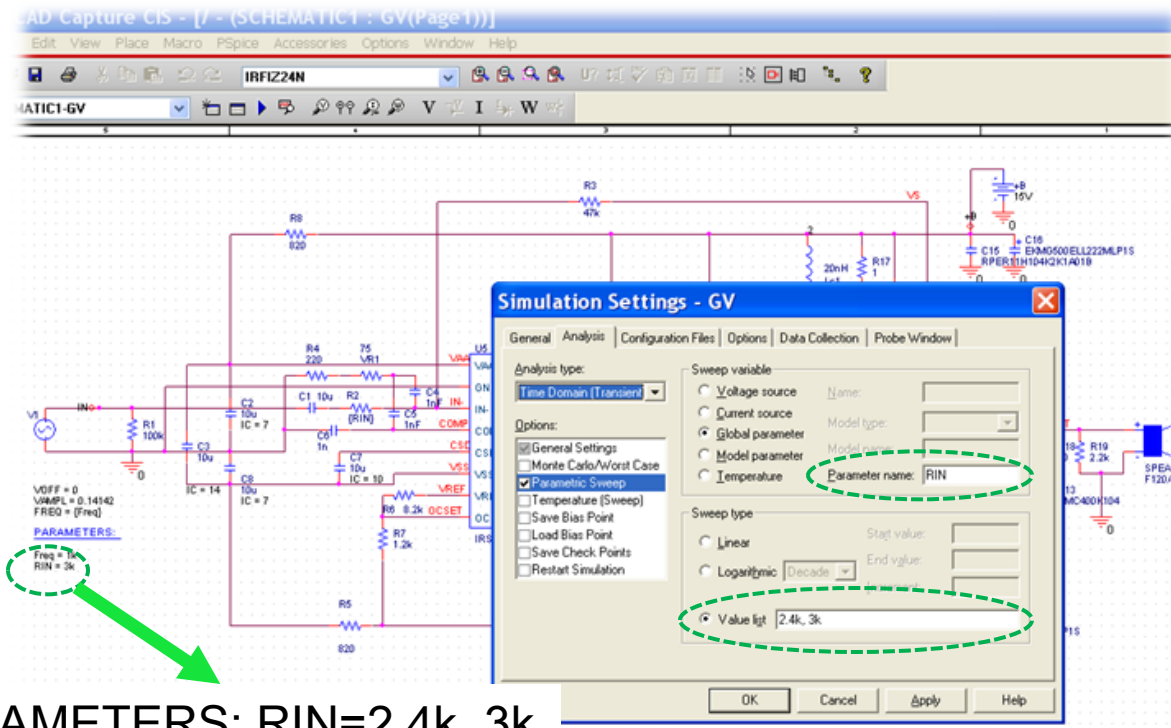
1. Open Project: ...¥Simulations¥Gv¥Gv.opj.
2. Enter test condition parameters:  $V_{IN}=100\text{mV}_{\text{RMS}}$  ( $0.14142\text{V}_{\text{PEAK}}$ ),  $R_{IN}=2.4 / 3 \text{ kohm}$ ,  $R_L=8 \text{ ohm}$  (speaker), and  $f_{in}=1\text{kHz}$ .
3. Run the simulation from 0 to 1 ms. (about  $1 \times 1\text{kHz}$  output cycles ). Use Parametric Sweep (Global parameter: RIN with value = 2.4k and 3k)






## 8. Change $R_{IN}$ (R2) and simulate to see change in $G_V$

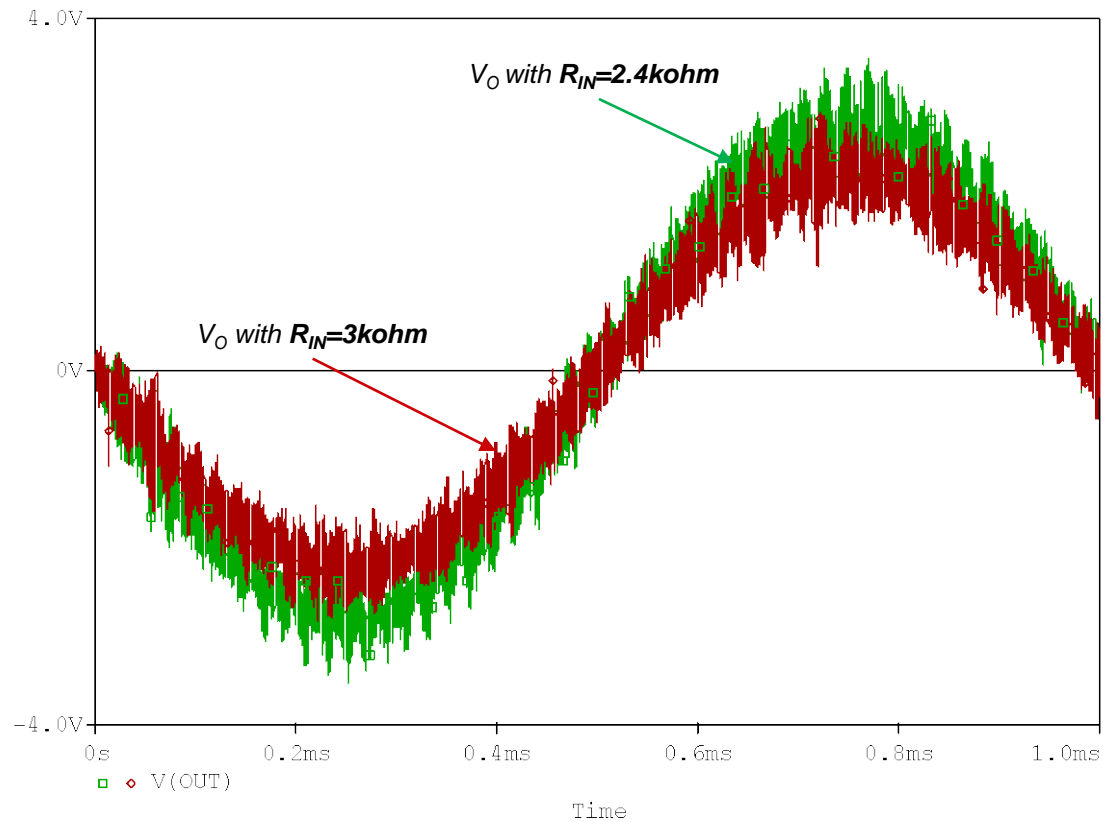4. Simulated result shows  $V_o$  with different gain  $G_V$ .
5. Change parameter:  $R_{IN}$  until you get a satisfied result.




## 9. Use Design Kit to select proper VR value

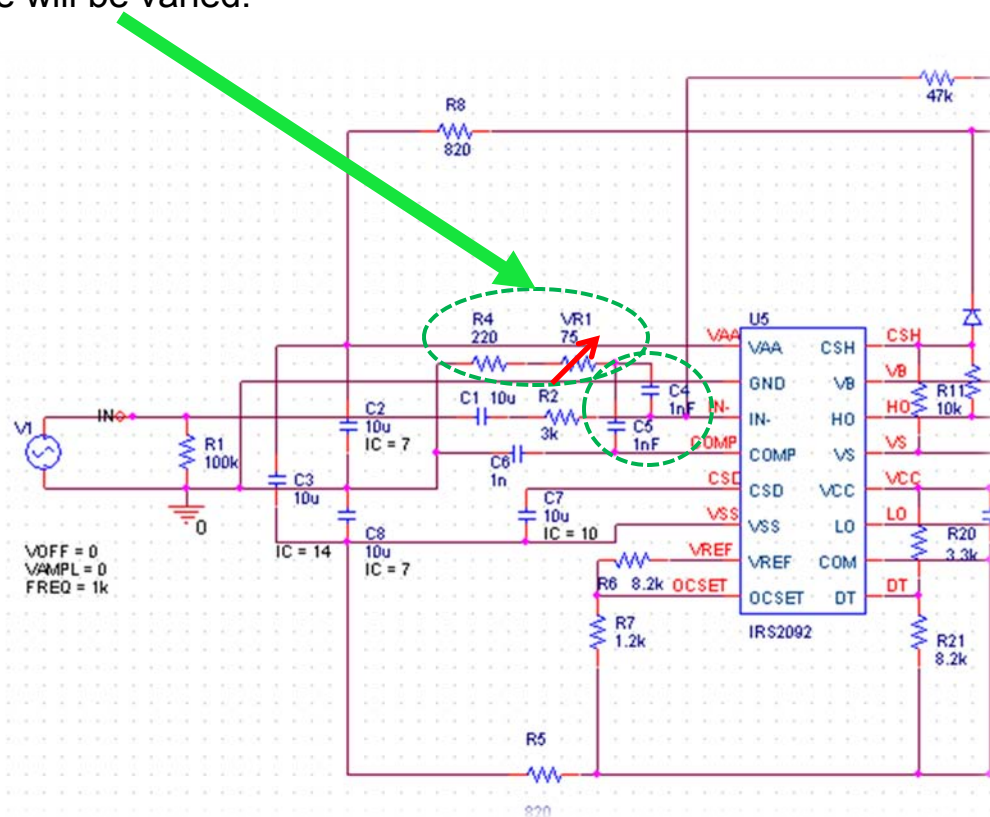1. Open Project: ...¥Simulations¥OSC¥Waveform.opj.
2. Input voltage:  $V_{IN}=0$ ,  $R_L=8$  ohm (speaker).
3.  $f_{OSC}=400\text{kHz}$  is chosen for this design,  $C4=C5=1\text{nF}$ ,  $R4=220$ , a variable resistor: VR1 value will be varied.




## 9. Use Design Kit to select proper VR value

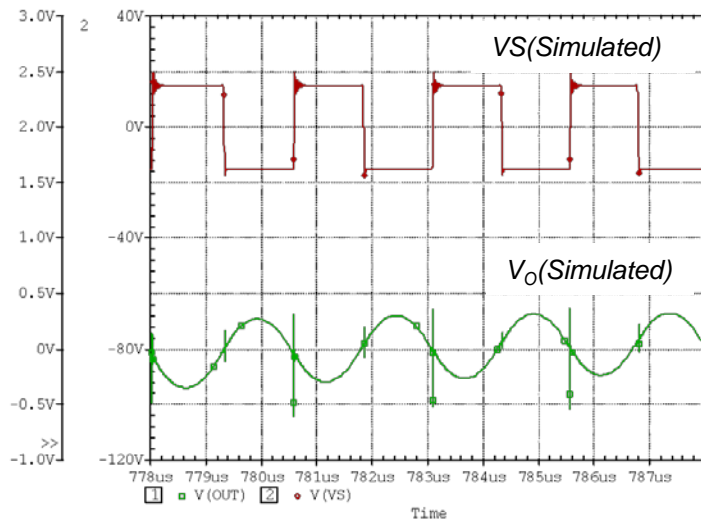4. Change VR1 value until simulation result with  $f_{OSC}=400\text{kHz}$  ( $VR1=75\text{ohm}$ ).
5. Choose VR1 that value more than 100 ohm for the design (this time  $VR1:1\text{k}$  is chosen).




*Simulated waveform with VR1: Value=75*

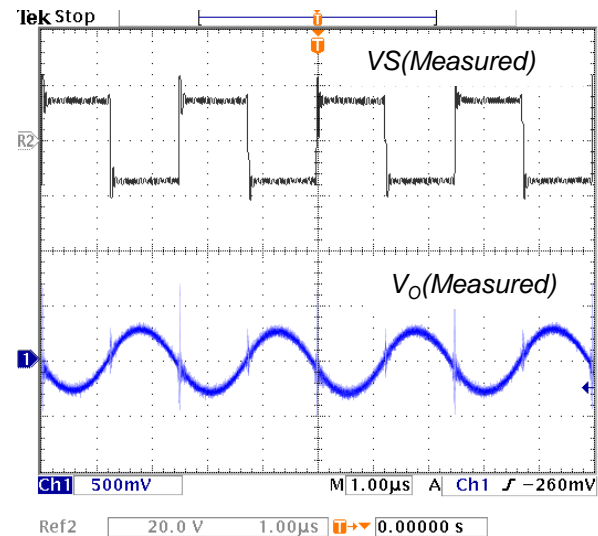

*Measured waveform from real circuit using VR1: 1k*


# 10. Use Design Kit to Predict Spike Voltage vs. Dead-time setting

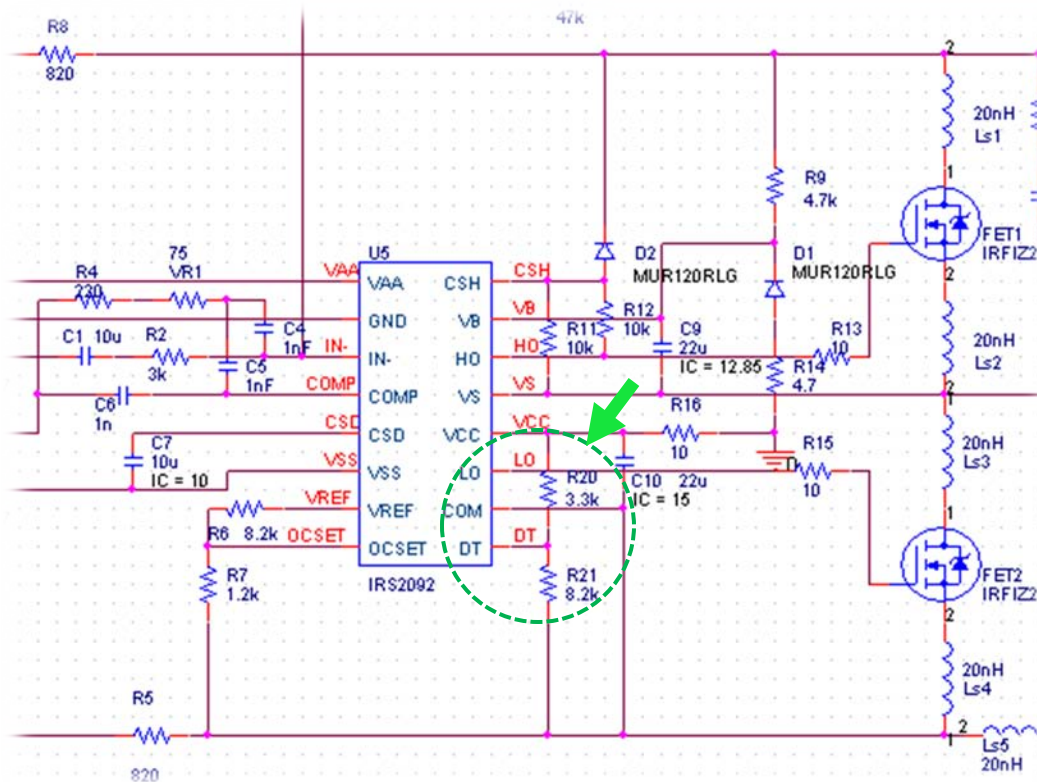1. Open Project: ...¥Simulations¥DT¥Waveform.opj.
2. Input voltage:  $V_{IN}=0$ ,  $R_L=8$  ohm (speaker).
3. Select dead-time setting DT1:  $R_{20}=3.3k / R_{21}=8.2k$ , Simulate and compare result with dead-time setting DT3:  $R_{20}=8.2k / R_{21}=3.3k$




# 10. Use Design Kit to Predict Spike Voltage vs. Dead-time setting

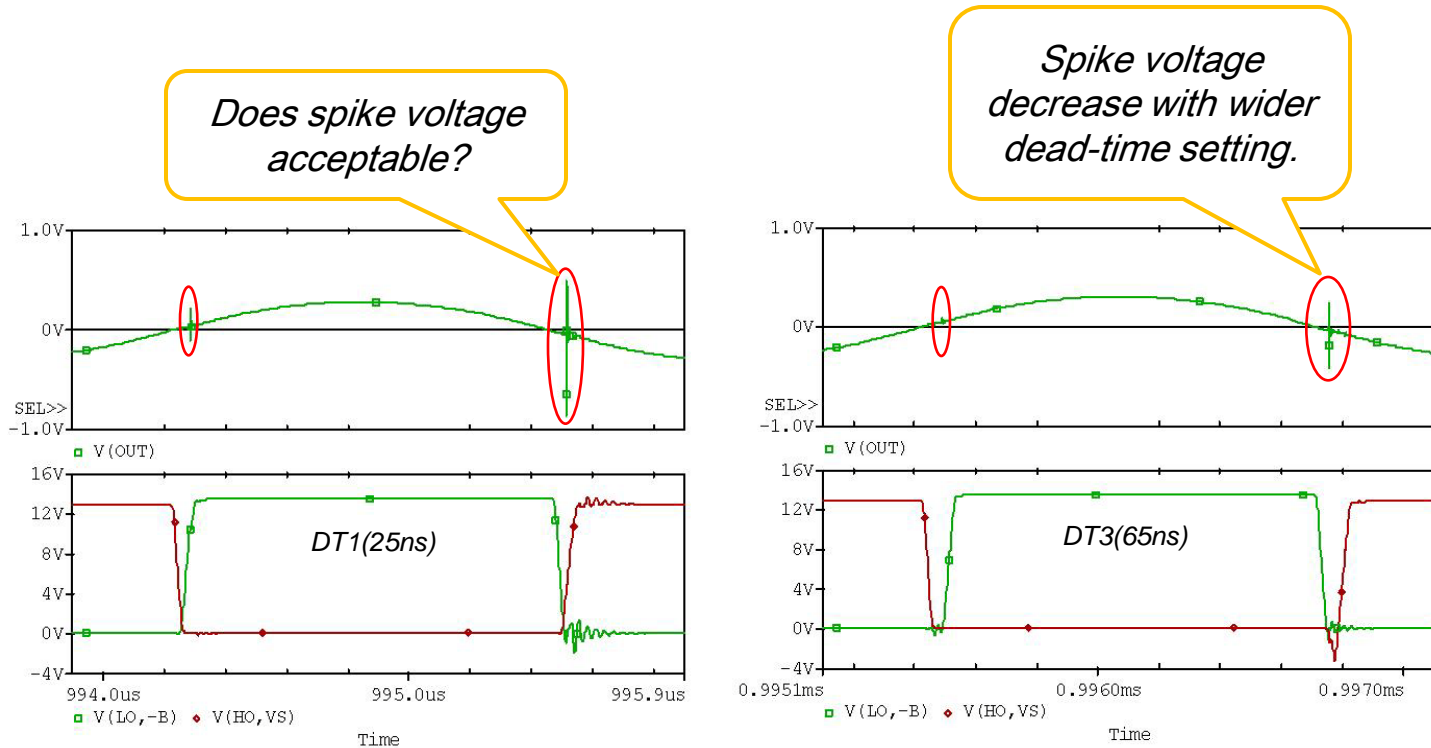4. Compare the results to see that spike voltages are acceptable or not for each dead-time setting.



# 11. Use Design Kit to Develop the Design (Change the FETs)

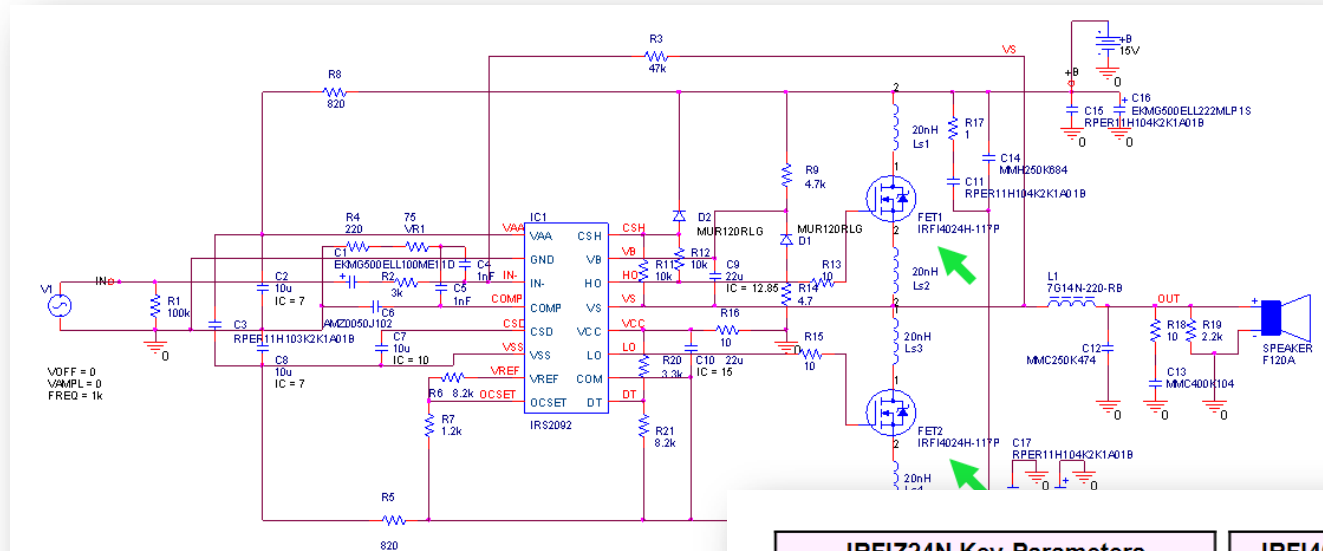1. Use the simulation files for the performance evaluation (ex. Efficiency, THD, and Waveform).
2. Replace MOSFET model IRFIZ24N with IRFI4024H-117P.
3. Run simulation file to check the design performance.




IRFIZ24N Key Parameters			IRFI4024H-117P Key Parameters		
$V_{DS}$	55	V	$V_{DS}$	55	V
$I_D$	14	A	$I_D$	11	A
$R_{DS(ON)}$ typ. @ 10V	70	m $\Omega$	$R_{DS(ON)}$ typ. @ 10V	48	m $\Omega$
$Q_g$ typ.	13.4	nC	$Q_g$ typ.	8.9	nC
$t_{ON}$ typ.	38.9	ns	$t_{ON}$ typ.	7.9	ns
$t_{OFF}$ typ.	46	ns	$t_{OFF}$ typ.	16.4	ns
$Q_{JT}$ typ.	120	nC	$Q_{JT}$ typ.	11	nC



# 11. Use Design Kit to Develop the Design (Change the FETs)

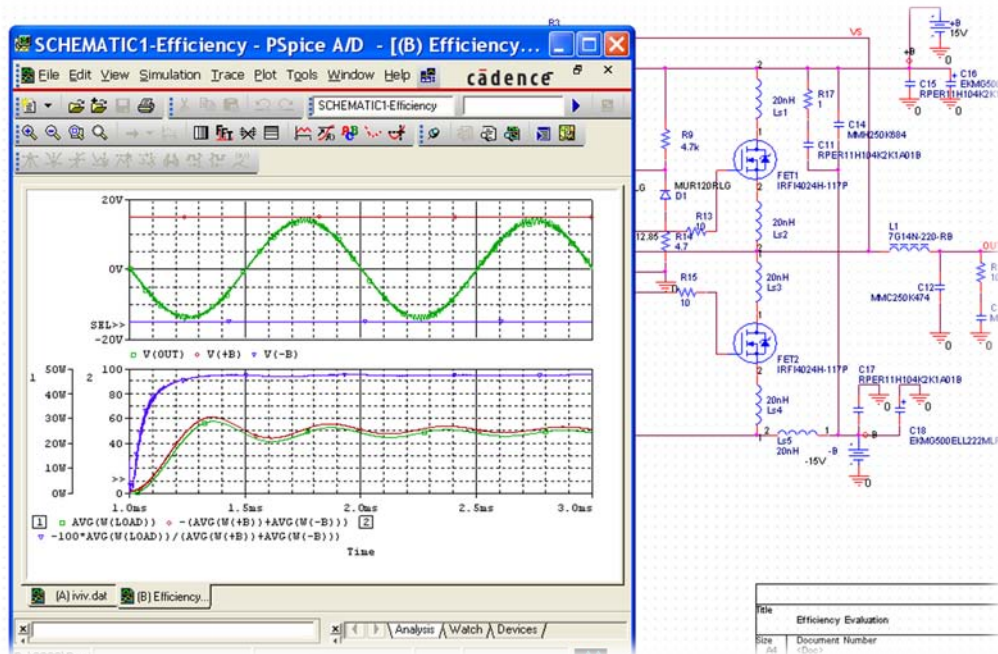3. Compare the performance of the circuit with difference FET.




%Efficiency is improved

	IRFIZ24N	IRFI4024H-117P
Efficiency (@ 25W, 4Ω)	93.505%	94.578%
Distortion (@ 1kHz, 4Ω, 10W)	0.0144 %THD	0.0201 %THD
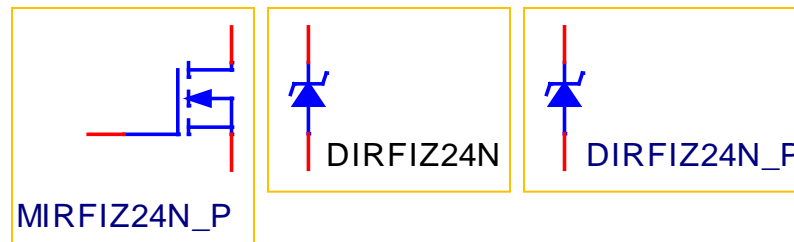
## 12. MOSFET Professional Model

- ▶ Library and symbol files are in folder ...¥Parts¥IRFIZ24N¥IRFIZ24N(PRO)
- ▶ IRFIZ24N Professional Model consists of MOSFET Professional (MIRFIZ24N\_P), body diode DIRFIZ24N, and body diode Professional DIRFIZ24N\_P.
- ▶ Use MOSFET Professional model to improve an accuracy Gate Charge characteristics  $Q_g$  of FET model.
- ▶ Use body diode Professional model to improve an accuracy Reverse Recovery Time characteristic  $T_{RR}$  of FET's body diode model.



※ Using Professional model will slow down the simulation time and might cause some convergence error.