

NJM2377-Boost DC/DC Converter

Table of component models used in the Design Kit

Code	Classification	Part No.	Manufacturer	SPEC
U1	PWM-IC	NJM2377	New Japan Radio Co., Ltd.	(2.7 to 18V, 50mA)
Q1	NPN-BJT	2SD2623	Panasonic	20V / 0.5A
D1	Schottky Barrier Diode (SBD)	HRU0302A	RENESAS	20V / 0.3A

Simulation files are stored in folders, as shown in list below.

Simulations	Folder name
1. NJM2377 – Soft Start Time Setting (Simulation).....	\IC-Config\SS
2. NJM2377 – Oscillation Frequency Setting.....	\IC-Config\OSC
3. Error Amp Feed Back Loop (Transient).....	\IC-Config\FB
4. Start-Up Transient Simulation (0~90ms.).....	Transient
5. Efficiency and Losses.....	Efficiency
6. Step-Load Response.....	Step-load
7. Voltage and Current Simulation.....	Stress
8. Switching Waveforms.....	Waveforms

* Please copy the folder named “Simulation” to your PC. Library files (.lib) are already added.

Design document: **NJM2377-Boost DC/DC Converter**

Contents

1. NJM2377 – Boost DC/DC Converter Circuit
2. PWM – Boost DC/DC Converter Basic Operation and Design
 - 2.1 Boost DC/DC Converter – V_{OUT}
 - 2.2 Boost DC/DC Converter – t_{ON} / t_{OFF}
 - 2.3 Boost DC/DC Converter – Inductor Selection
 - 2.4 Boost DC/DC Converter – Inductor Peak Current
 - 2.5 Boost DC/DC Converter – C_{OUT} Selection
3. NJM2377 – Application Circuit Configuration
 - 3.1 NJM2377 – Soft Start Time Setting
 - 3.2 NJM2377 – Oscillation Frequency Setting
 - 3.3 Error Amp Feed Back Loop Setting
4. Performance Characteristics
 - 4.1 Output Start-Up Voltage and Current
 - 4.2 Output Ripple Voltage
 - 4.3 Efficiency
 - 4.4 Step-Load Response
5. Voltage and Current Simulation Result
6. Losses
 - 6.1 Bipolar Junction Transistor Losses
 - 6.2 Schottky Barrier Diode Losses
7. Waveforms
 - 7.1 Start-Up Sequencing Waveforms
 - 7.2 Switching Waveform at Load 50mA
 - 7.3 Switching Waveform at Load 10mA

[Simulations index](#)

[Simulations Settings](#)