


Design Kit

Quasi-Resonant Switching Power Supply using FA5541


Contents

	Slide #
1. Quasi-Resonant Switching Power Supply 19V/5A.....	3
1.1 Output voltage.....	4
1.2 Output current.....	5
1.3 Output ripple voltage	6
1.4 Step-load response.....	7
2. Basic operation of switching power supply using FA5541.....	8-11
3. Start-up sequence simulation.	12-15
4. Bridge diode peak current at start-up.....	16-17
5. Transformer.....	18-20
6. Transformer leakage inductance.....	21-22
7. RCD Clamping network.....	23-24
8. Power MOSFET switching device.....	25-27
9. Schottky barrier diode D21 and D22 waveforms.....	28-30
10. Photocoupler.....	31-32
Simulations index.....	33

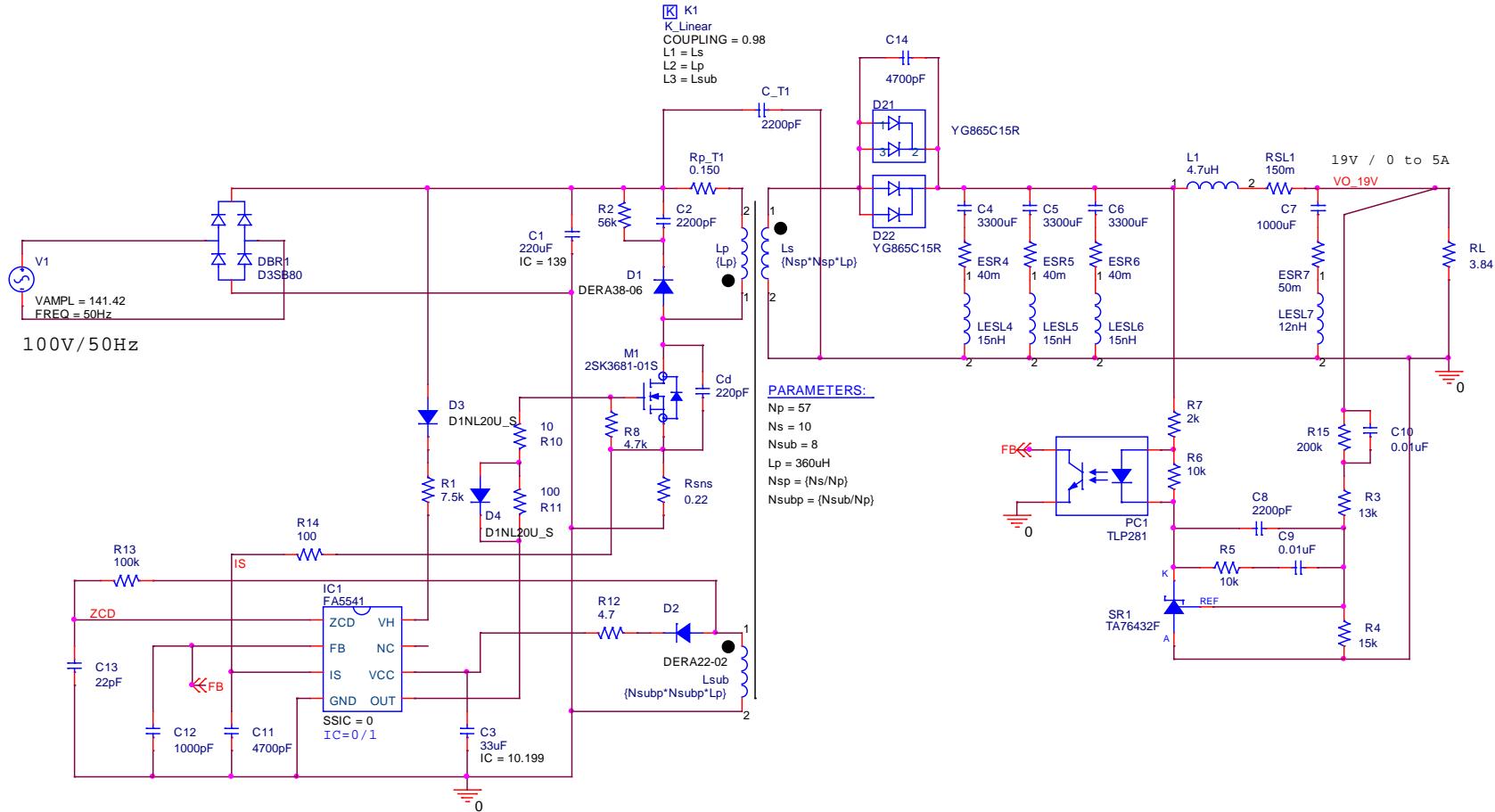1. Quasi-Resonant Switching Power Supply 19V/5A




1.1 Output voltage

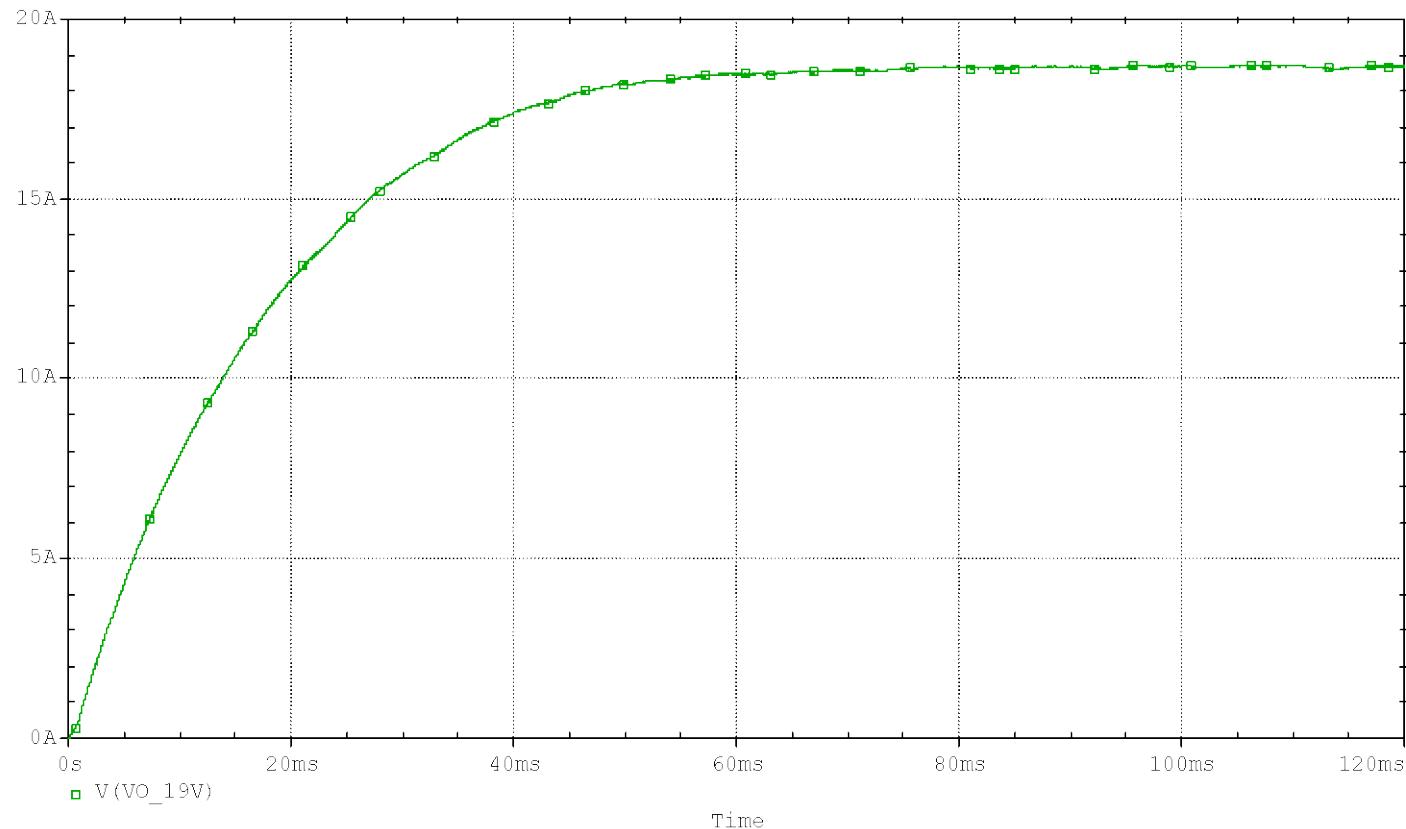


- Simulation result confirming that the output voltage would be 19 Volt at 5-A load. The result also shows that the circuit need 60ms to reach steady state.

1.2 Output current

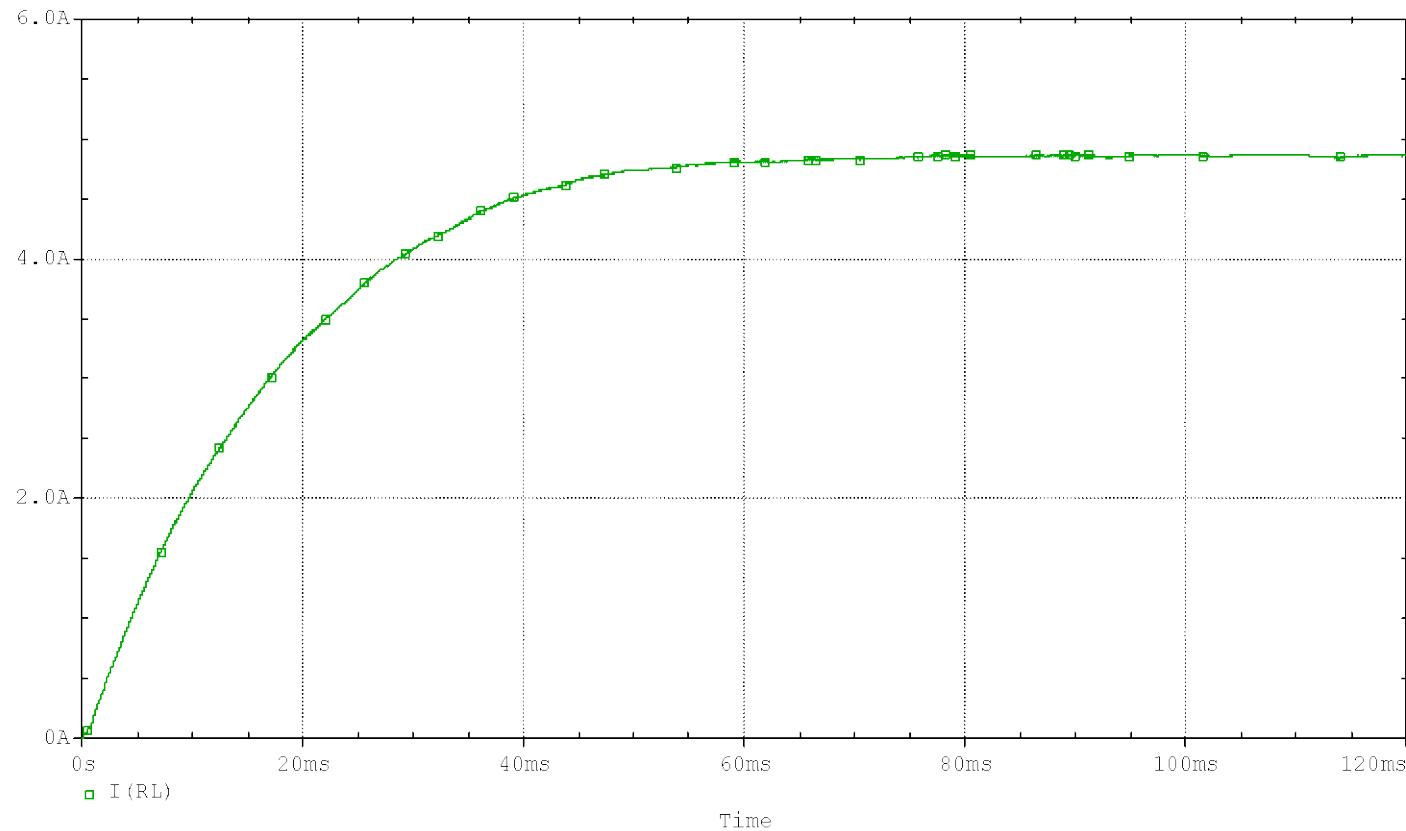


- Simulation result confirming that the output current would be 5 Amp. The result also shows that the circuit need 60ms to reach steady state.

1.3 Output ripple voltage

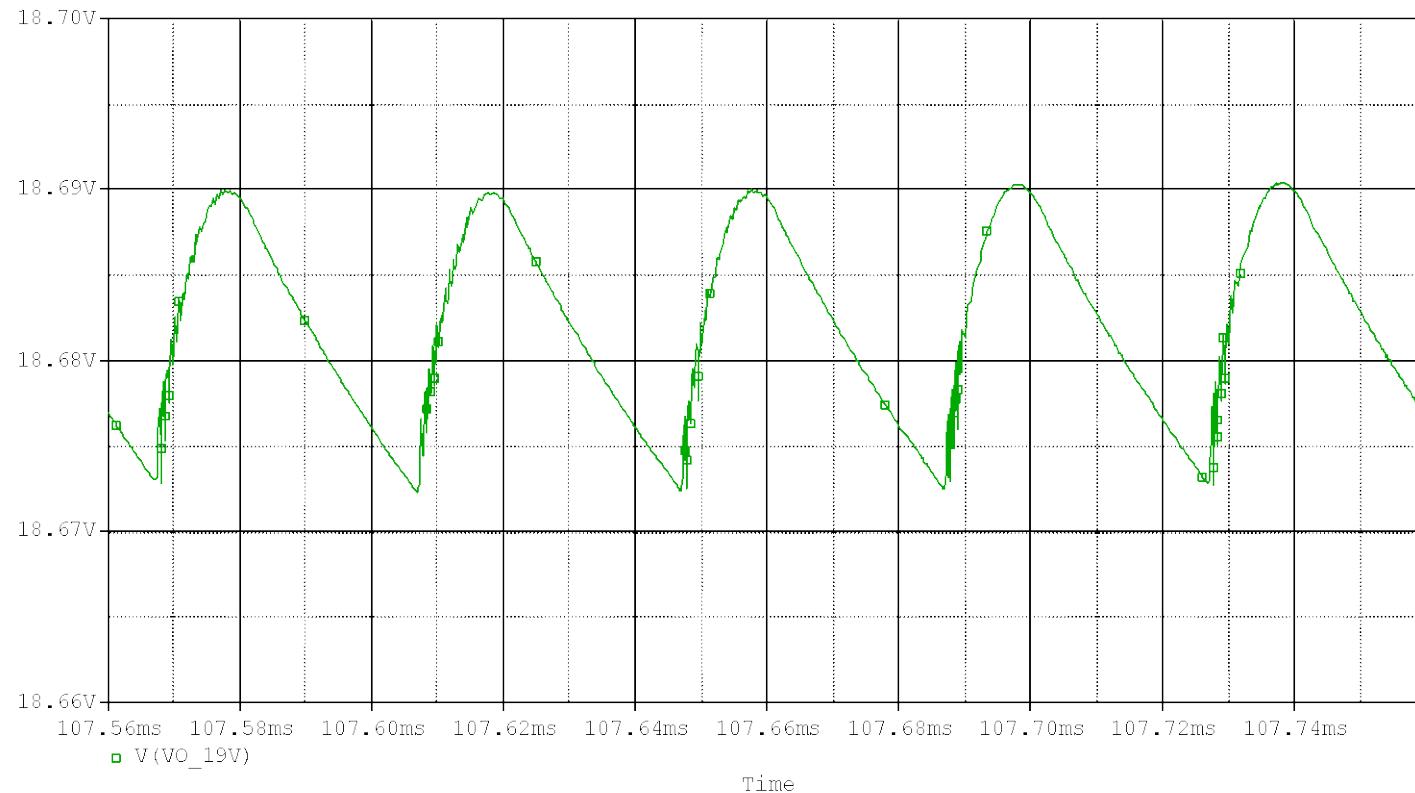


- Simulation results shows the output ripple voltage at maximum current load (approximately 17.5mV_{P-P}).

1.4 Step-load response

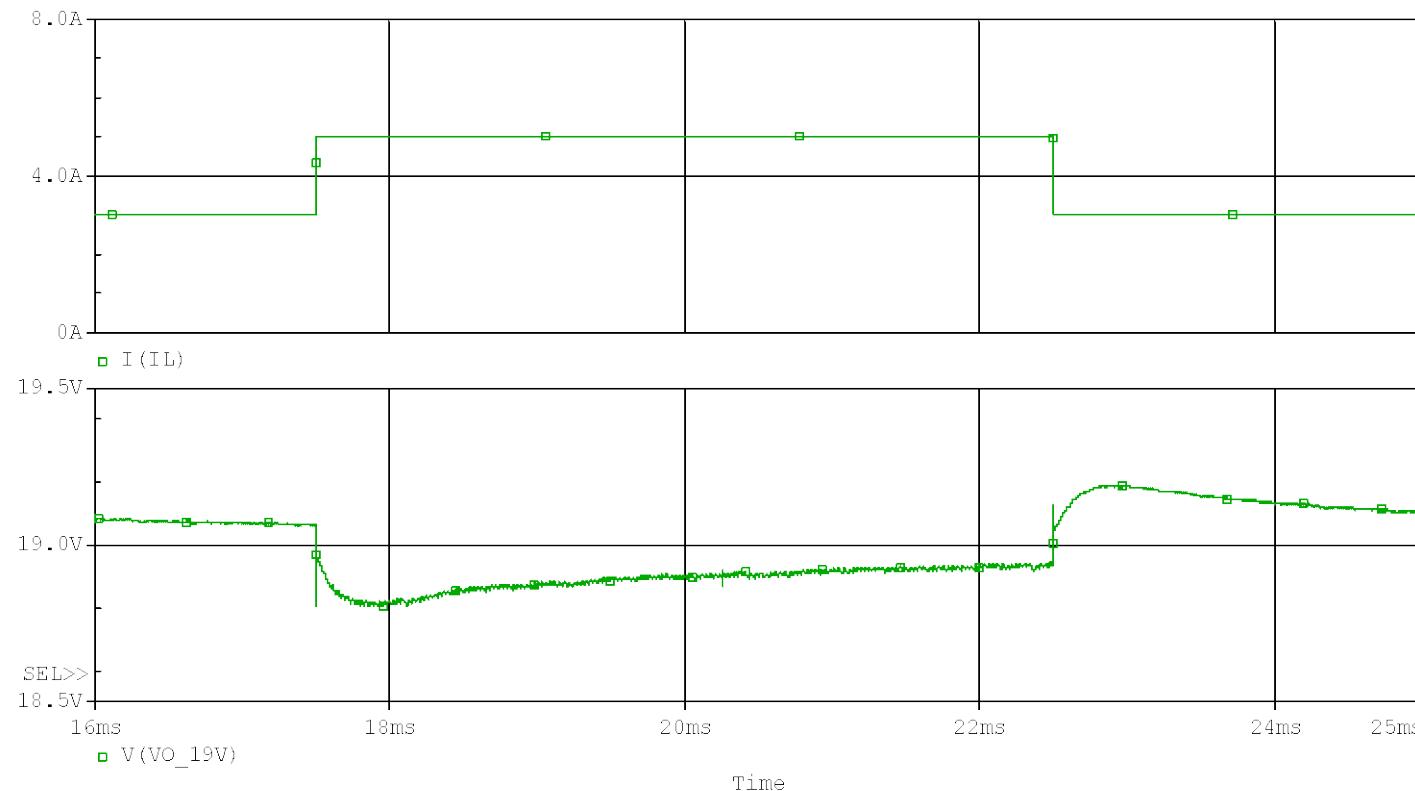


- Simulation results shows waveform of the output voltage responding to stepping current 3/5A.

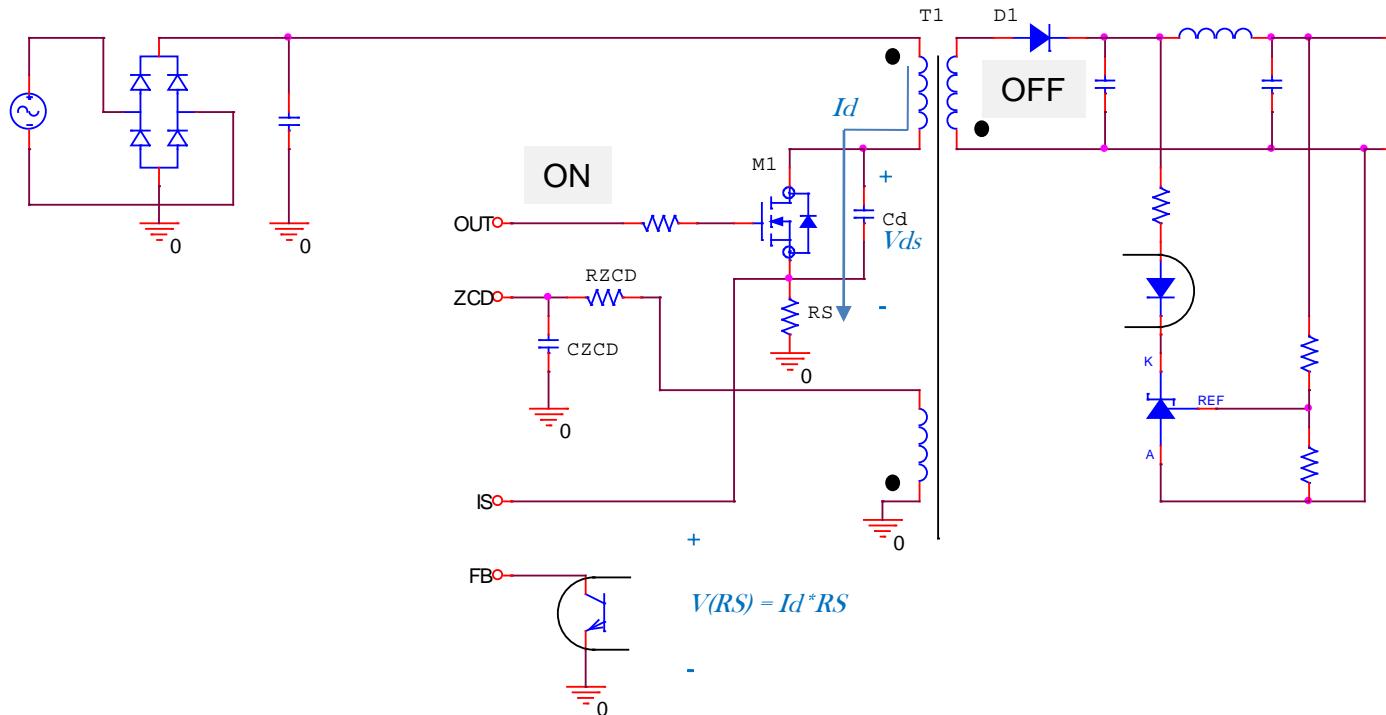2. Basic operation of switching power supply using FA5541




- Power supply using FA5541 is switching using self-excited oscillation.
- When IC turns the MOSFET ON ,drain current Id (primary current of T1) begins to rise from zero.
- $V(IS$ pin) is voltage-converted from the Id current.

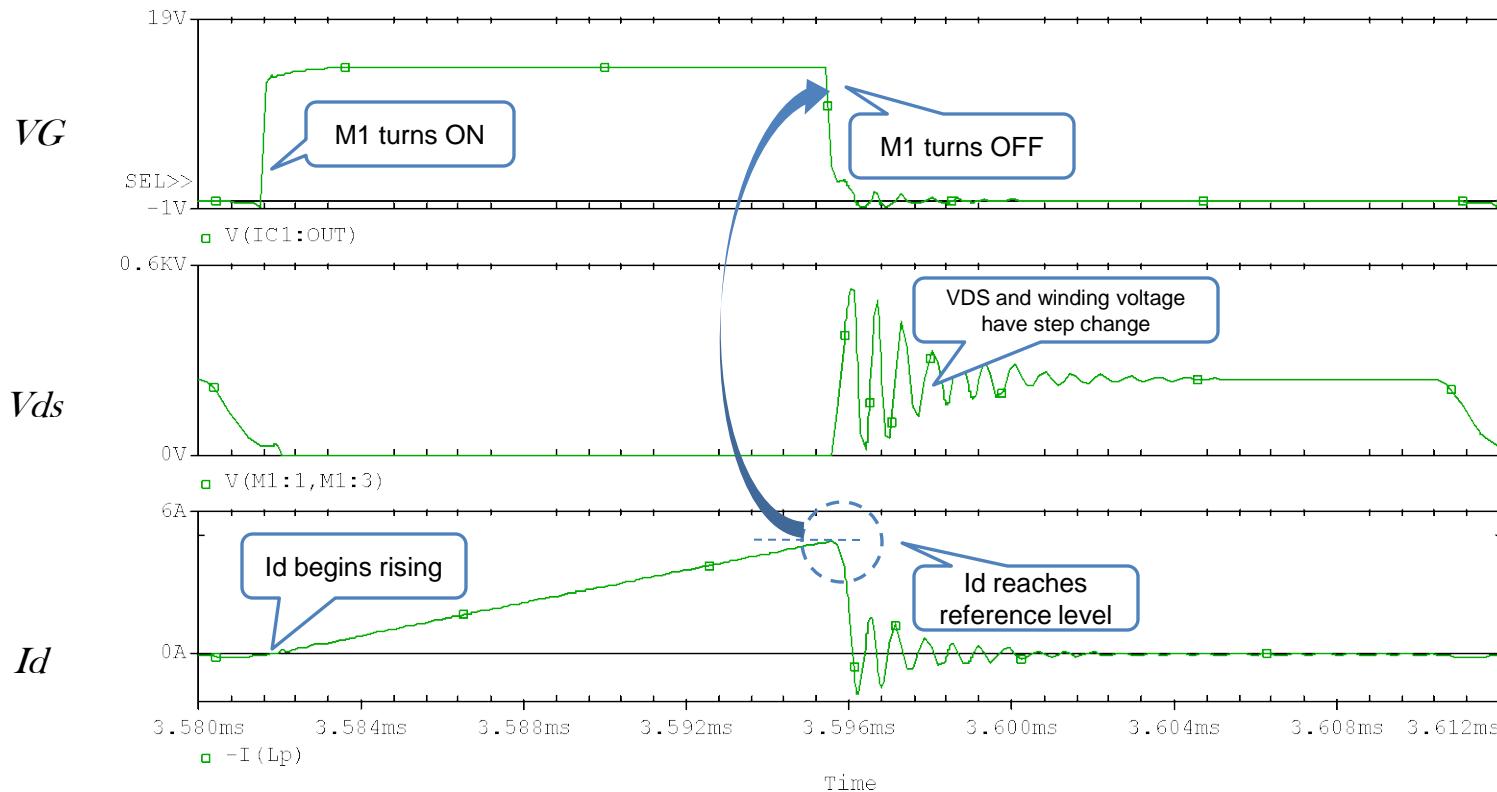2. Basic operation of switching power supply using FA5541




- When I_d reaches the reference level, FA5541 will turn M1 OFF

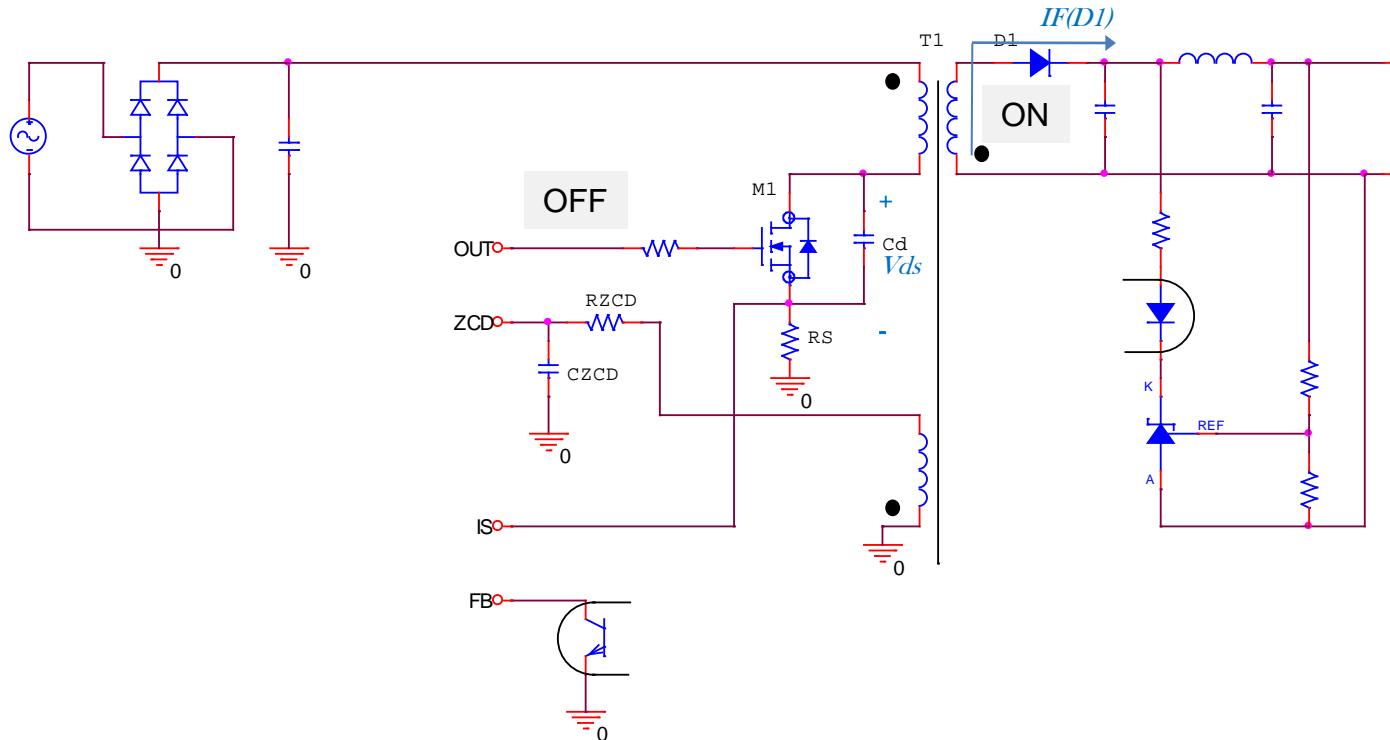2.Basic operation of switching power supply using FA5541




- When M1 turns OFF ,and the winding voltage of the transformers has step change and IF(D1) is provided from the transformer into secondary side.

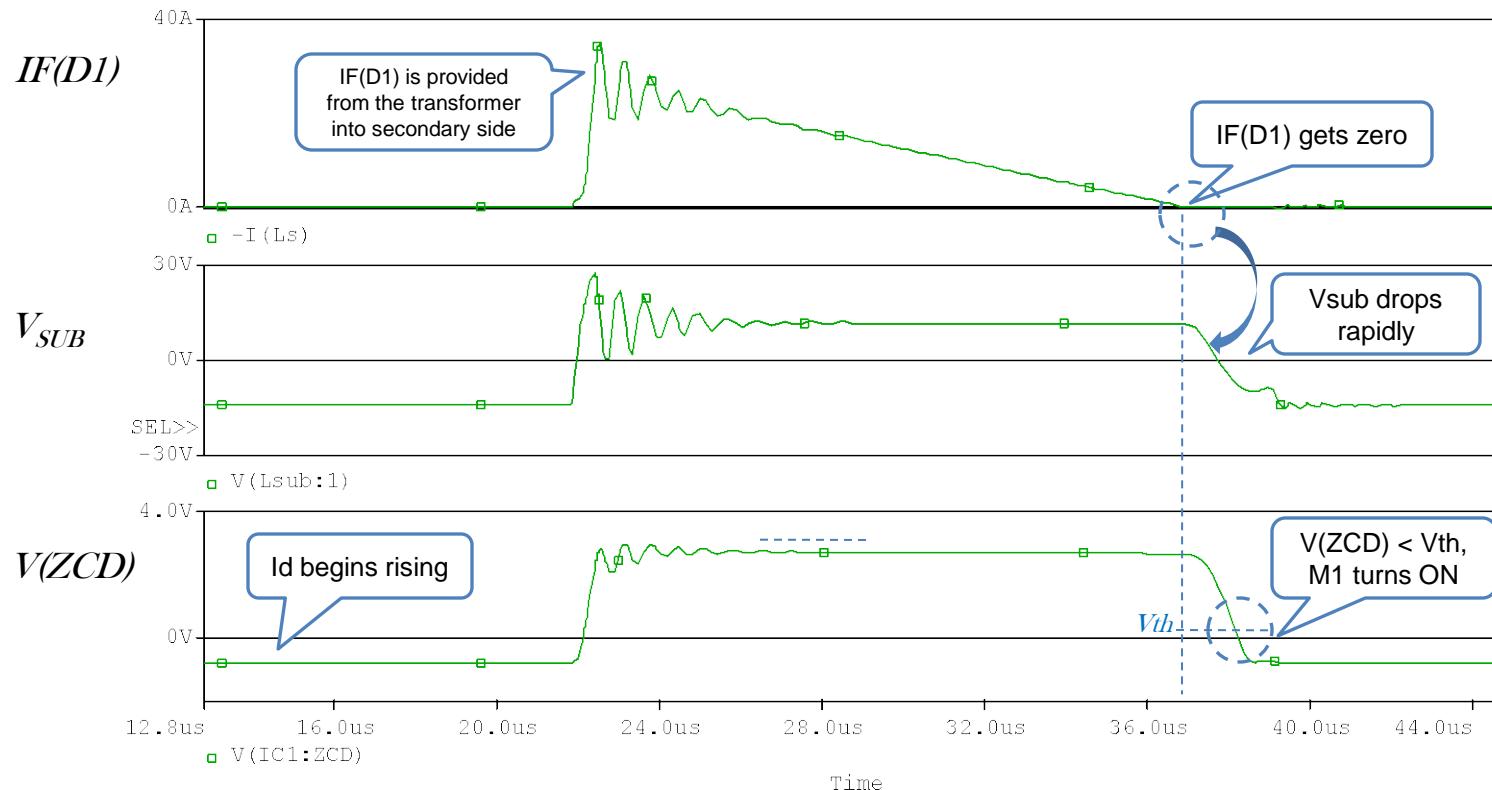2. Basic operation of switching power supply using FA5541




- When IF(D1) gets zero, V_{ds} drops rapidly due to resonance of transformers inductance and C_d . At the same time V_{sub} also drops rapidly.
- When $V(ZCD) < V_{th}$ (of valley detection) ,FA5541 turns M1 ON again

3. Start-up sequence simulation

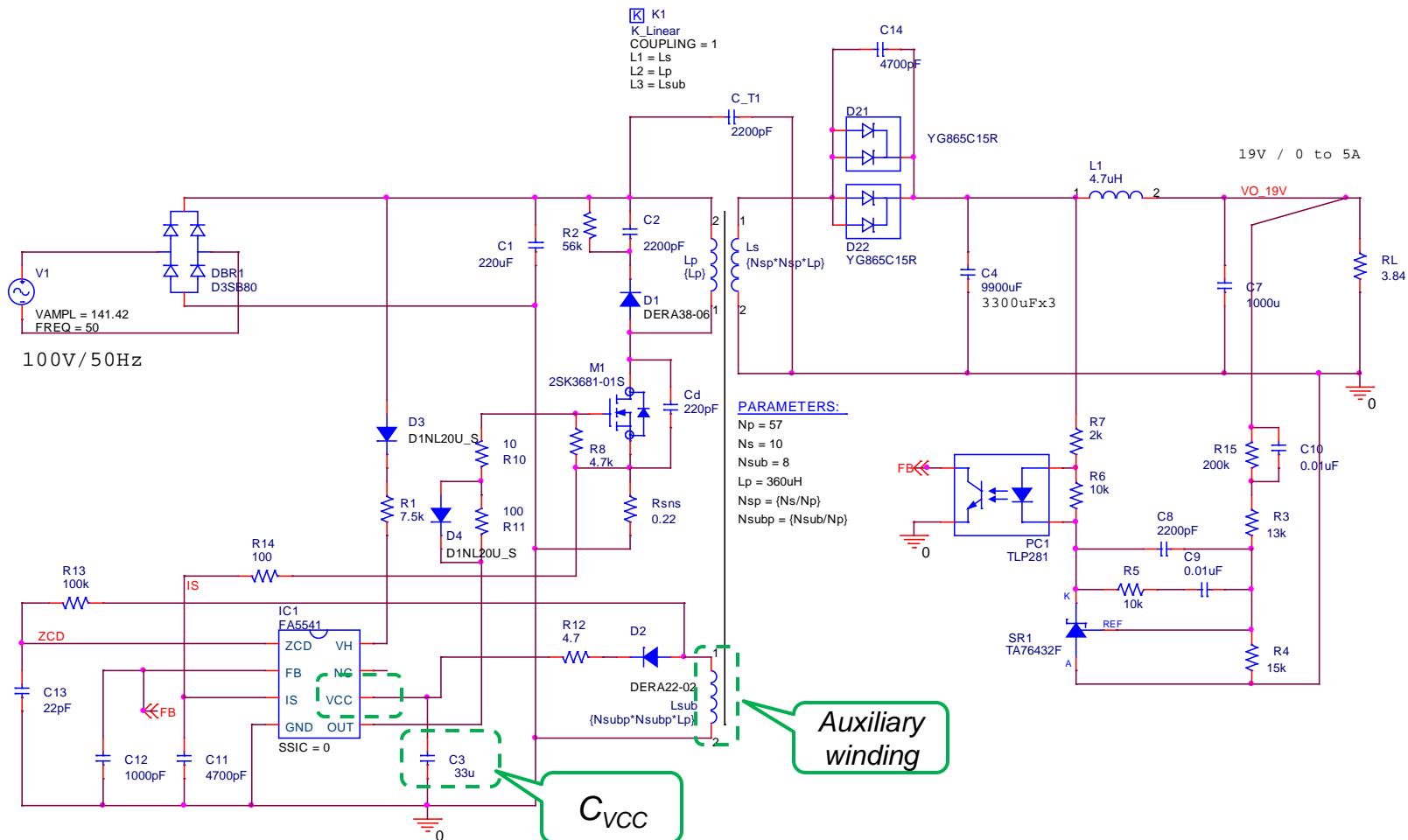

※ No parasitic elements and no initial condition is set


3. Start-up sequence simulation

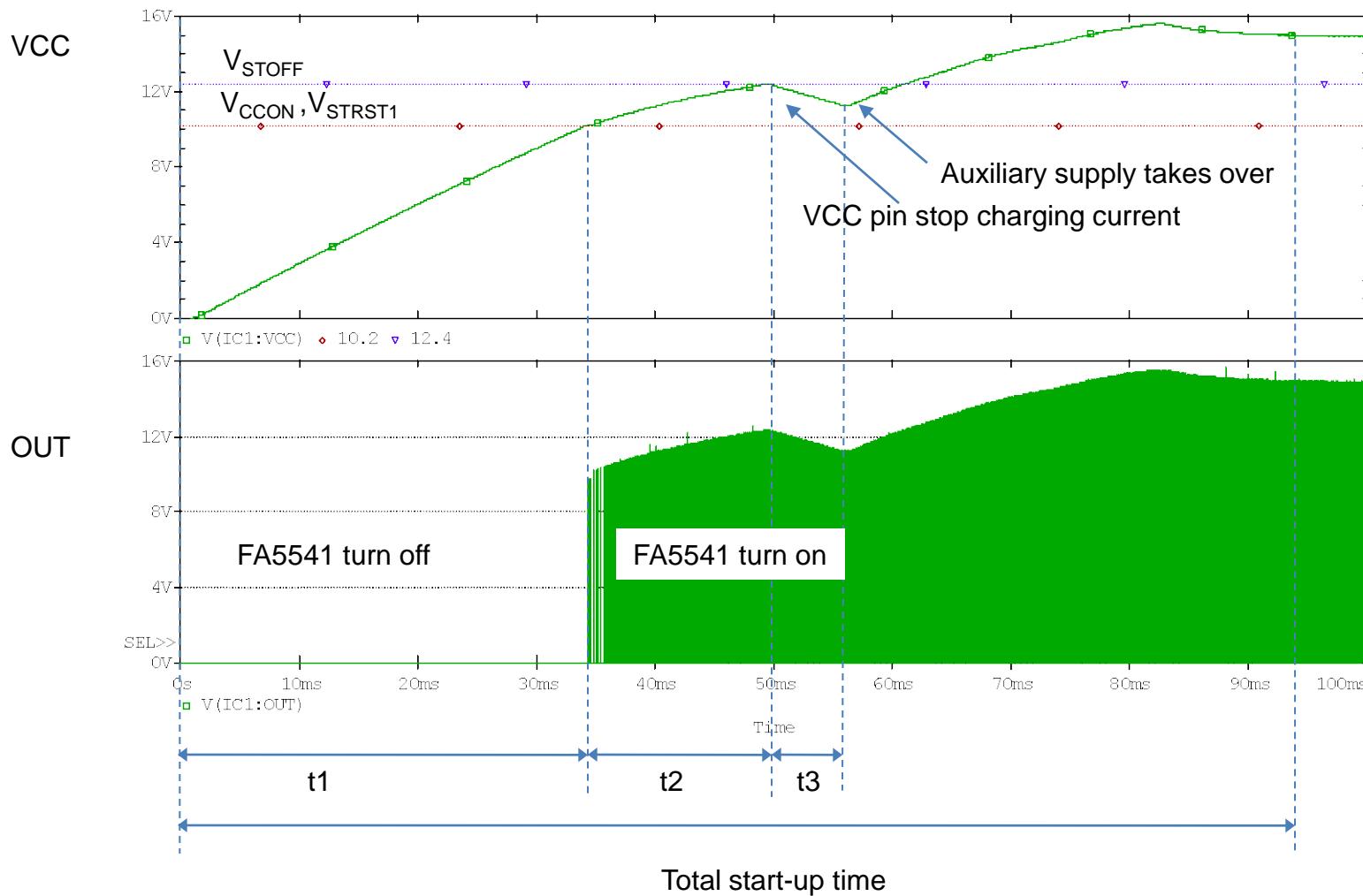

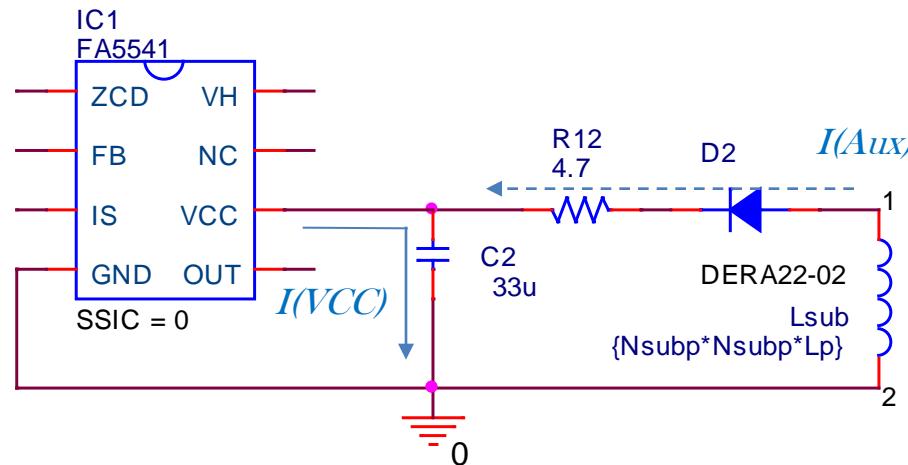3. Start-up sequence simulation

FA5541 under voltage lockout (UVLO) characteristics (VCC pin)

- ON threshold voltage: $V_{CCON} = 10.2V$
- Startup circuit shutdown: $V_{STOFF} = 12.4V$
- Startup circuit reset voltage: $V_{STRST1} = 10.2V$




t1,t2: $V_{CC} < V_{STOFF}$, startup circuit turns on ,VCC pin charges capacitor C_{VCC} (C_2).

t2: V_{CC} reaches V_{CCON} ,FA5541 is turned on


t3: after V_{CC} reaches V_{STOFF} ,startup circuit turns off , V_{CC} decreases until Auxiliary supply takes over.

3. Start-up sequence simulation

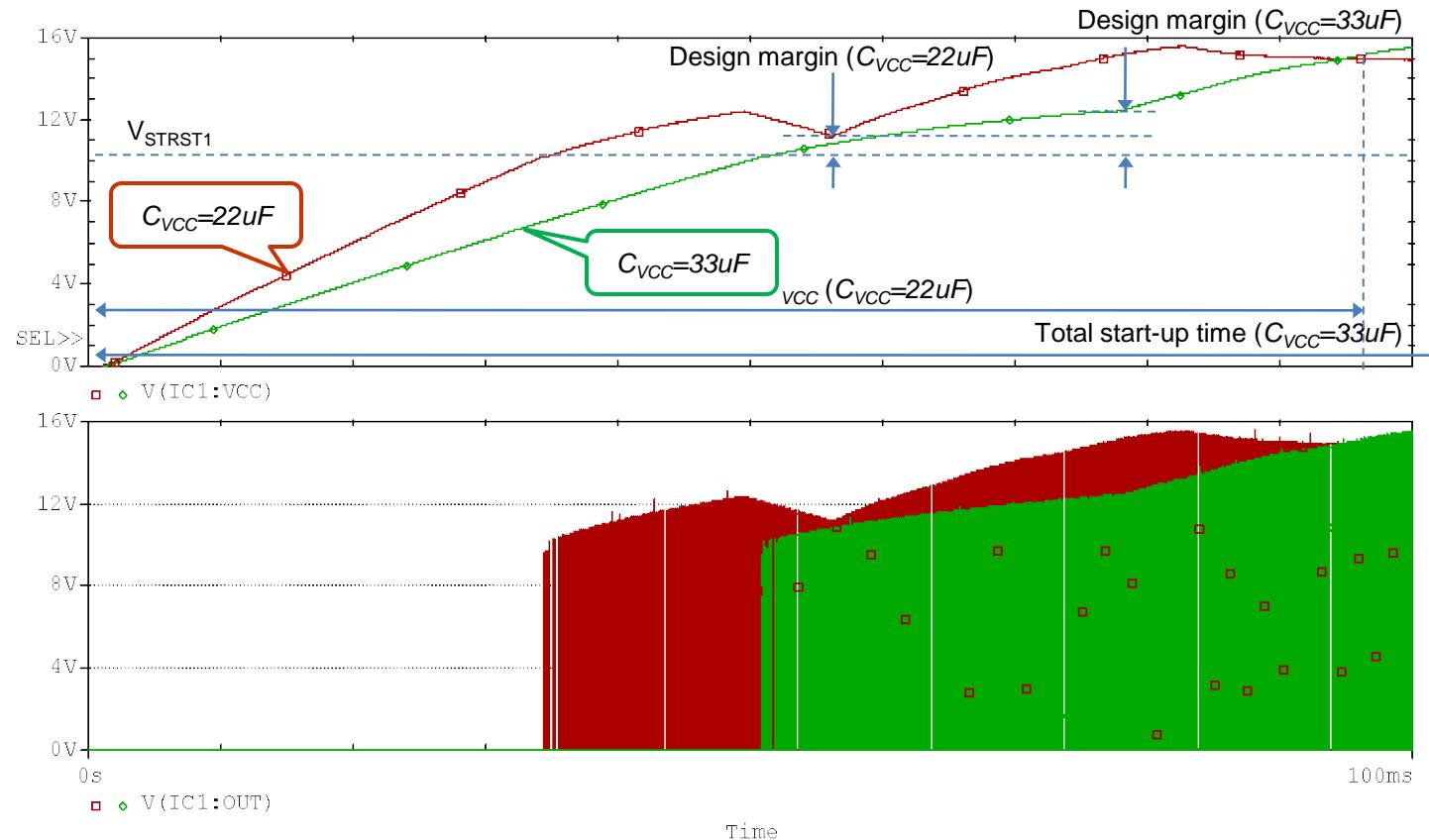


- the simulation result shows the tradeoff between Total start-up time and Design margin, which is the difference of $V(VCC)$ and V_{STRST1} when the auxiliary winding takes over from the IC startup circuit.
- $33\mu F$ -CVCC is selected for higher Design margin although total start-up time is high.

4. Bridge diode peak current at start-up

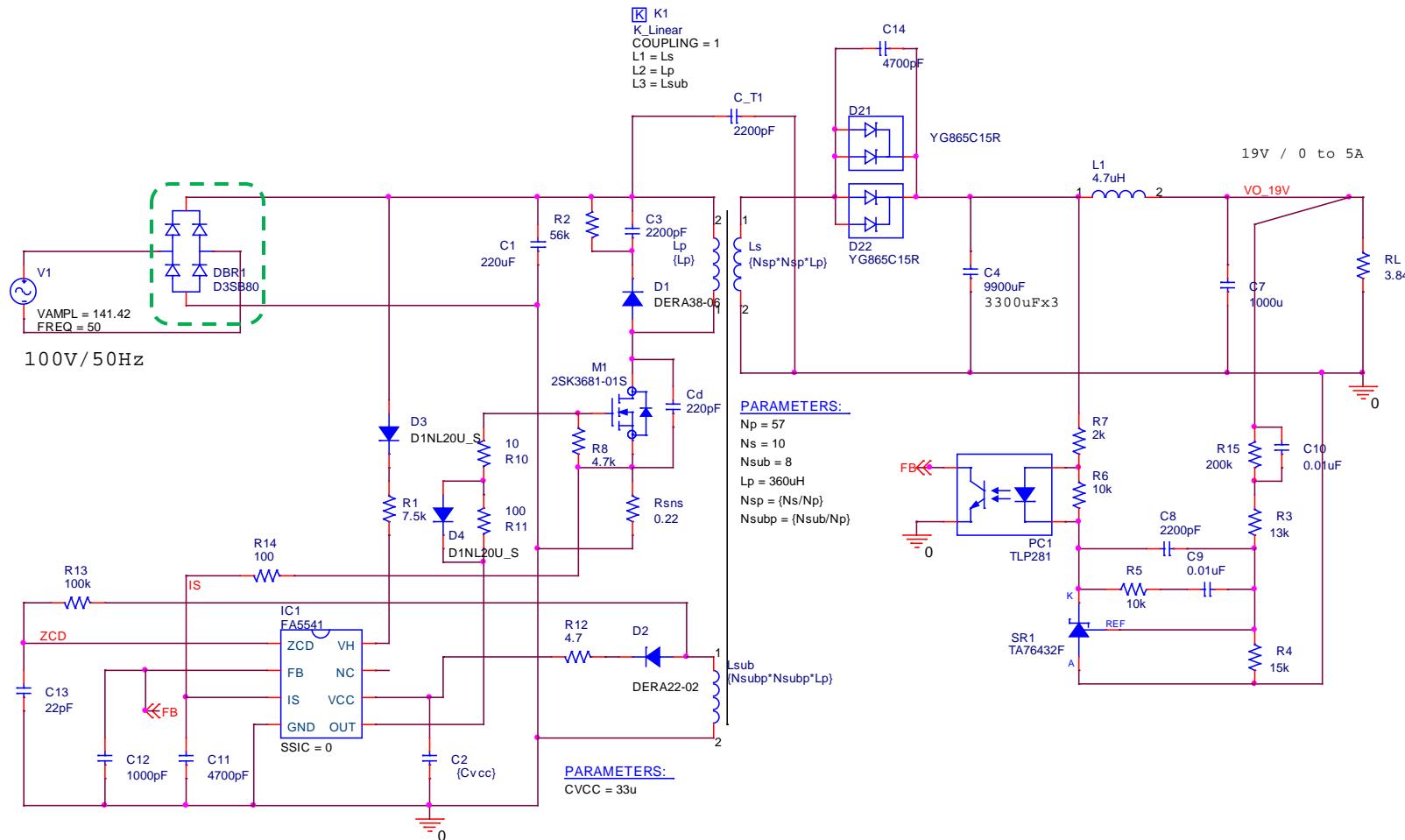


※ No parasitic elements and no initial condition is set

4.Bridge diode peak current at start-up

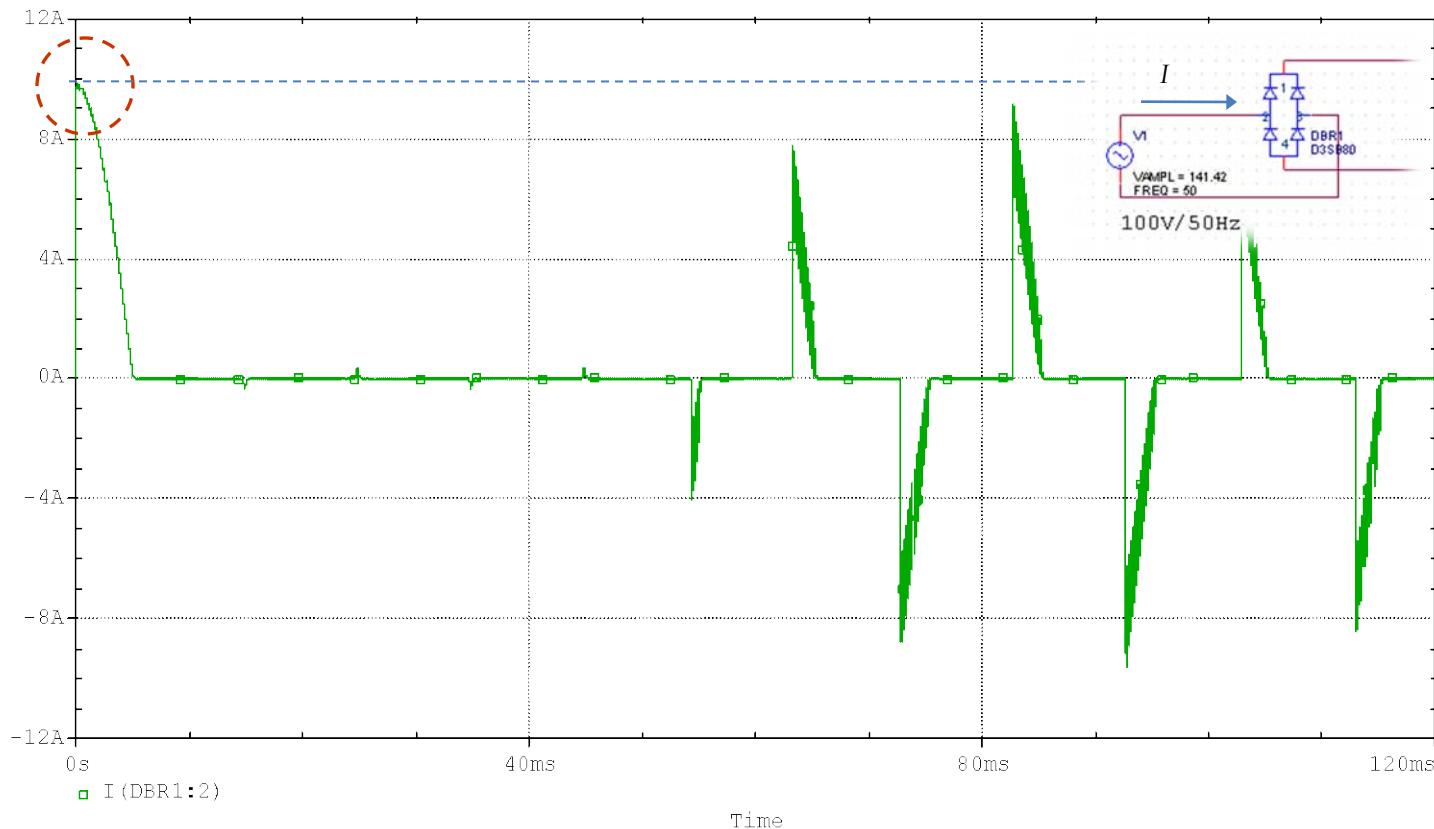


- Simulation result of the current through bridge rectifier diode DBR1 when the power supply is plug to the wall outlet. the peak current is approximately 9.8 which is less than Absolute maximum value IFSM from the datasheet.

5. Transformer

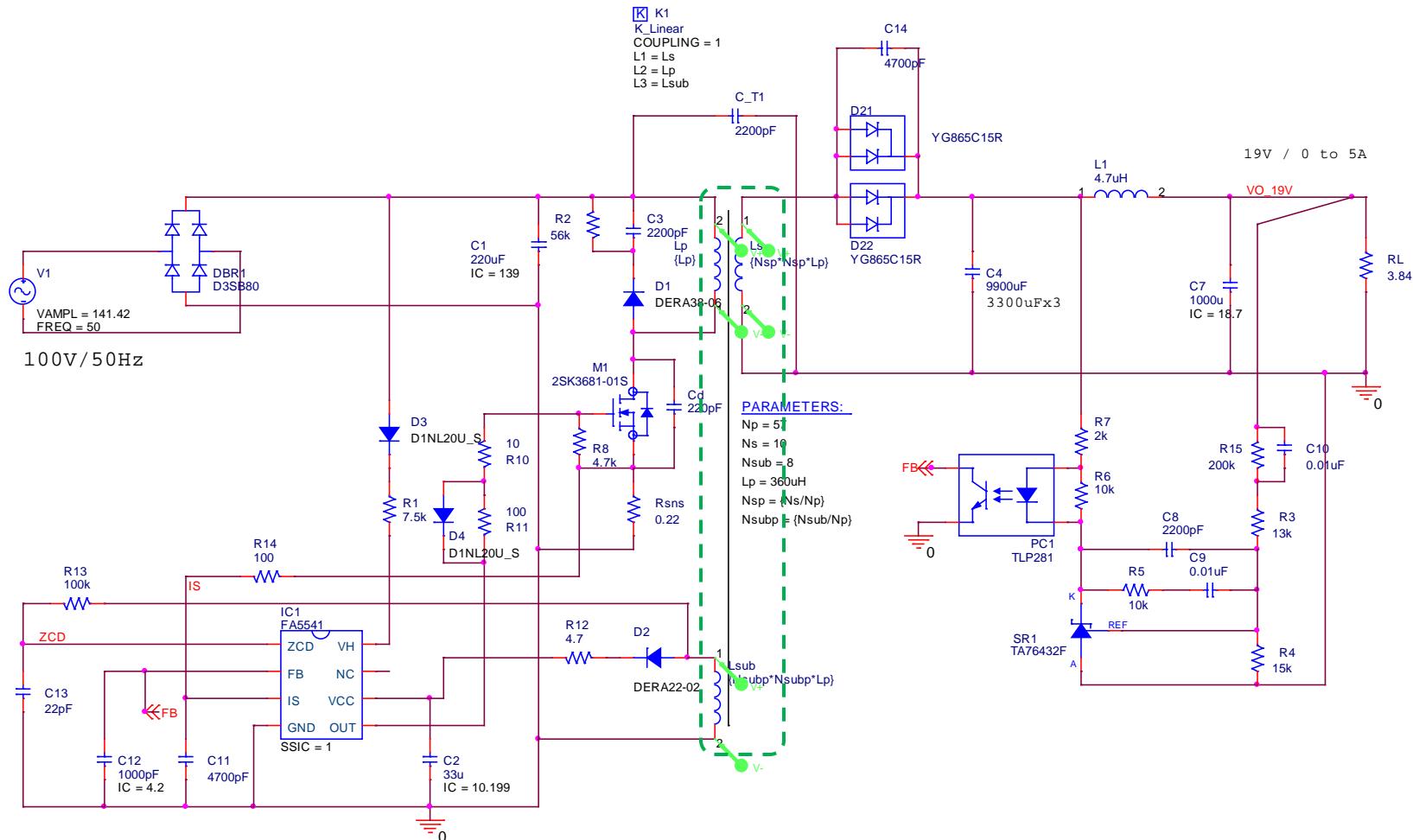


※ No parasitic elements

5. Transformer

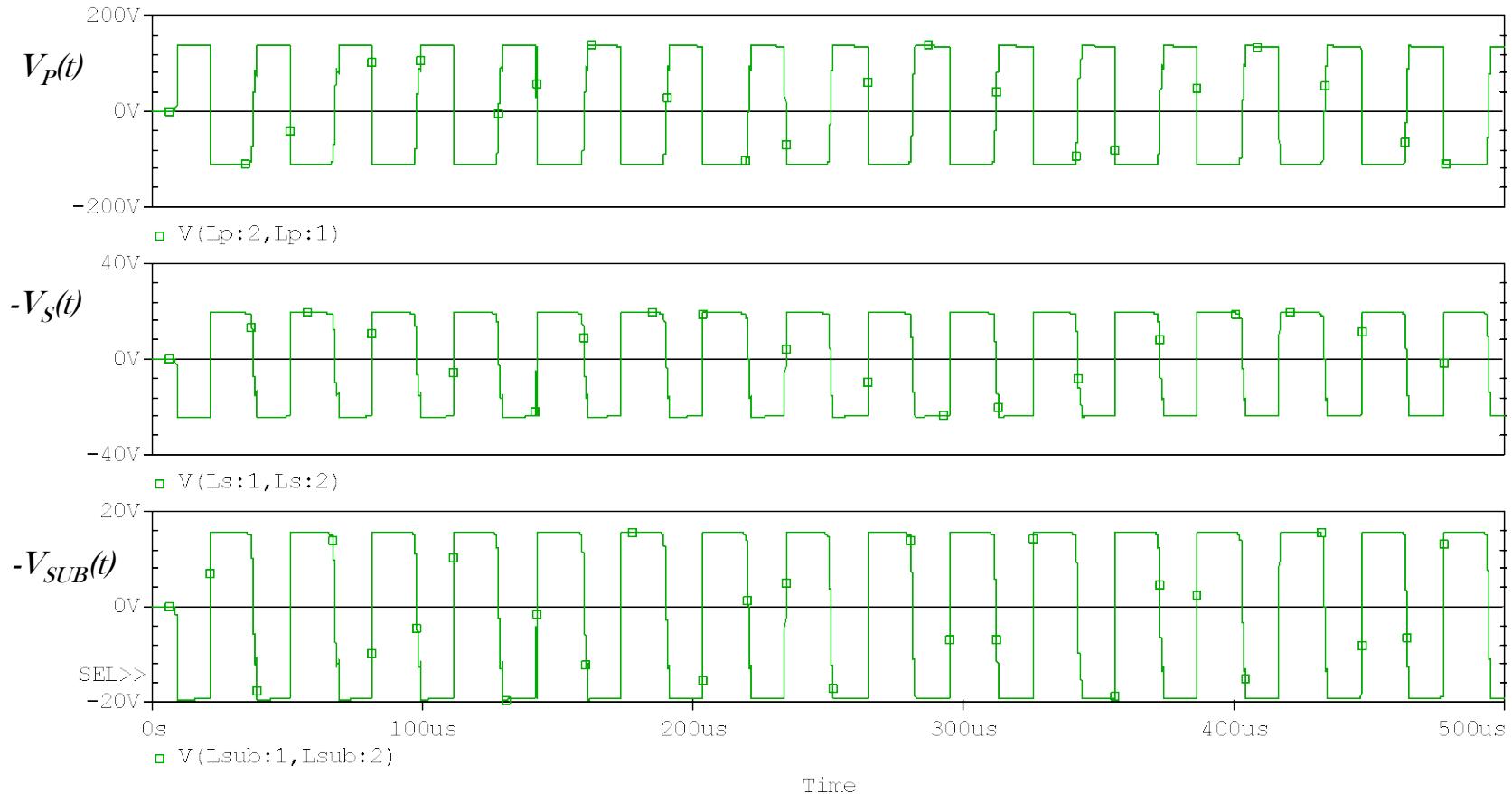

5. Transformer

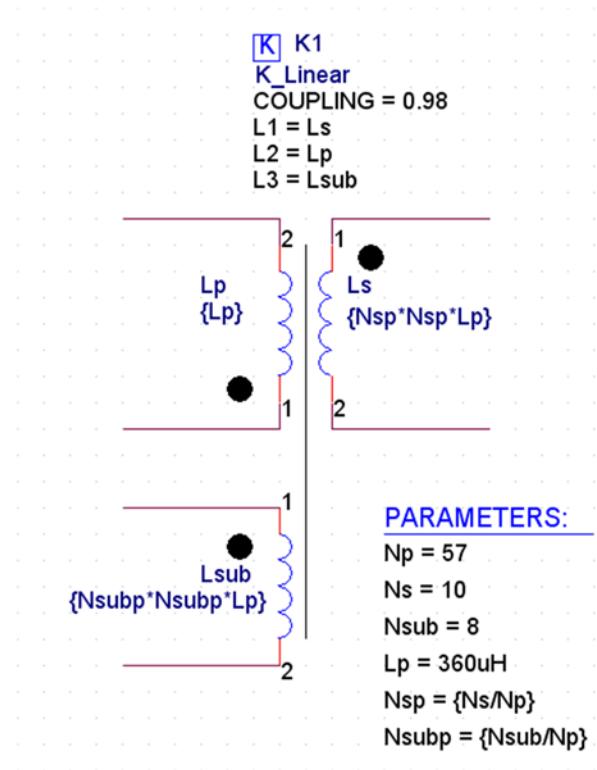

- $L_{leak} = L_P(1-k^2)$
- $L_S/L_P = N^2$


N : winding ratio of the transformer

$$V_S = V_P * (N_S/N_P)$$


$$V_{SUB} = V_P * (N_{SUB}/N_P)$$

- Transformer is modeled by using SPICE primitive k , the transformer spec is $L_p=360\mu H$ and $N_p:N_s:N_{sub}=57:10:8$

6. Transformer leakage inductance

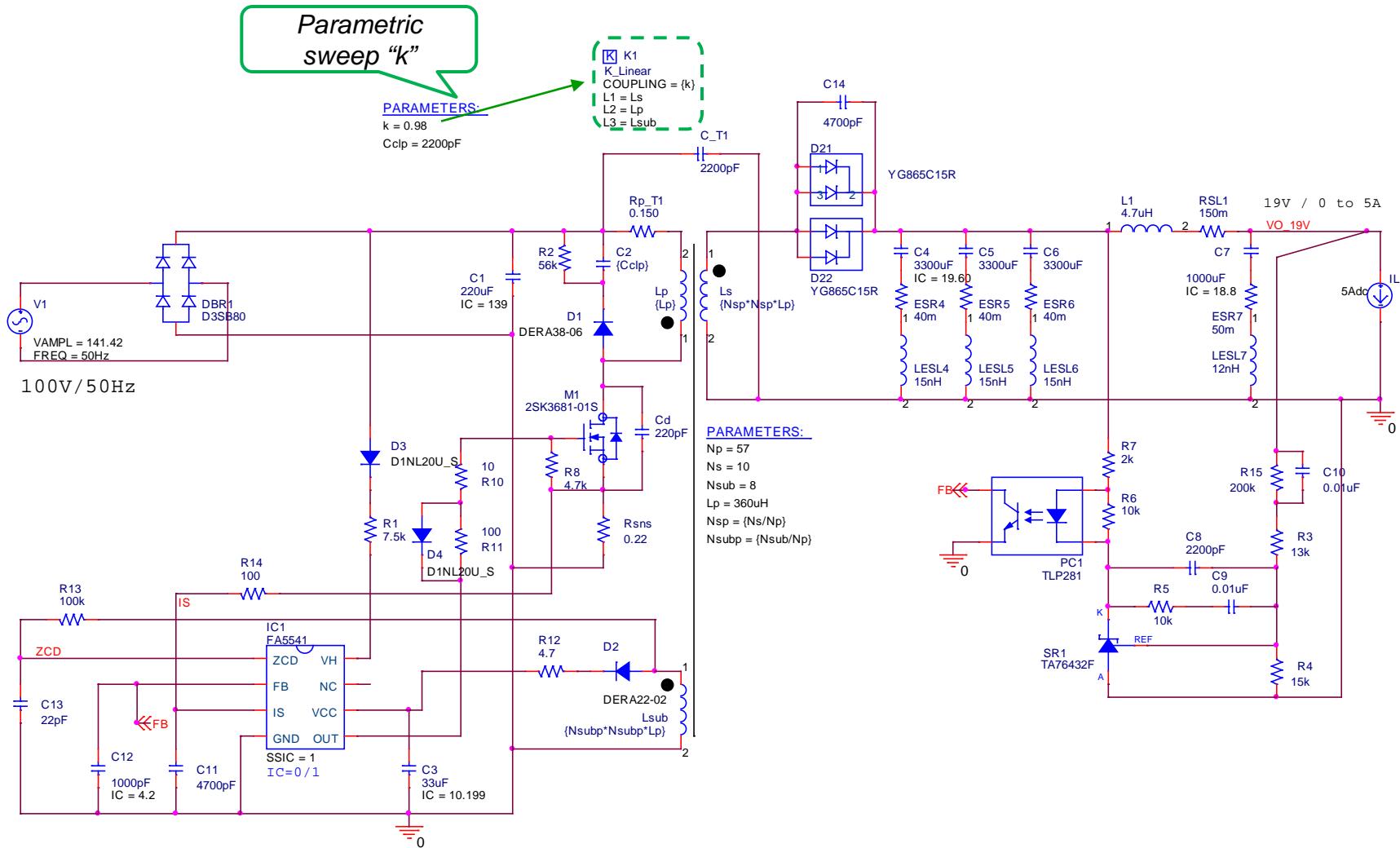


6. Transformer leakage inductance

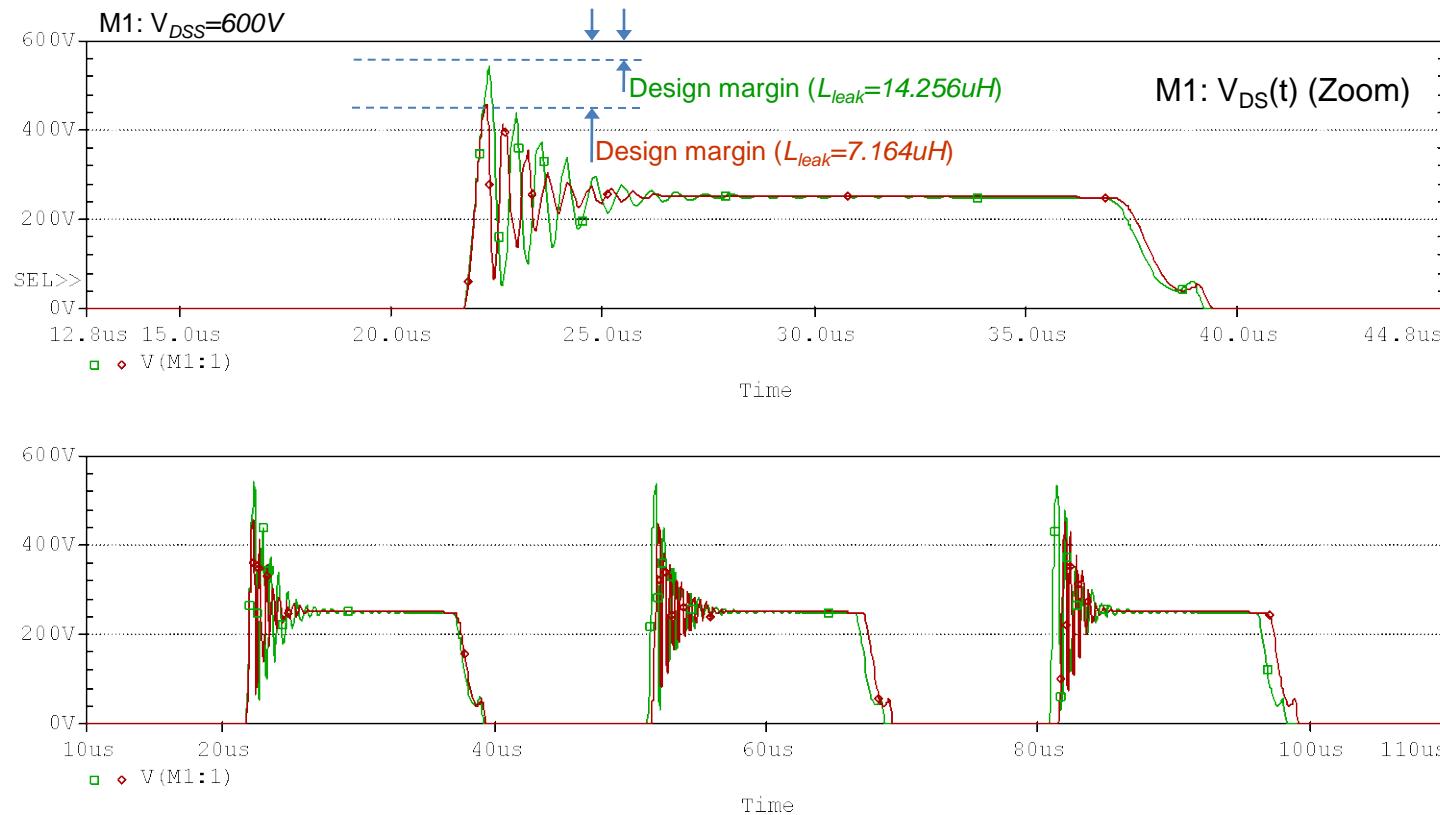


- Transformer model using SPICE primitive k , leakage inductance: $L_{leak} = L_P(1-k^2)$
- $L_P=360\mu H$, leakage inductance is $14.256\mu H$ for $k=0.98$ and $7.164\mu H$ for $k=0.99$
- Check the VDS overshoot voltage versus the transformer leakage inductance.

7.RCD Clamping network

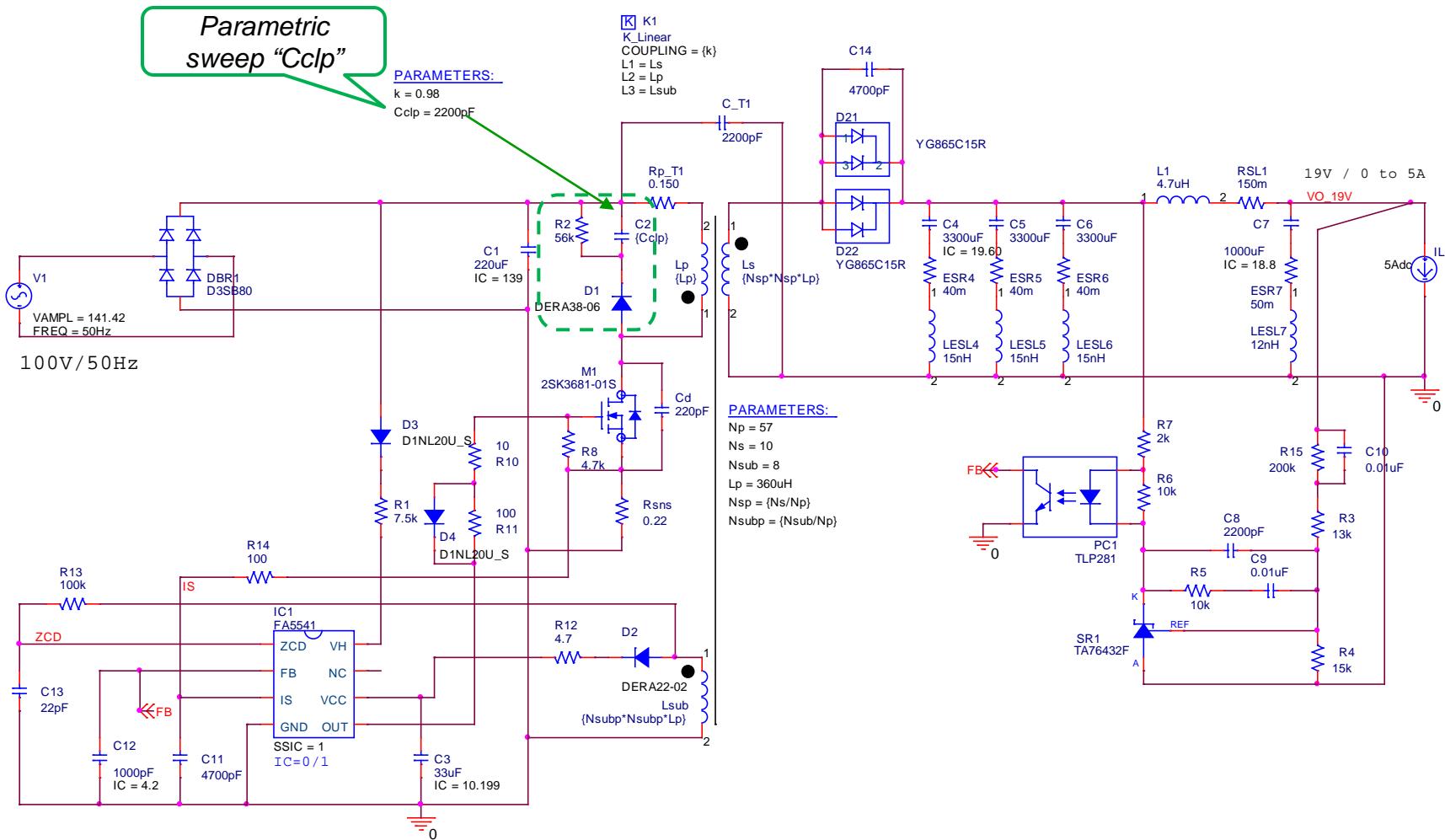


7.RCD Clamping network

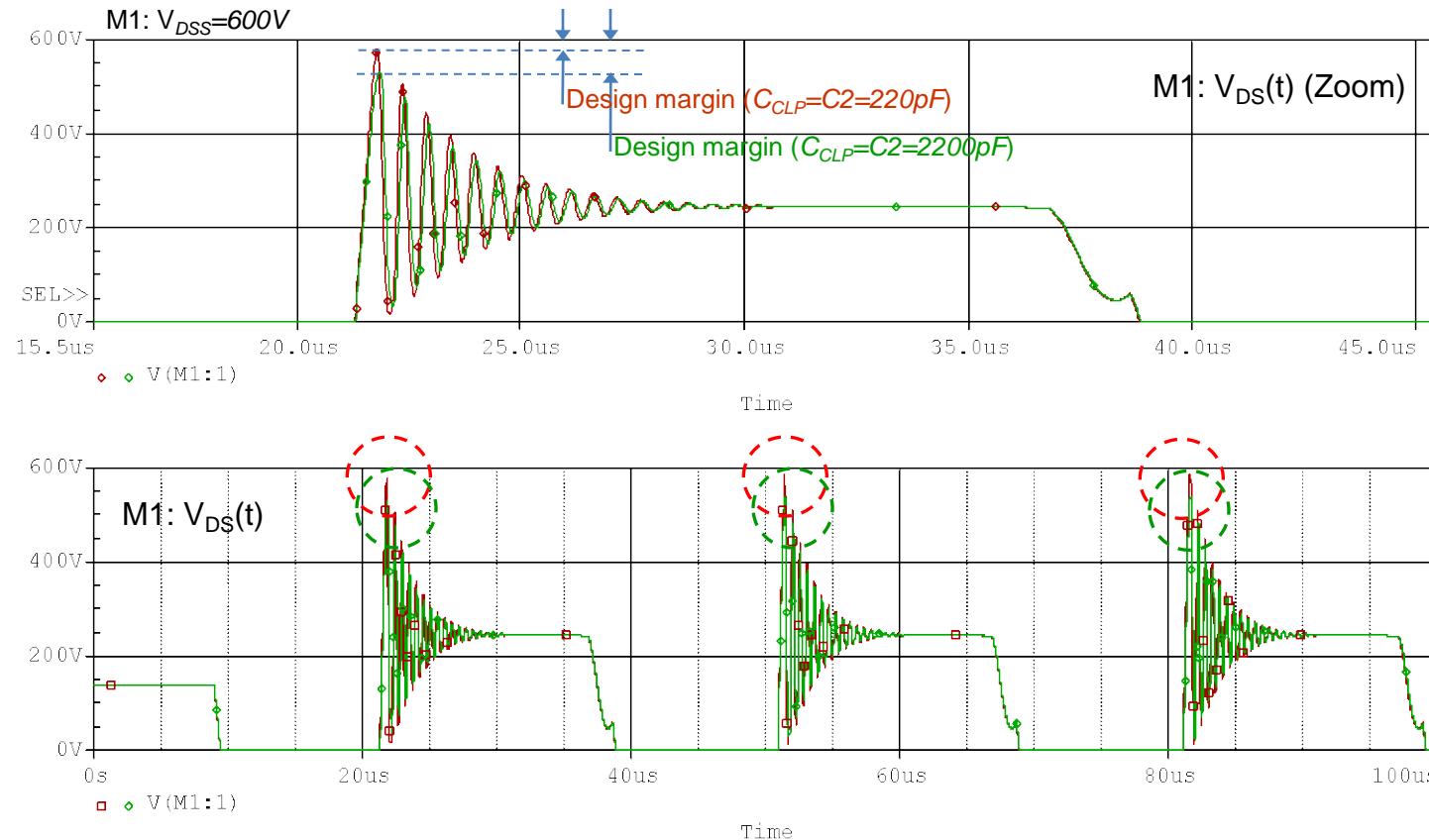


- Compare V_{DS} overshoot of the circuit with $C_{CLP}(C_2) = 220\text{pF}$ and 2200pF , larger C_{CLP} value get better design margin for MOSFET V_{DS}
- $C_{CLP}=2200\mu\text{F}$ is selected for the better M1: V_{DS} design margin.

8.Power MOSFET switching device

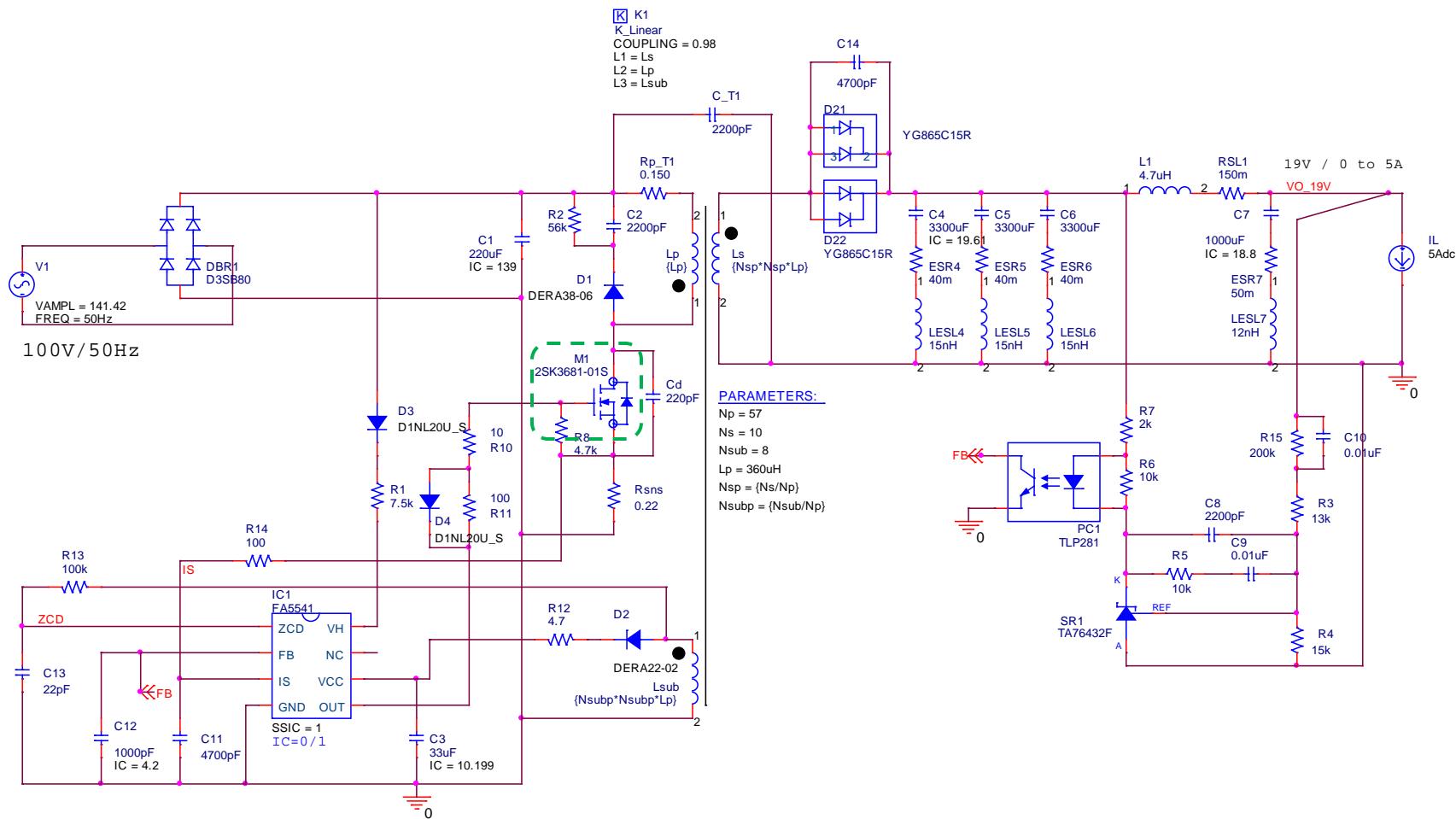


8.Power MOSFET switching device

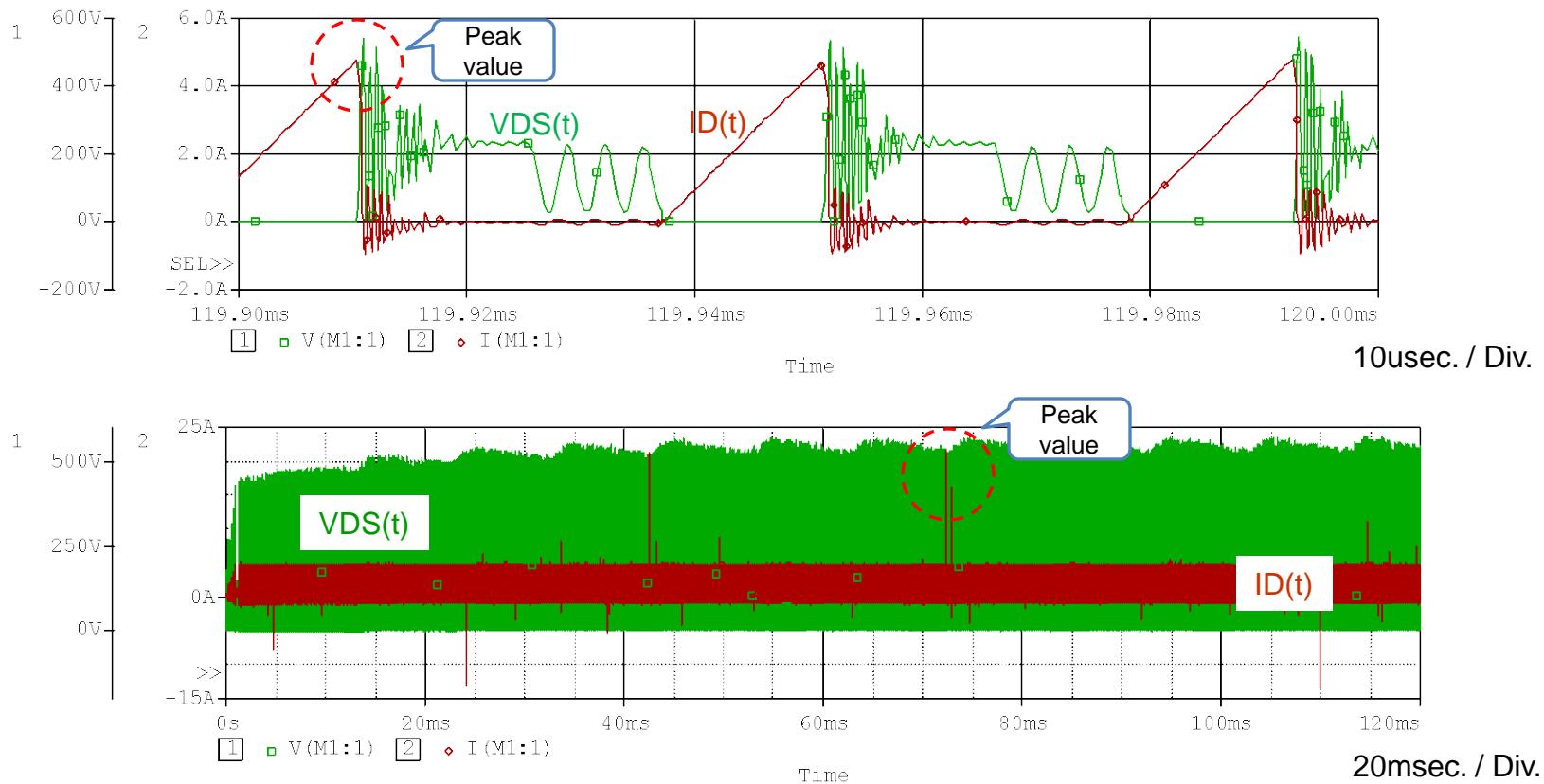


- Simulation results shows the peak value of M1: VDS and ID .

8.Power MOSFET switching device


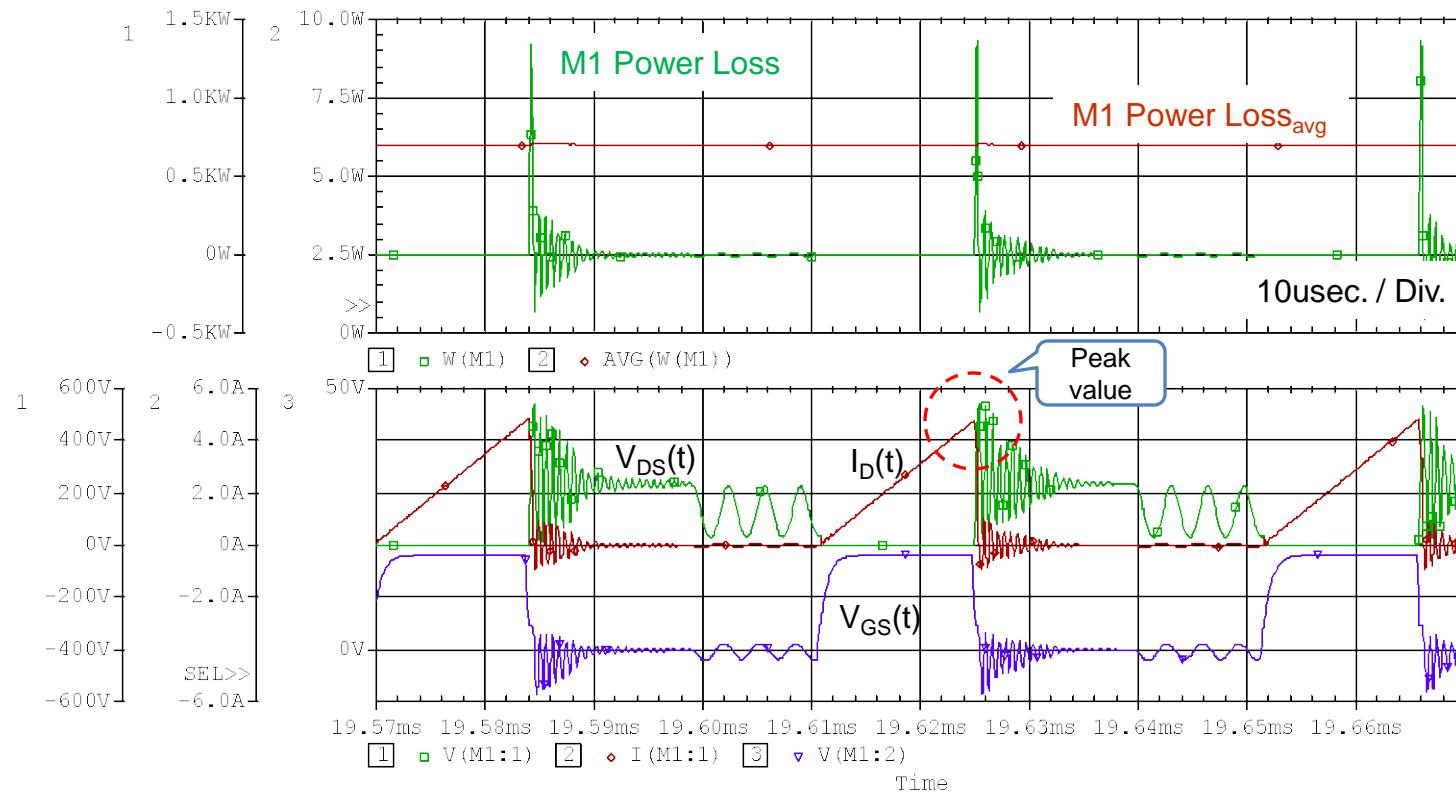


- Simulation results shows the peak value of MOSFET VDS and ID . Calculated switching power loss and average power loss are also shown

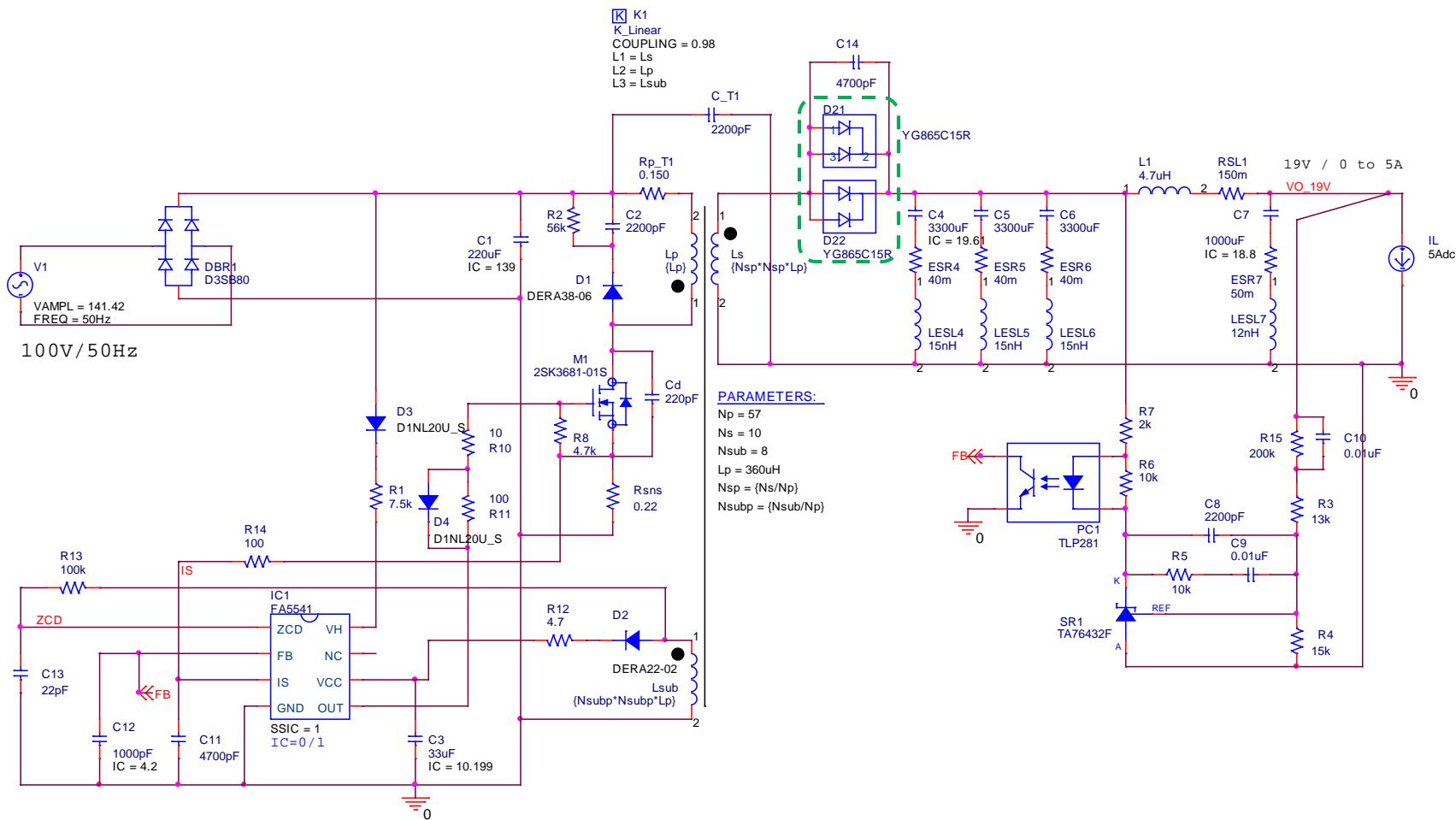9. Schottky barrier diode D21 and D22 waveforms




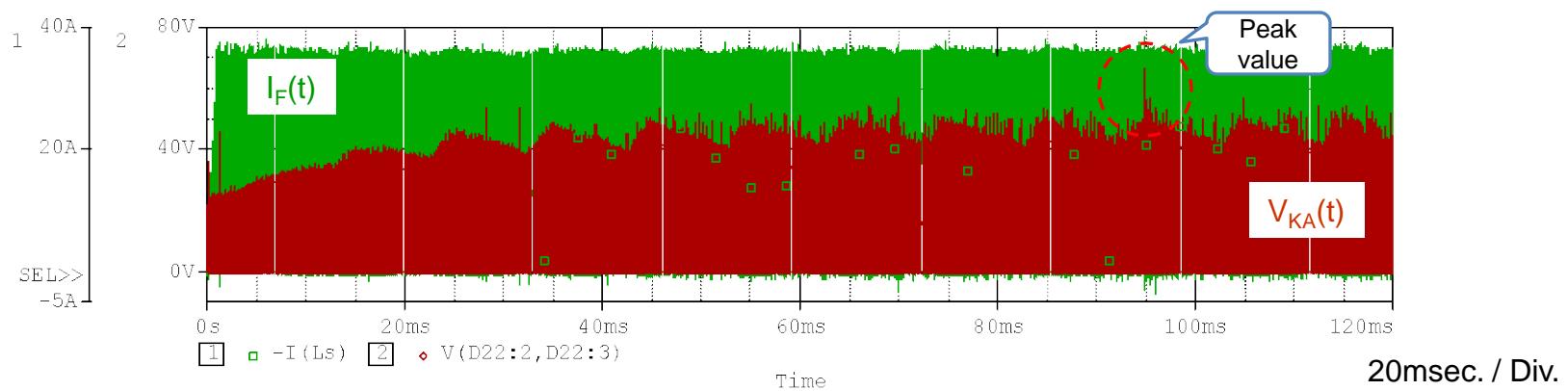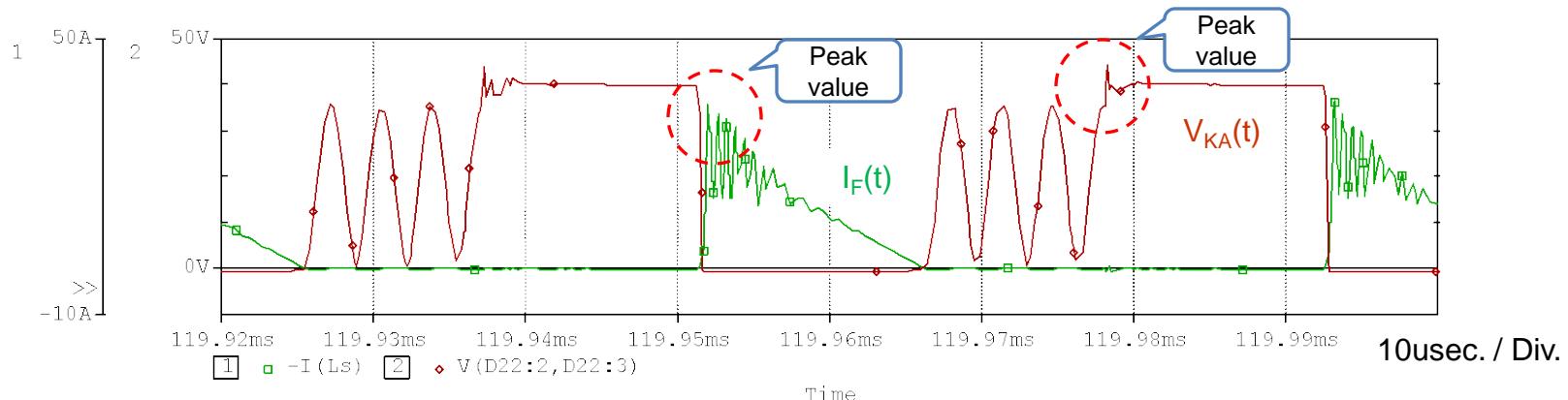9. Schottky barrier diode D21 and D22 waveforms




- Simulation results shows the peak value of SBD: V_{KA} and I_F .

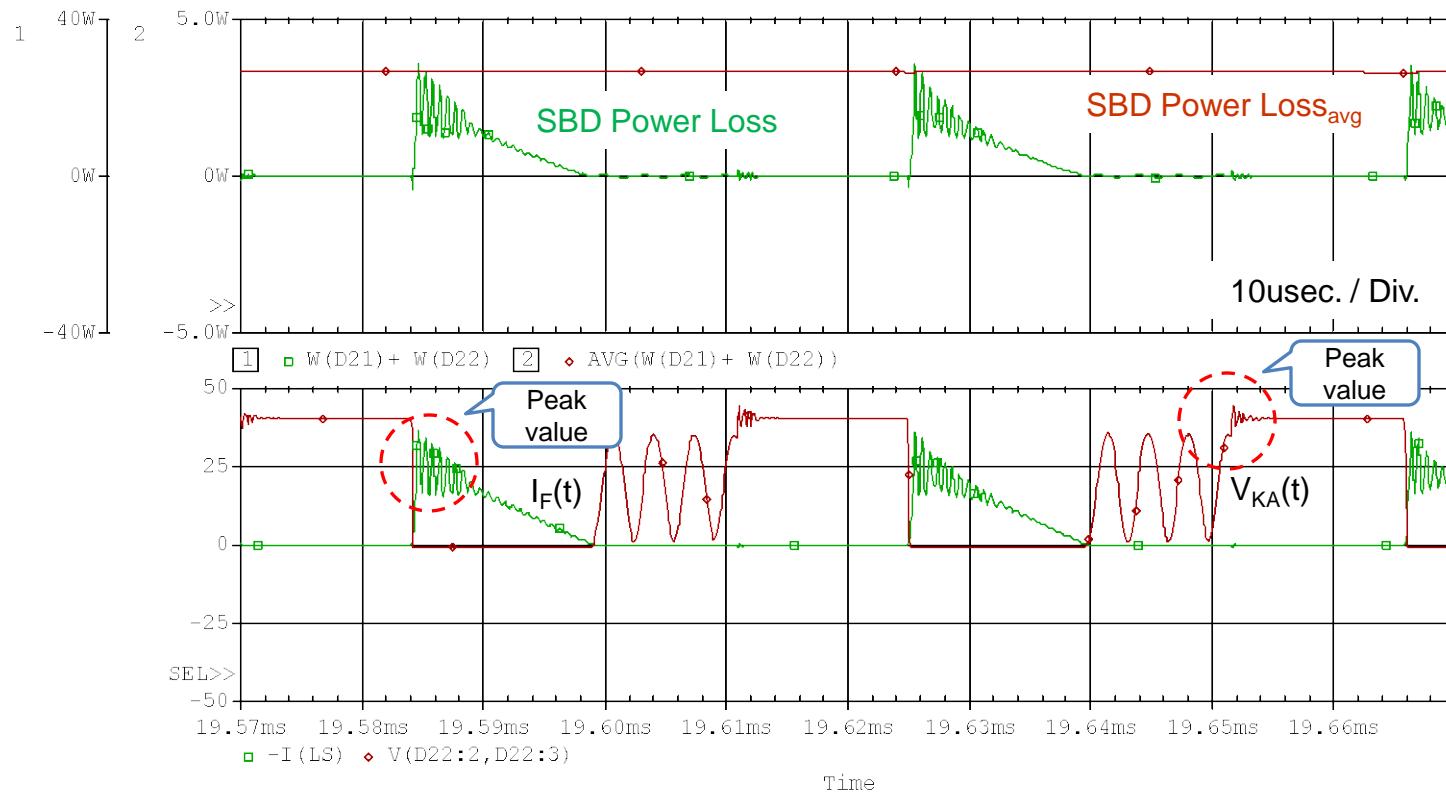9.Schottky barrier diode D21 and D22 waveforms




- Simulation results shows the peak value of SBD V_{KA} and I_F . Calculated power loss and average power loss are also shown

10. Photocoupler

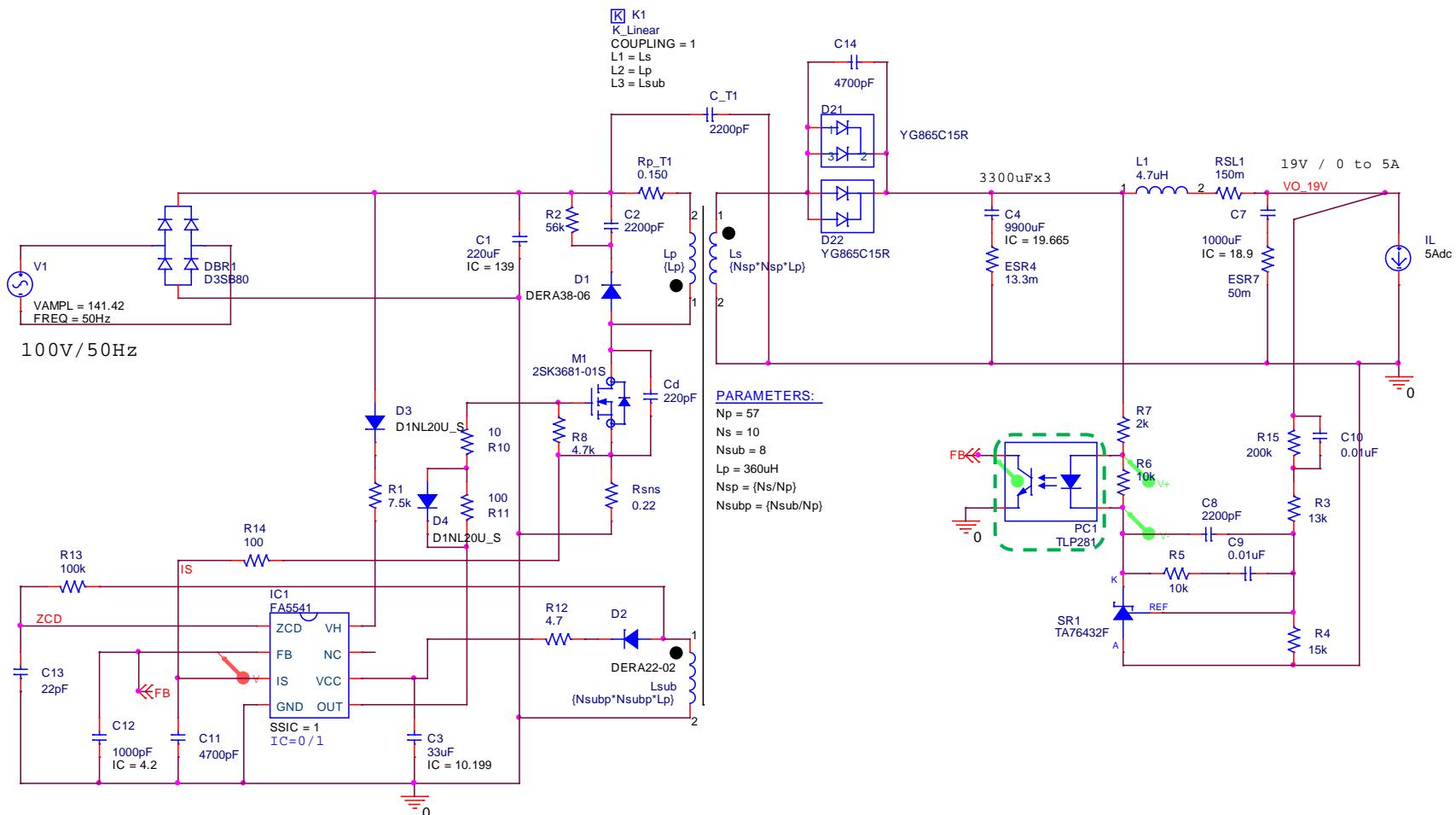

* No parasitic elements: Leak and ESL ,to aid simulation convergence

10. Photocoupler

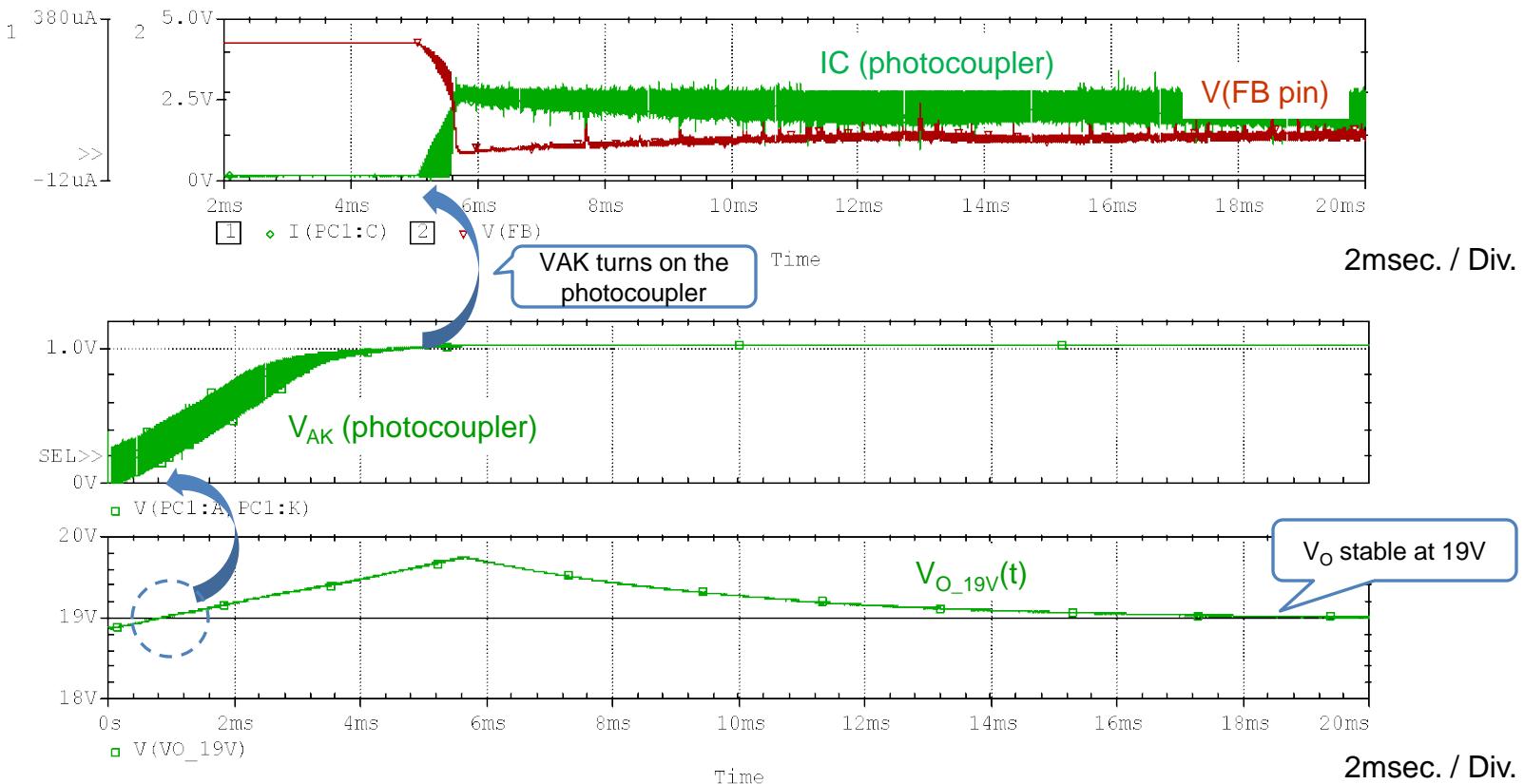

- When power supply output reaches spec voltage (19V), a shunt regulator draws current through resistor (R6) and VAK of photocoupler increases.
- When VAK turns on photocoupler, collector current I_c increases. This causes FB pin voltage to decrease before power supply output voltage go to the stable state.

Simulations index

Simulations	Folder name
1. Start-up sequence simulation.....	Startup
2. Quasi-Resonant Switching Power Supply Waveforms.....	Waveforms
3. Step-load response.....	Stepload
4. Power switch devices (M1 and SBD losses)	Losses
5. Variable design parameters ($L_{I_{\text{eak}}}$ and C_2)	Params