

# Design Kit

## 2-Phase Bipolar Stepping Motor Driver Using TB62206FG



# Contents

	Slide #
1. Background	
1.1 Bipolar Stepping Motors.....	3
1.2 Torque vs. Speed.....	4
1.3 Bipolar Operating Mode.....	5-6
2. Application Circuit.....	7
2.1 Specification.....	8-9
2.2 Calculating Equations.....	10
3. Stepper Motor Switching Sequences	
3.1 Full Step Switching Sequence.....	11-12
3.2 Half Step Switching Sequence.....	13-14
4. Functions	
4.1 STANDBY.....	15-16
4.2 TORQUE.....	17-18
4.3 Phase A Over-current Protection.....	19-20
4.4 Phase B Over-current Protection.....	21-22
5. Output Ripple Current.....	23
5.1 Stepping Motor Phase Inductance at The Chopping Frequency.....	24
5.2 Ripple Current Simulation.....	25-26
6. The Current Changing Rate.....	27
6.1 Stepping Motor Phase Inductance at The Phase Frequency.....	28
6.2 Current Changing Rate Simulation.....	29-30
7. Optimization of The Drive Voltage VM.....	31-32
Simulations index.....	33

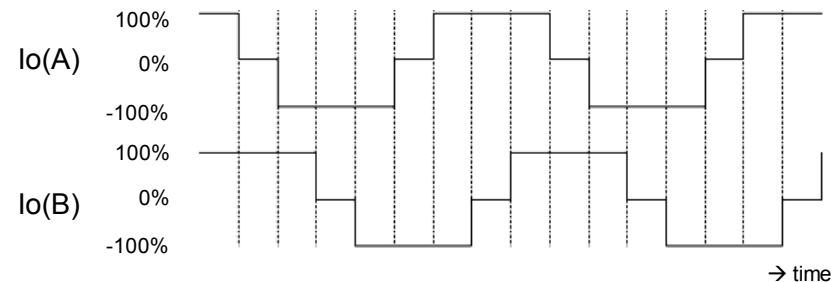
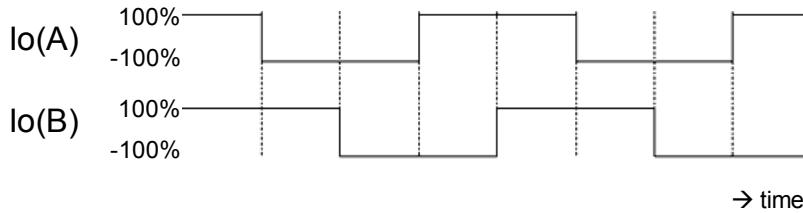
## 1.1 Bipolar Stepping Motors



- There are two winding with no center taps.
- The drive circuitry requires an H-bridge control circuit for each winding, as the drive circuit need to change the polarity of each pair of motor poles.
- The current sequences are shown below.
- Full Step
- Half Step




## 1.2 Torque vs. Speed

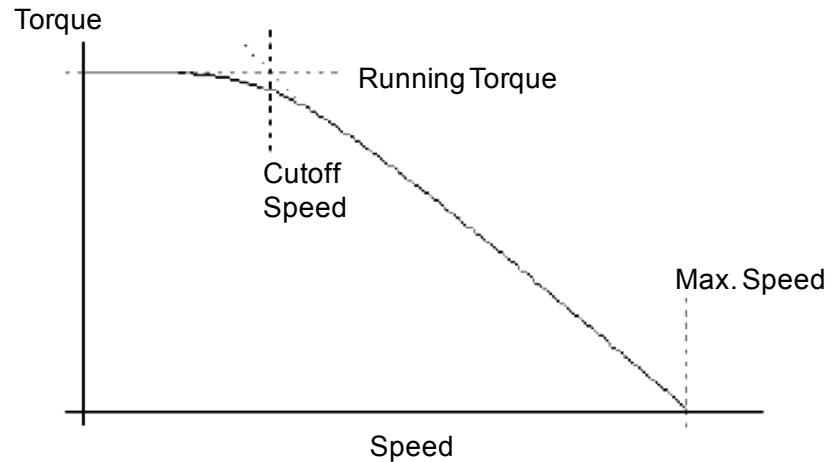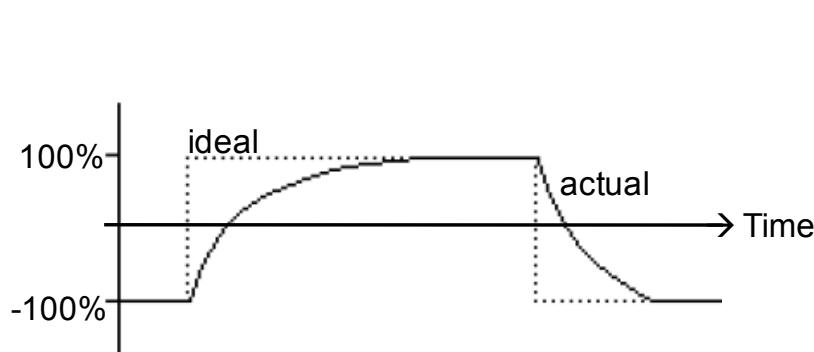


- The inductance of the motor winding determines the rise and fall time of the current through the winding.
- The current-vs-time function through each winding depend on the drive circuitry and the motor characteristics.
- The rise time is determined by the drive voltage, while the fall time depends on the circuitry used to dissipate the stored energy in the motor winding (fast or slow decay).
- The effect of the inductance of the motor windings is to reduce the available torque, as shown in the Torque-vs-Speed curve.

## 1.3 Bipolar Operating Mode


Charge mode

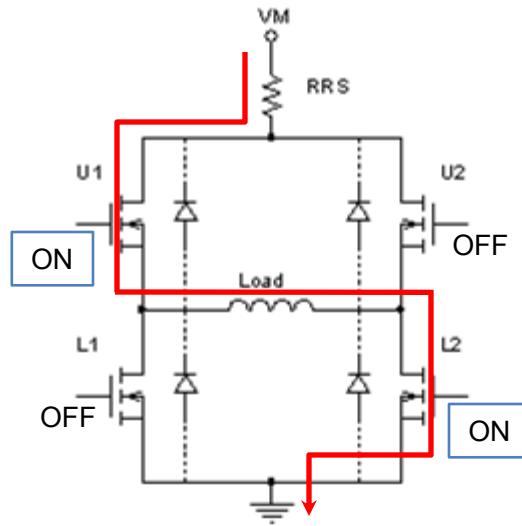

Slow decay mode

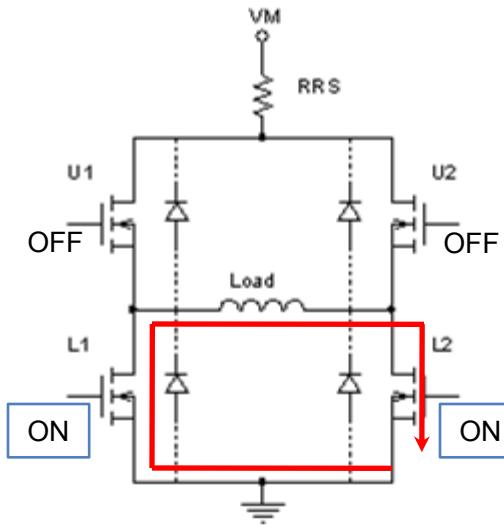

Fast decay mode

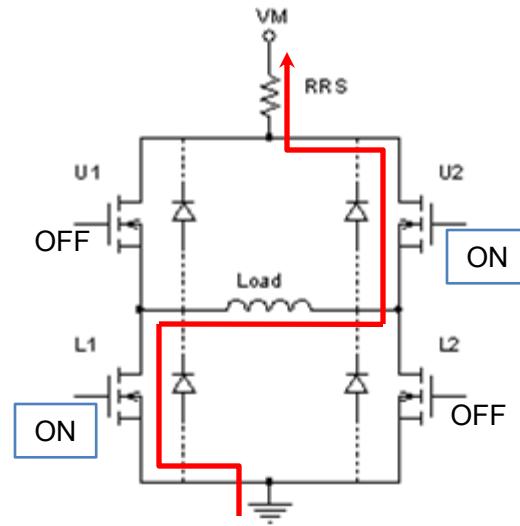

- These figures show how TB62206FG switches the current in each motor winding on and off, and controlling its direction, in three different modes.

## 1.3 Bipolar Operating Mode


---

- Charge mode, the H-bridge forward state to allow current to flow from the supply through the motor winding and onward to ground.
- Slow decay mode, in this mode, winding current is re-circulated by enabling both of the low-side FETs in the bridge.
- Fast decay mode, the H-bridge reverses state to allow winding current to flow in a reverse direction.

	U1	U2	L1	L2
Charge	ON	OFF	OFF	ON
Slow	OFF	OFF	ON	ON
Fast	OFF	ON	ON	OFF

- In TB62206FG, three modes as shown above are automatically switched to control the constant current

## 2. Application Circuit

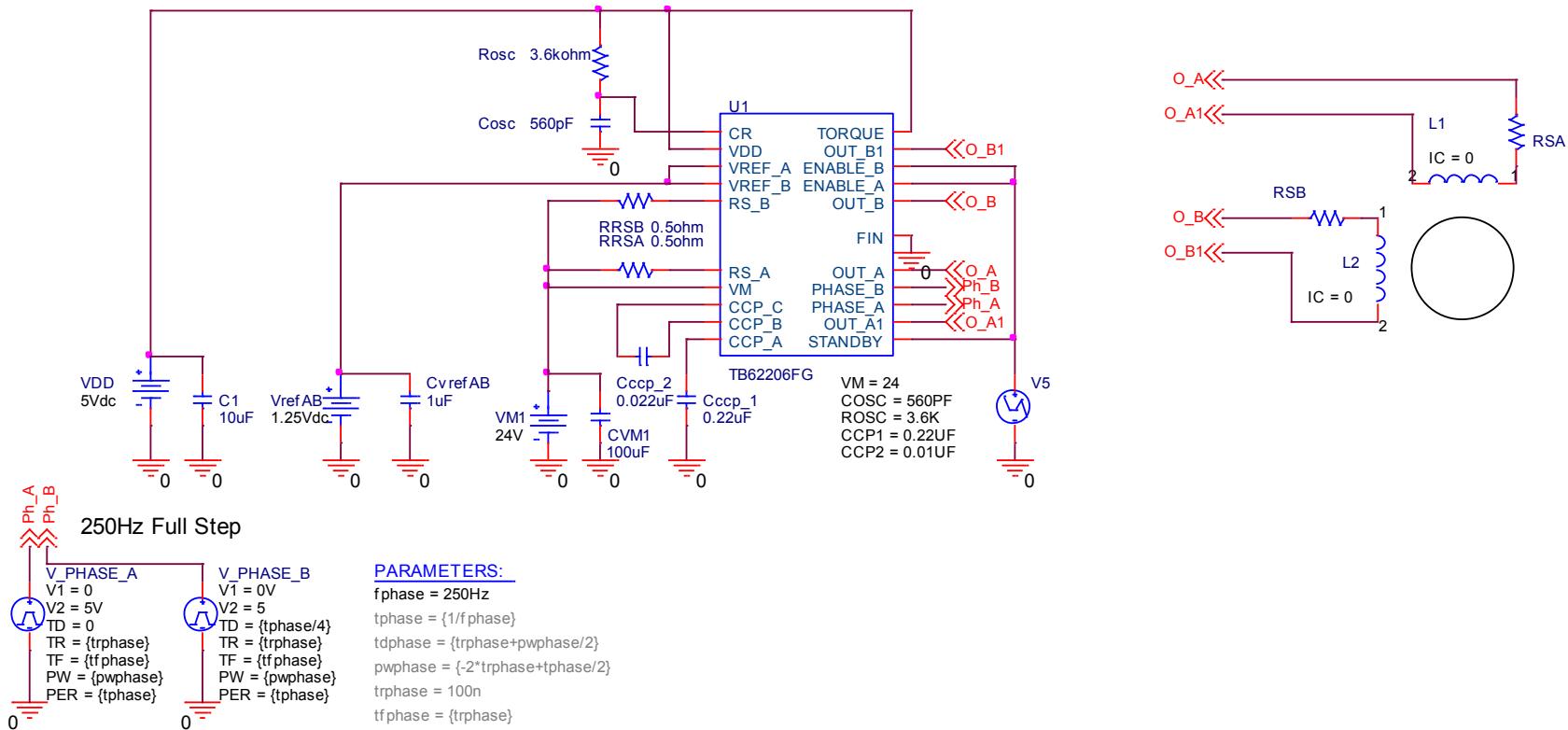


## 2.1 Specification

### Operating Conditions

Characteristics	Symbol	Value	Unit
Power supply voltage	$V_{DD}$	5	V
Motor supply voltage	$V_M$	24	V
Reference voltage	$V_{REF}$	1.25	V
Logic input voltage	$V_{IN}$	5	V
Output current	$I_{OUT}$	0.5	A
Phase signal input frequency	$f_{PHASE}$	250	Hz
Chopping frequency	$f_{chop}$	101	kHz
Oscillation frequency	$f_{CR}$	813	kHz

## 2.1 Specification

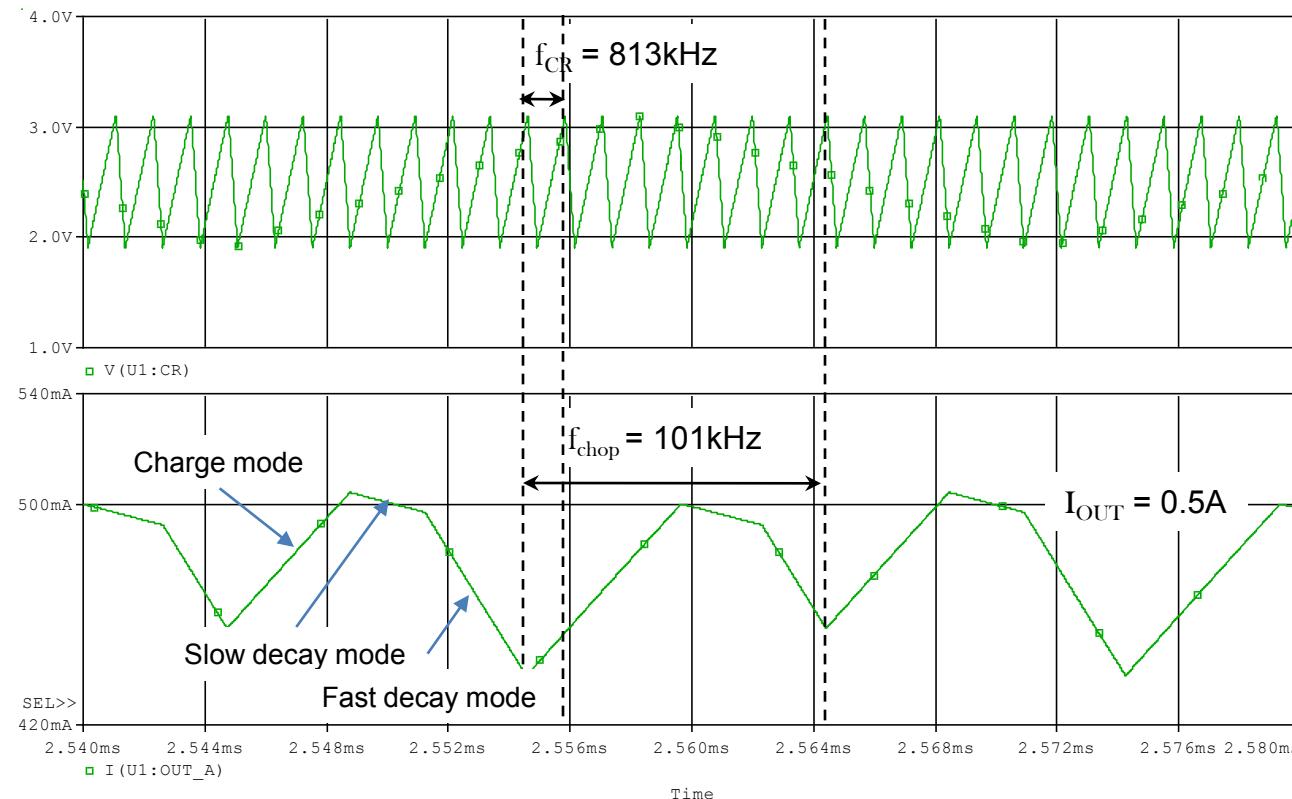

- This figure shows the output current  $I_{OUT}$ , the oscillation frequency  $f_{CR}$ , and the chopping frequency  $f_{chop}$ .

## 2.2 Calculating Equations

---

- The output current value (set current value) can be determined by setting the sensing resistor ( $R_{RS}$ ) and reference voltage ( $V_{ref}$ ).

$$I_{OUT} = \frac{1}{5} \times V_{ref} \times \frac{Torque_{(Torque=100,71\%)}}{R_{RS} \times 100\%} \quad (1)$$


- The oscillation frequency is calculated as follows:

$$f_{CR} = \frac{1}{0.523 \times (C_{osc} \times R_{osc} + 600 \times C)} \quad (2)$$

- The chopping frequency  $f_{chop}$  is calculated as follows:


$$f_{CR} = \frac{f_{chop}}{8} \quad (3)$$

## 3.1 Full Step Switching Sequence

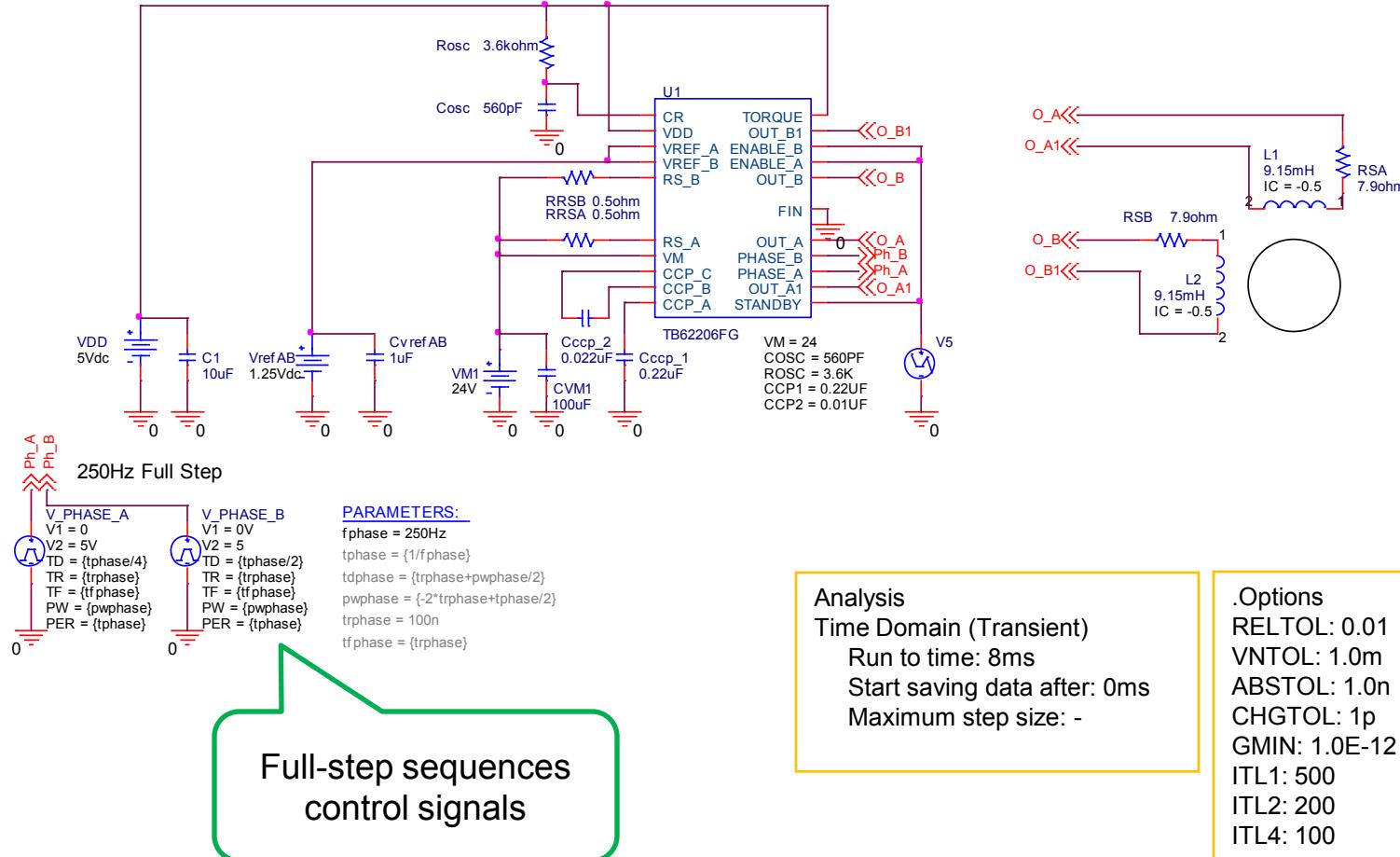


Full-step sequences  
control signals

### 3.1 Full Step Switching Sequence

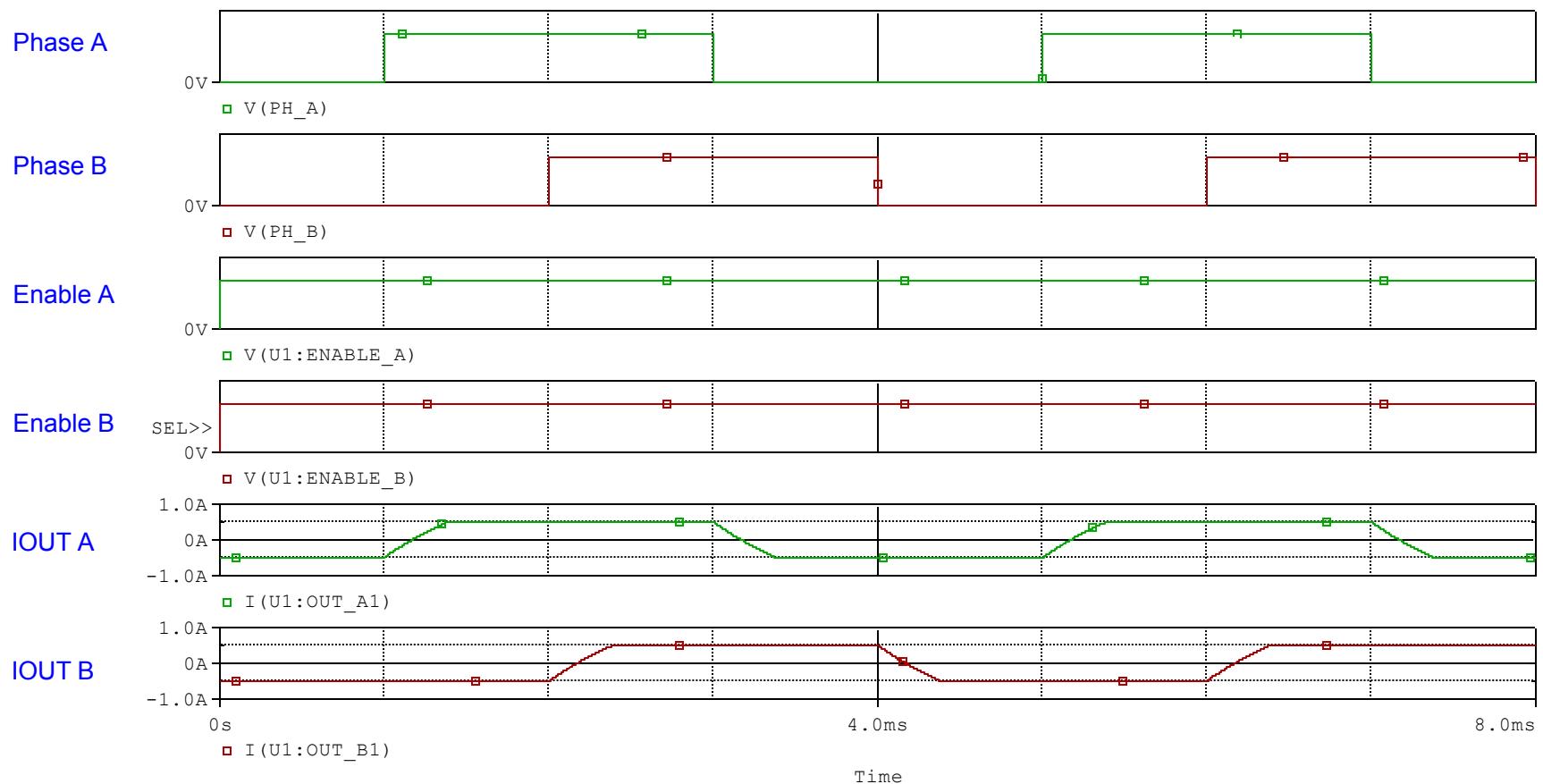


- This figure shows the simulation result of the circuit with Full-step switching sequence.

## 3.2 Half Step Switching Sequence

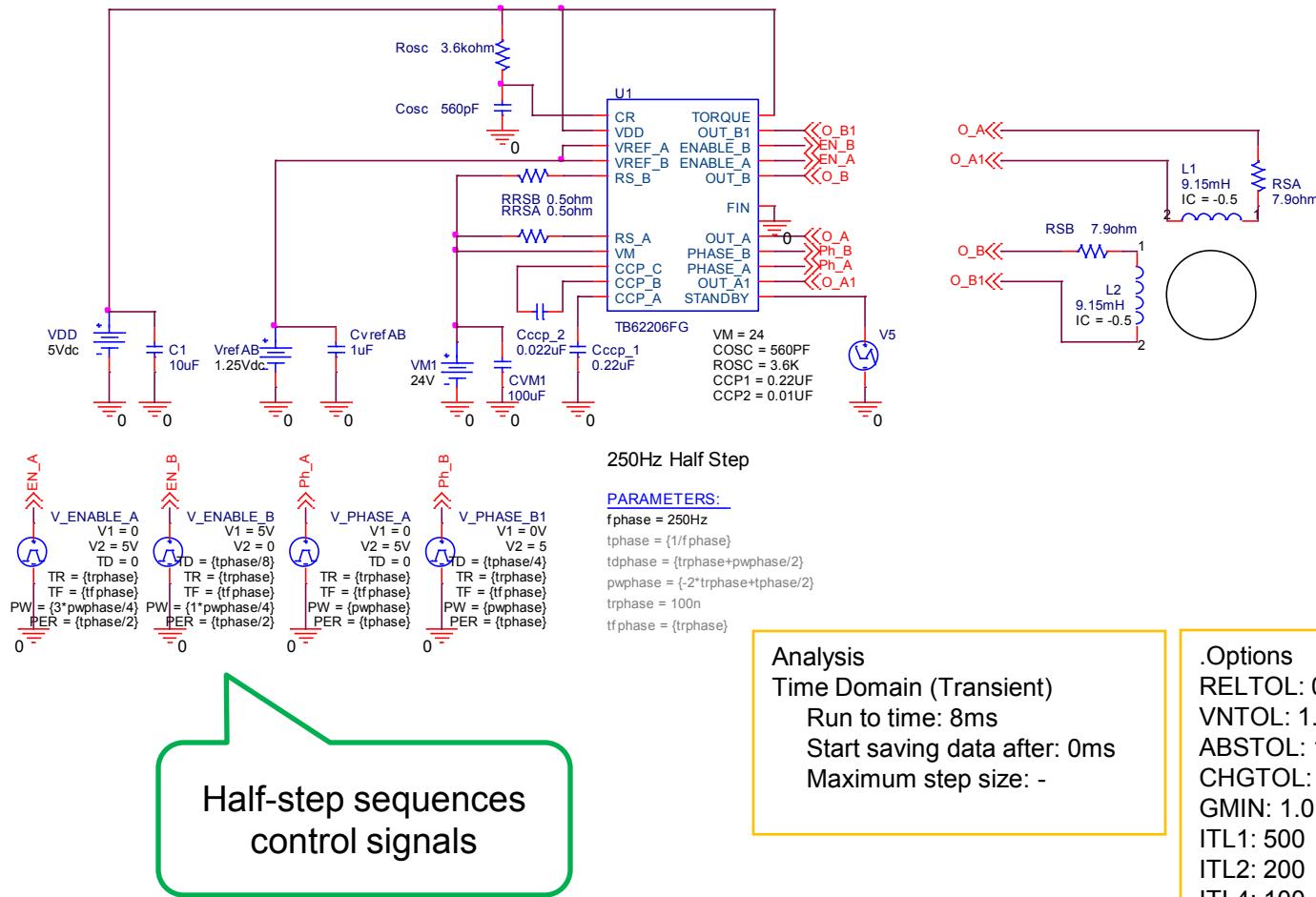


## 3.2 Half Step Switching Sequence

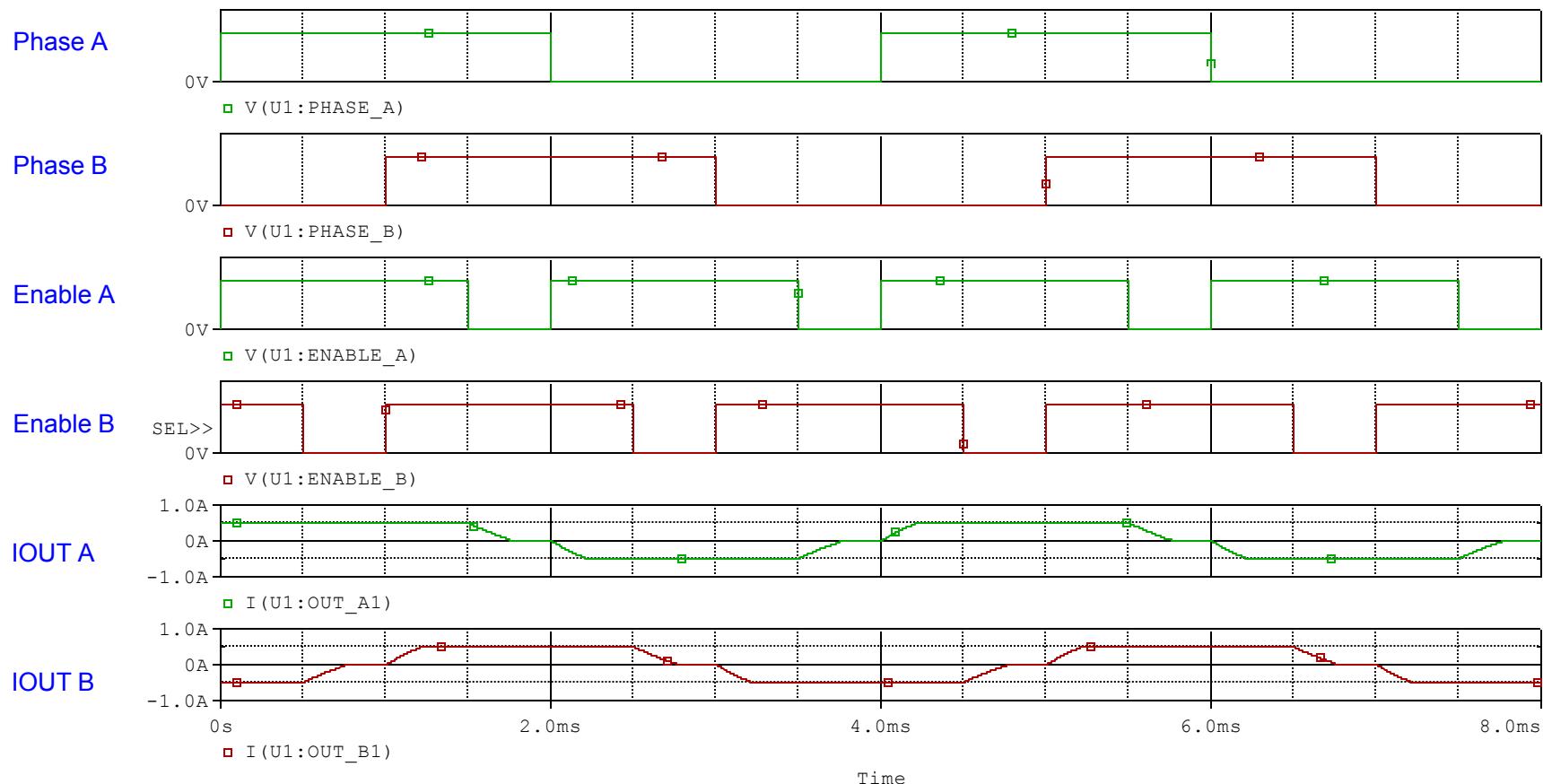

- This figure shows the simulation result of the circuit with Half-step switching sequence.


## 4.1 STANDBY

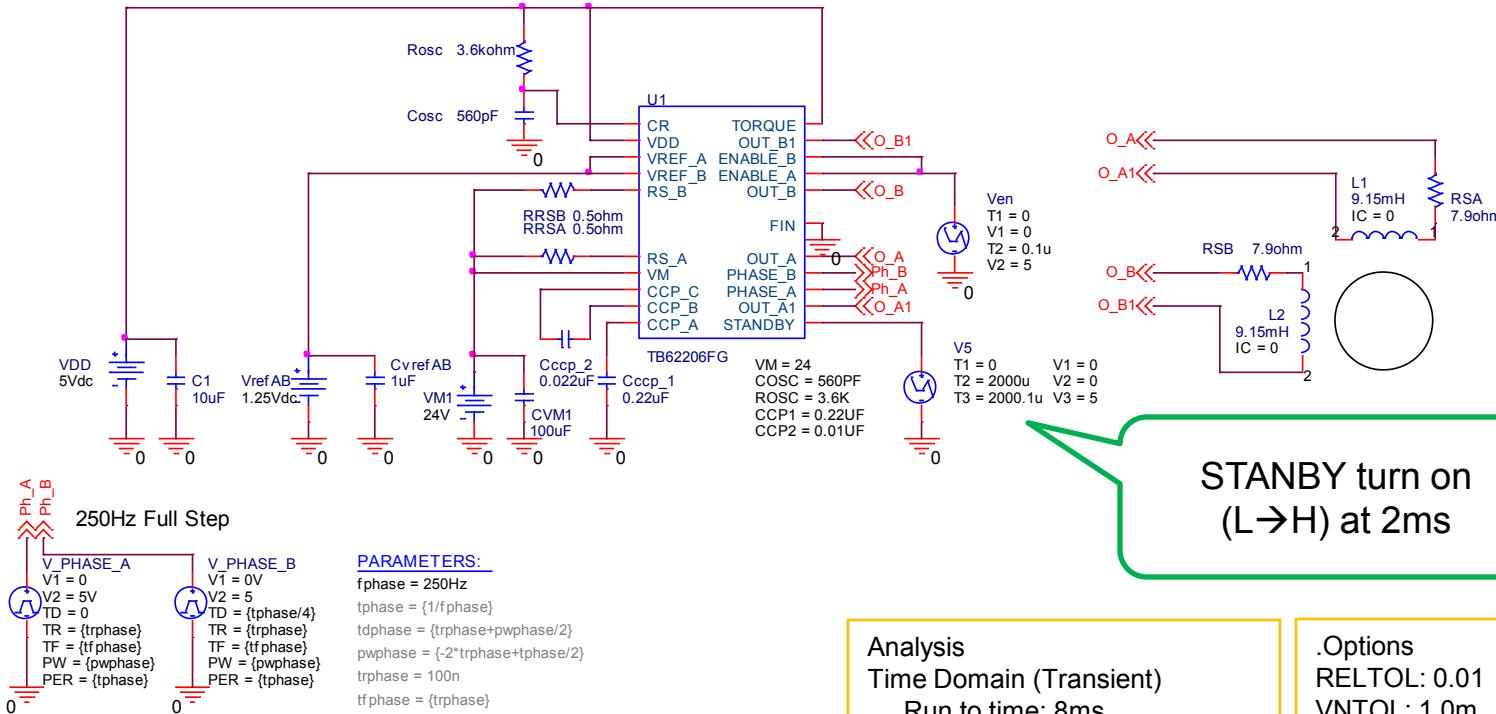

**Analysis**  
**Time Domain (Transient)**  
Run to time: 8ms  
Start saving data after: 0ms  
Maximum step size: -


**Options**  
REL TOL: 0.01  
VNTOL: 1.0m  
ABSTOL: 1.0n  
CHGTOL: 10p  
GMIN: 1.0E-12  
ITL1: 500  
ITL2: 200  
ITL4: 100

## 4.1 STANDBY

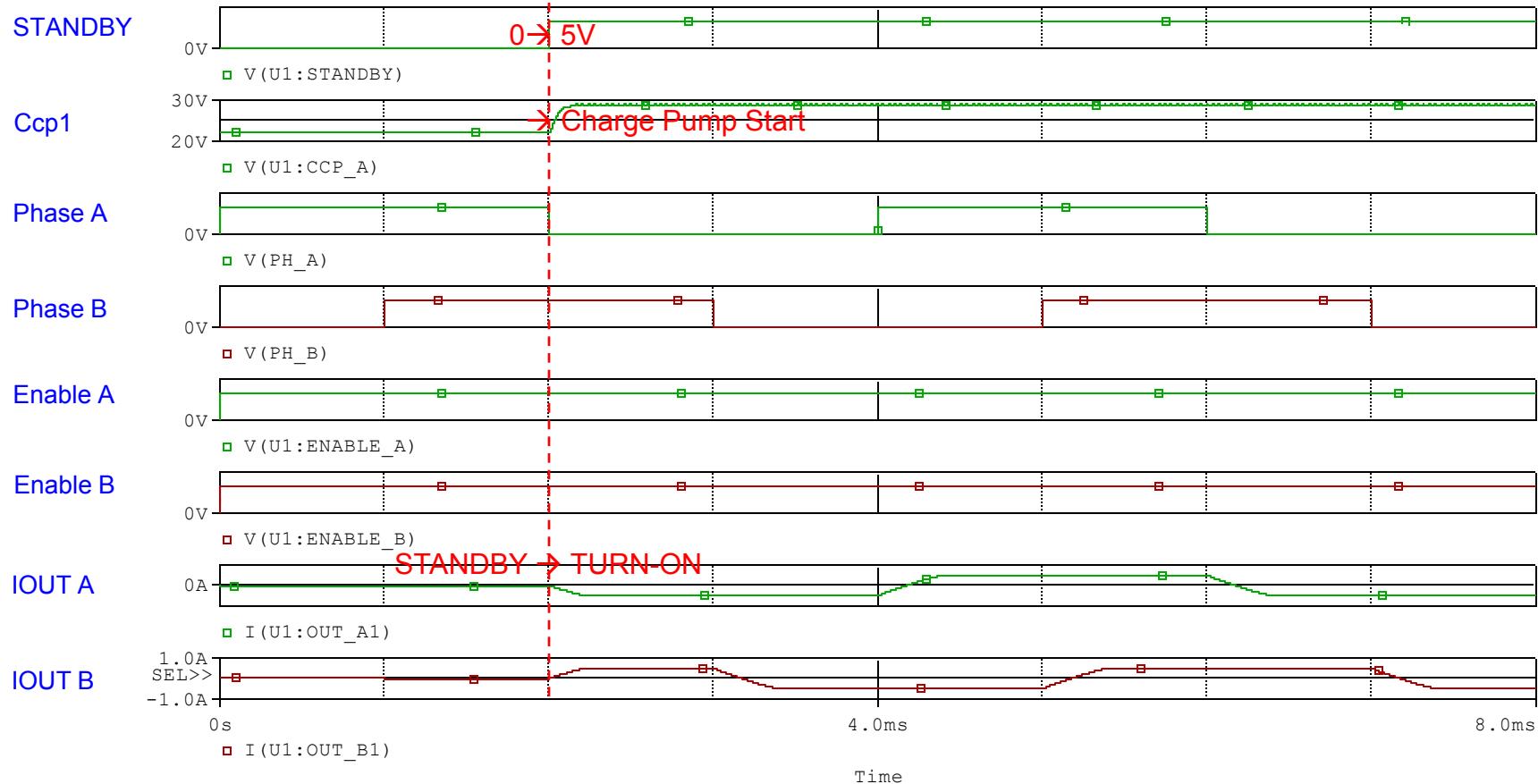


- This figure shows the simulation result of the circuit when V(STANDBY) changes from L→H.

## 4.2 TORQUE

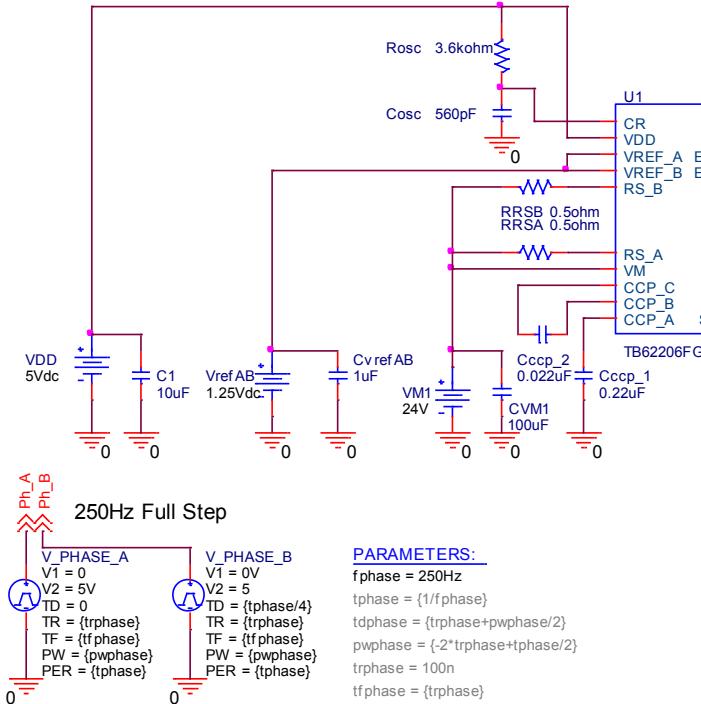

**PARAMETERS:**  
fphase = 250Hz  
tphase = {1/fphase  
tdphase = {trphase  
pwphase = {-2\*trph  
trphase = 100n  
tfphase = {trphase}


## TORQUE ( $H \rightarrow L$ ) at 4ms

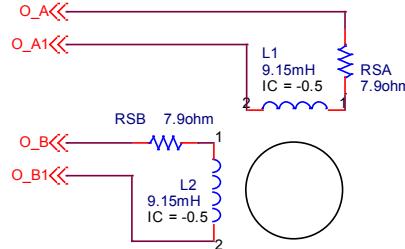

Analysis  
Time Domain (Transient)  
Run to time: 8ms  
Start saving data after: 0ms  
Maximum step size: -

```
.Options  
RELTOL: 0.01  
VNTOL: 1.0m  
ABSTOL: 1.0n  
CHGTOL: 1p  
GMIN: 1.0E-12  
ITL1: 500  
ITL2: 200  
ITL4: 100
```


## 4.2 TORQUE

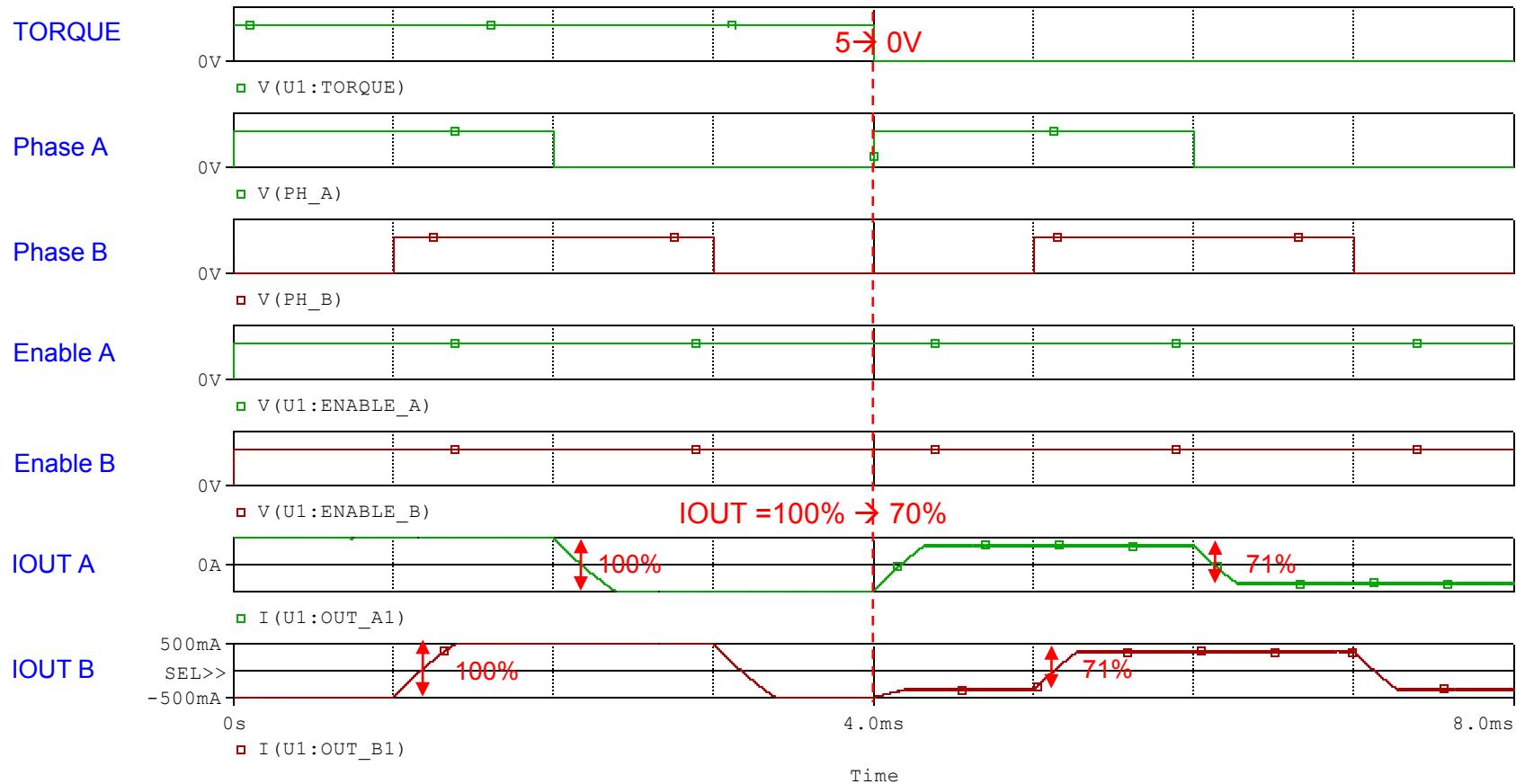


- This figure shows the simulation result of the circuit when  $V(TORQUE)$  changes from H $\rightarrow$ L, then the output current changes from 100% to 71%.
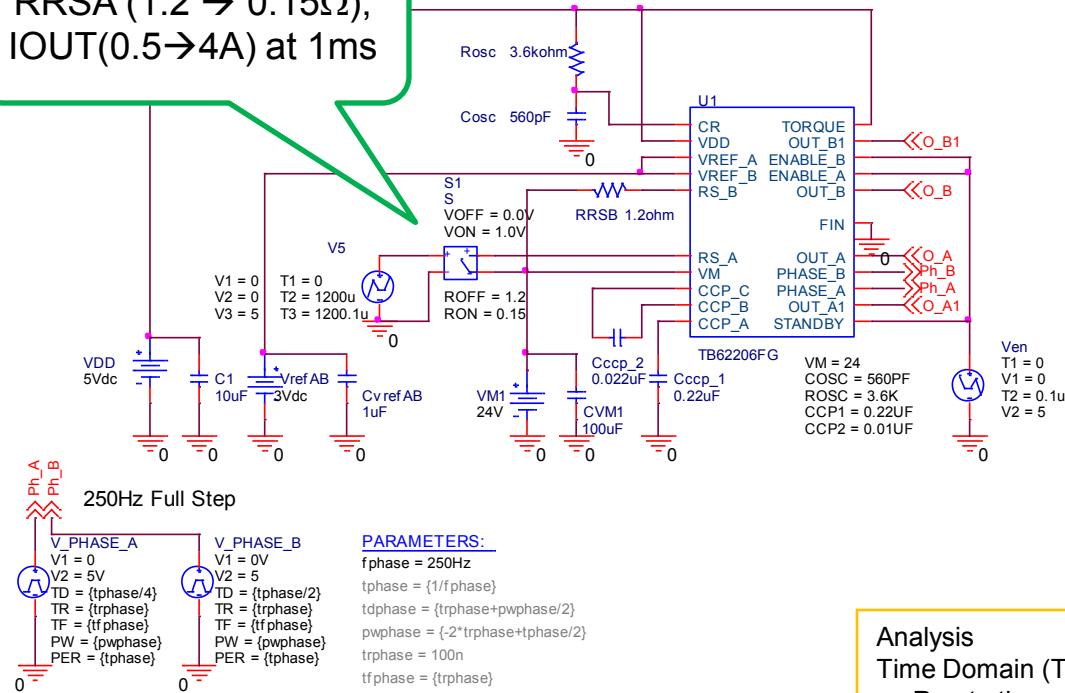
## 4.3 Phase A Over-current Protection

RRSA ( $1.2 \rightarrow 0.15\Omega$ ),  
IOUT( $0.5 \rightarrow 4A$ ) at 1ms



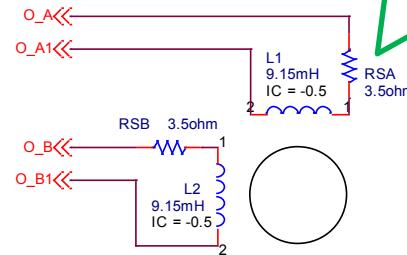
RS is a small value to test over current condition.



Analysis  
Time Domain (Transient)  
Run to time: 4.5ms  
Start saving data after: 0ms  
Maximum step size: -

.Options  
REL TOL: 0.01  
VNTOL: 1.0m  
ABSTOL: 1.0n  
CHGTOL: 1p  
GMIN: 1.0E-12  
ITL1: 500  
ITL2: 200  
ITL4: 100


## 4.3 Phase A Over-current Protection

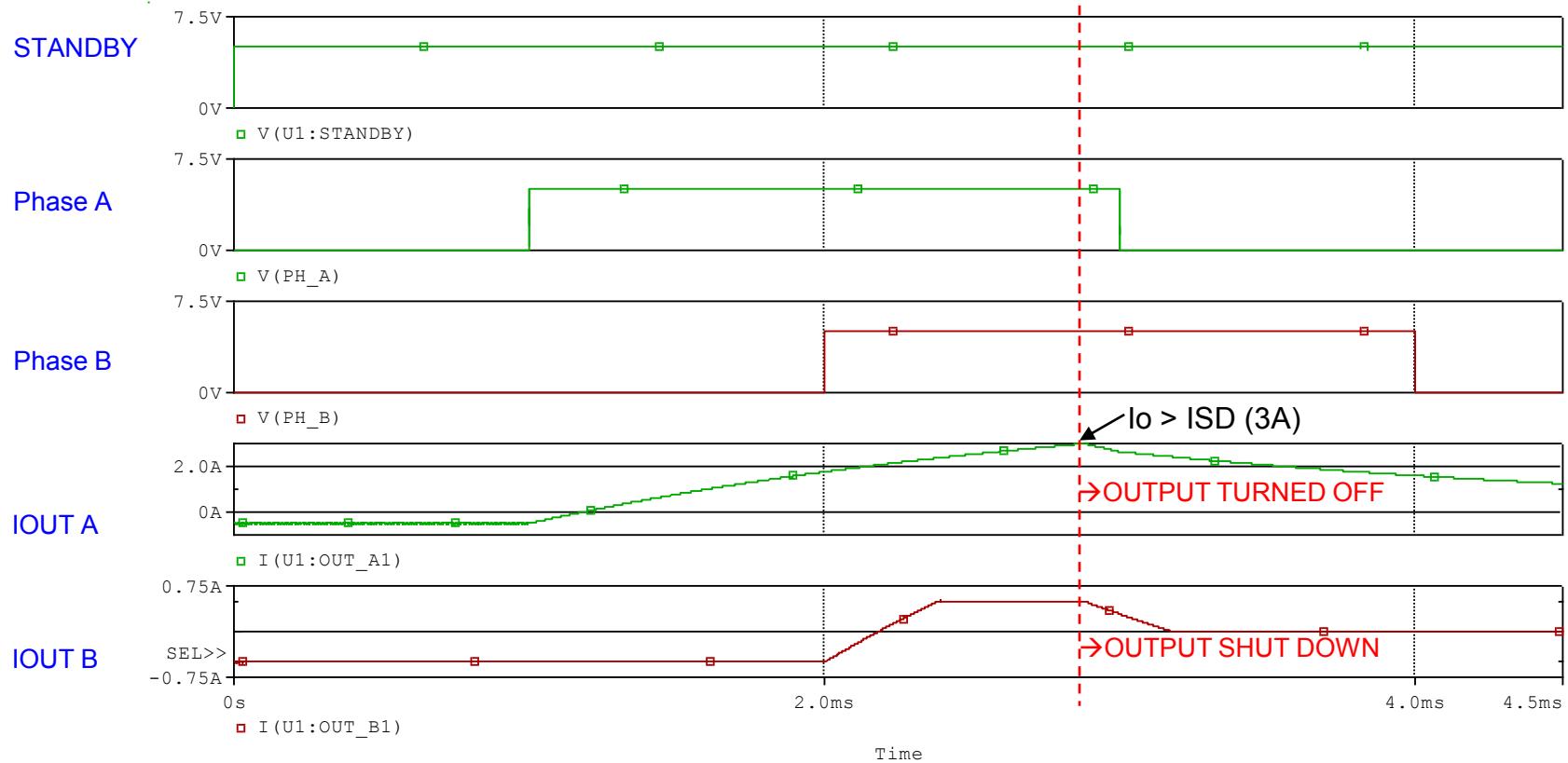


- This figure shows the simulation result of the circuit when Phase A output current exceeds the ISD(3A), then OCP shutdowns the output.
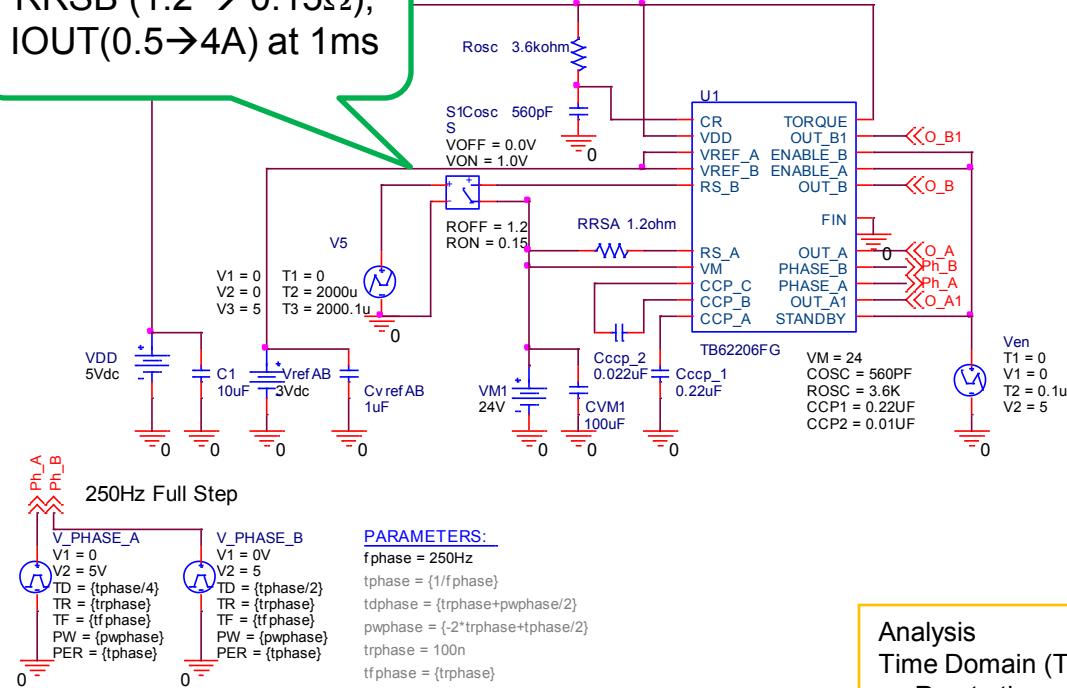
## 4.4 Phase B Over-current Protection

RRSB (1.2 → 0.15Ω),  
IOUT(0.5→4A) at 1ms



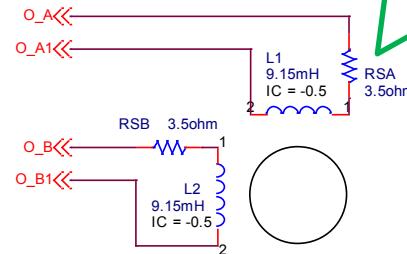
RS is a small value to test over current condition.



Analysis  
Time Domain (Transient)  
Run to time: 6ms  
Start saving data after: 0ms  
Maximum step size: -


Options  
REL TOL: 0.01  
VNTOL: 1.0m  
ABSTOL: 1.0n  
CHGTOL: 1p  
GMIN: 1.0E-12  
ITL1: 500  
ITL2: 200  
ITL4: 100

## 4.4 Phase B Over-current Protection

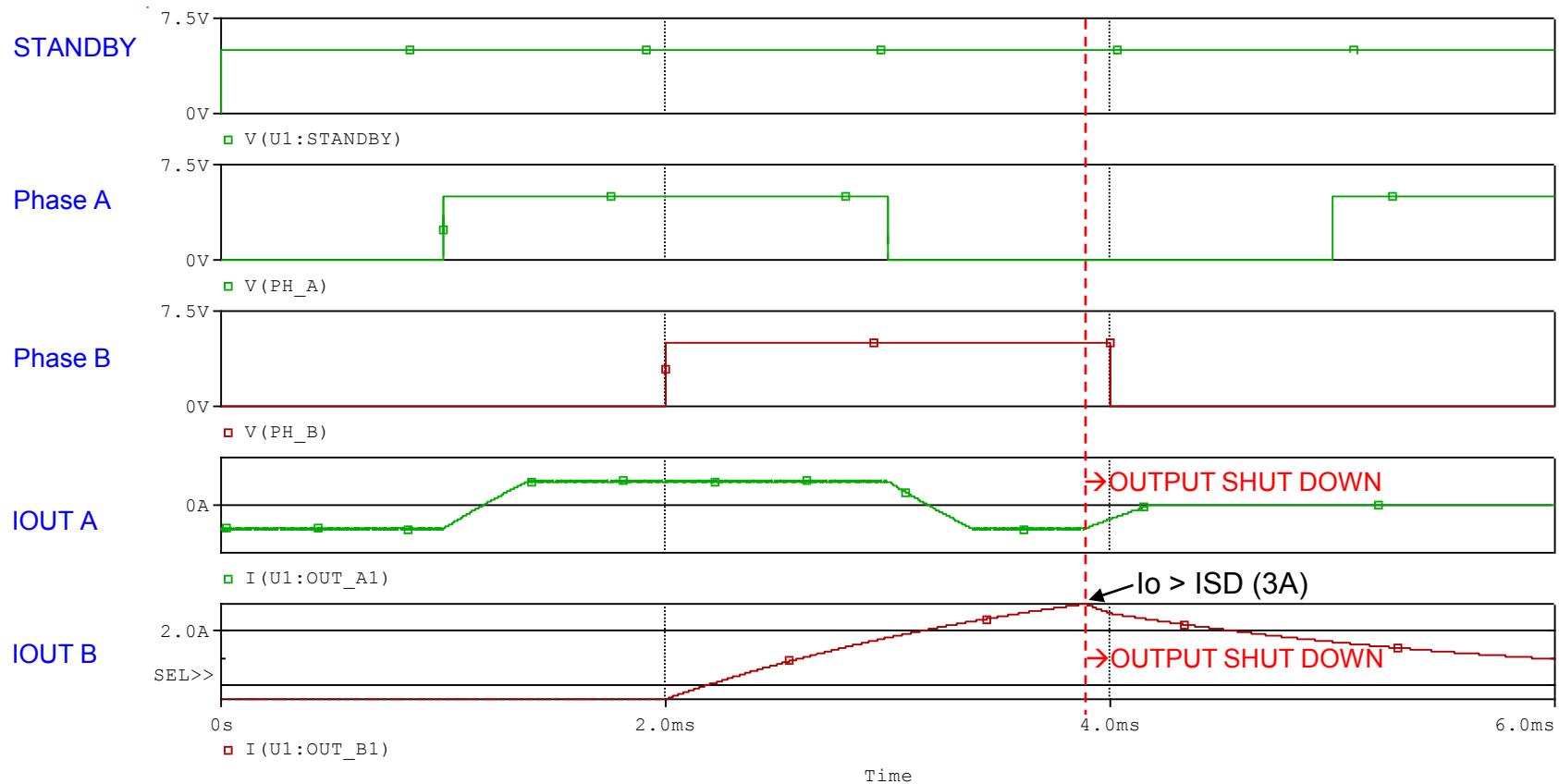


- This figure shows the simulation result of the circuit when Phase B output current exceeds the ISD(3A), then OCP shutdowns the output.

## 5 Output Ripple Current

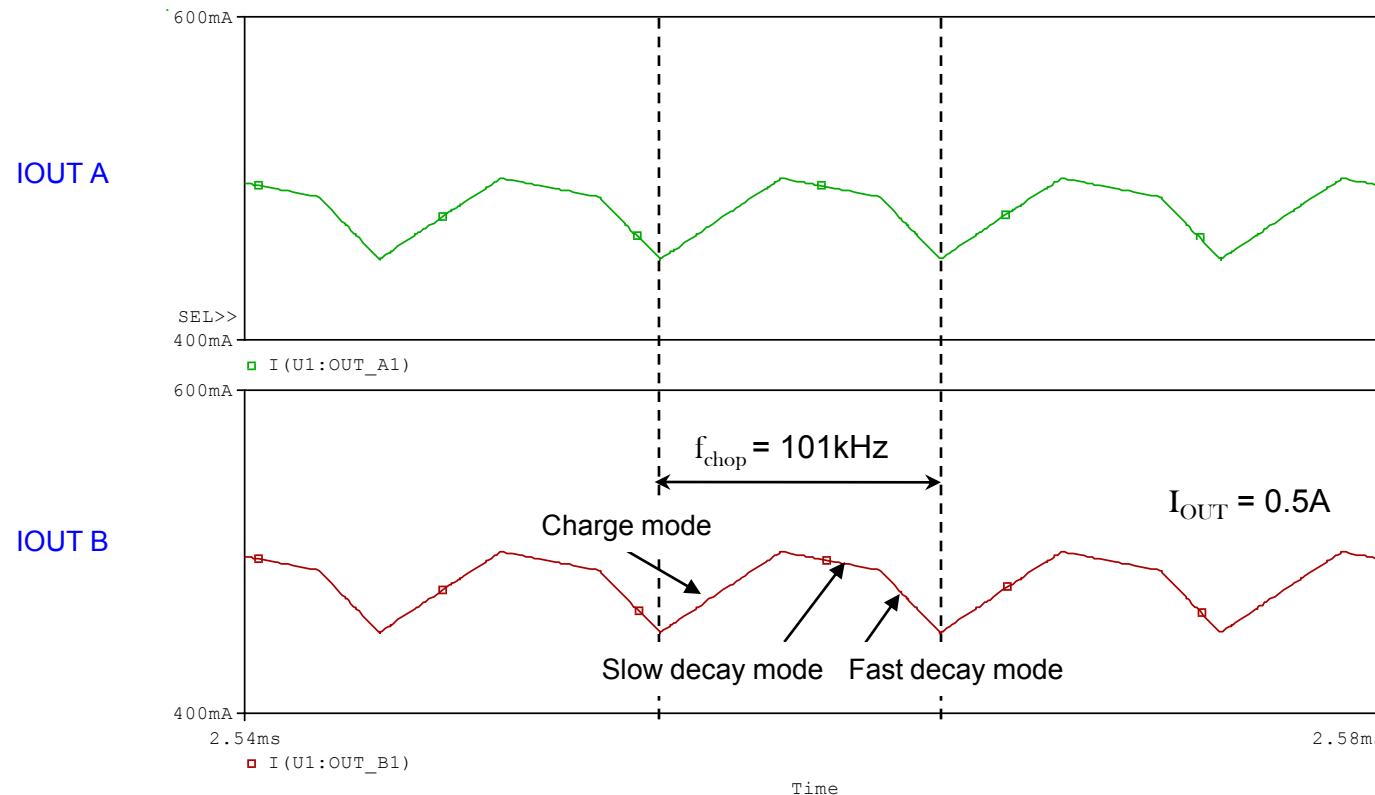


- This figure shows the output ripple current of the Mixed Decay Mode ,which consist of Charge ,Slow decay ,and Fast decay mode ,with 101kHz chopping frequency.
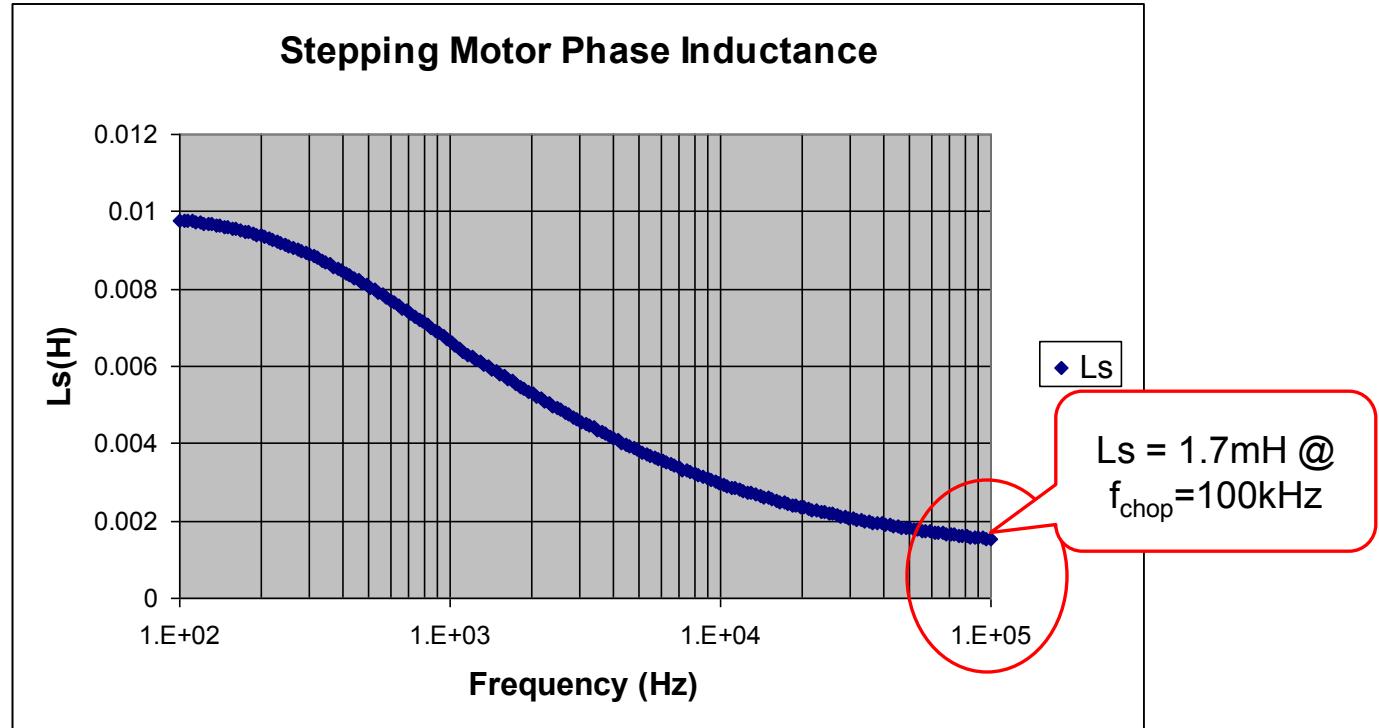
## 5.1 Stepping Motor Phase Inductance at The Chopping Frequency




- $L_s(H)$  vs. Frequency(Hz) is shown in figure above.  $L_s$  value at the chopping frequency (approximately 100kHz) will be used as stepping motor phase inductance.

## 5.2 Ripple Current Simulation

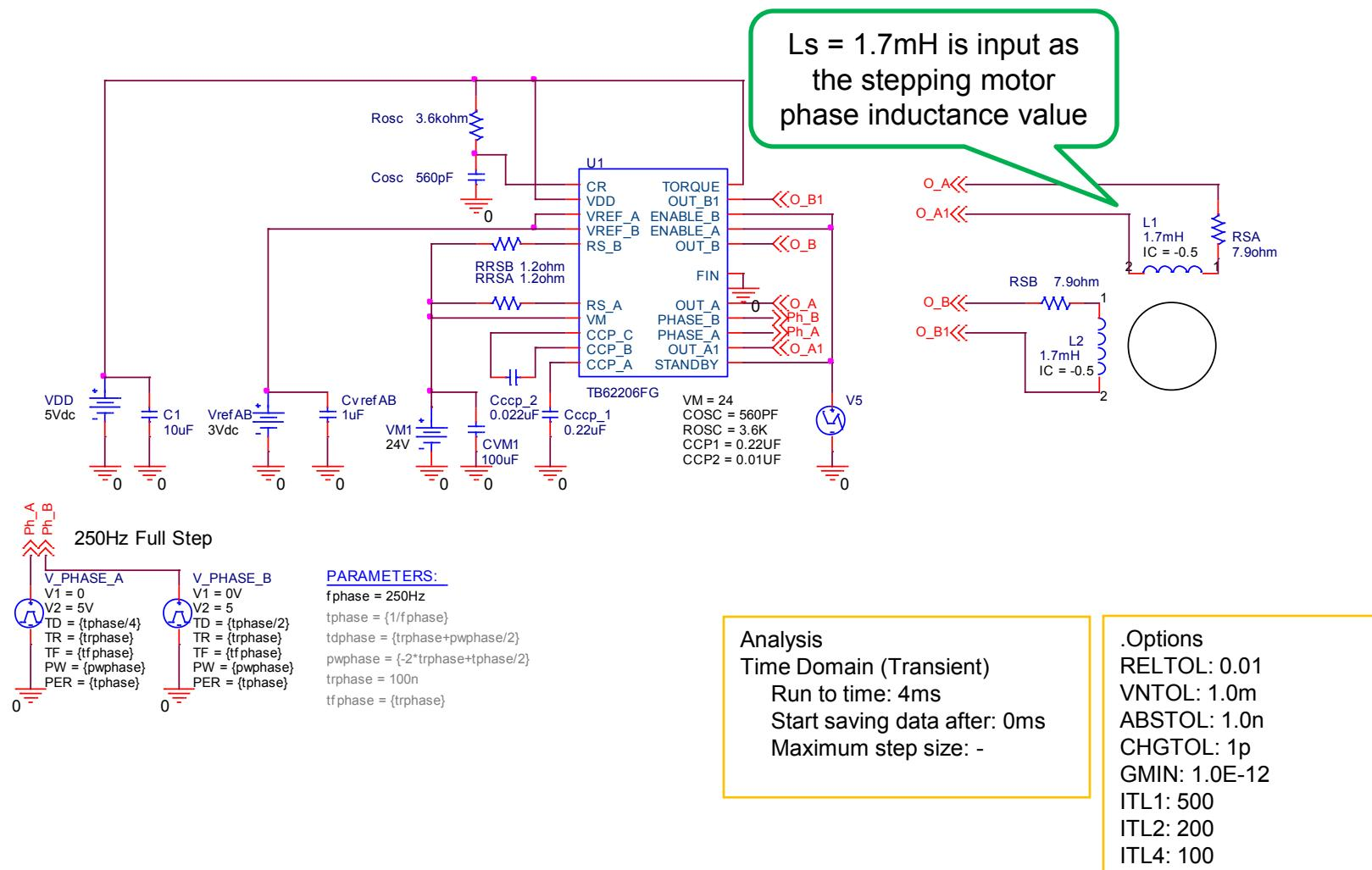


## 5.2 Ripple Current Simulation

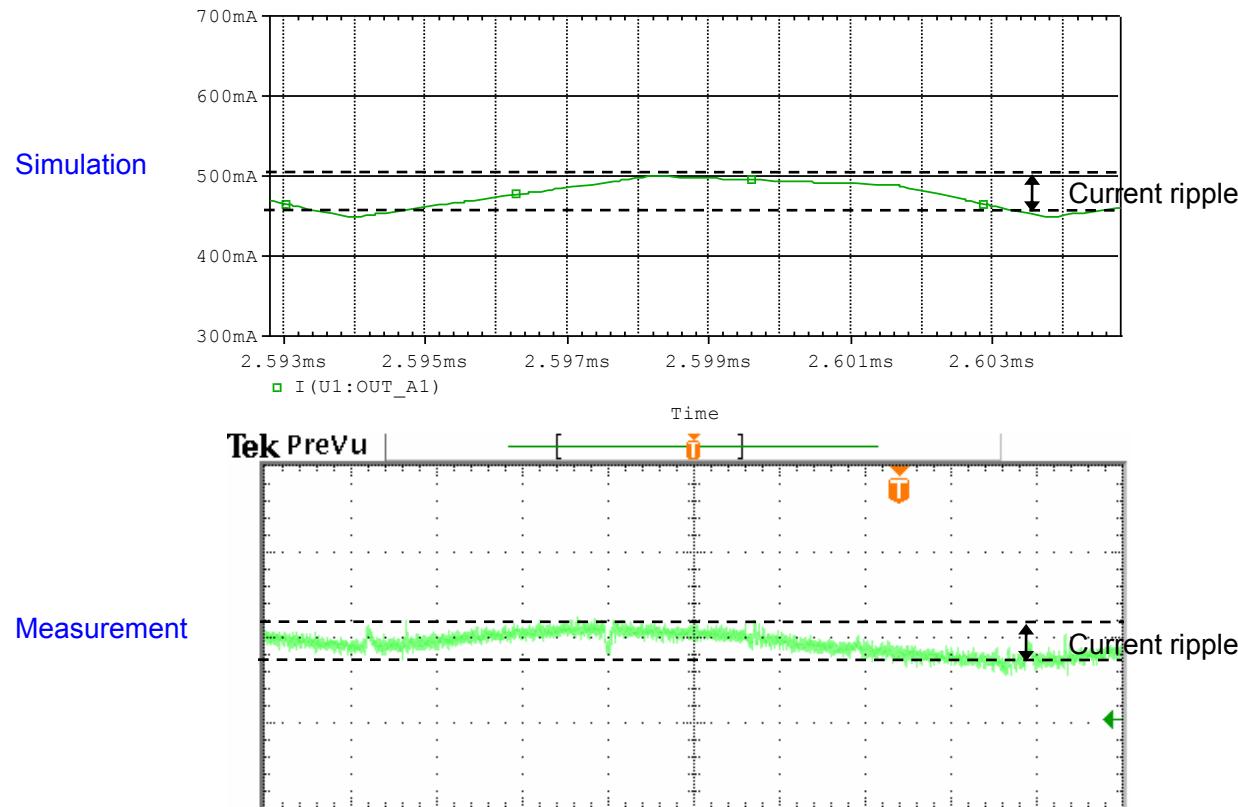


- The simulation result shows the current ripple that agrees to the measurement data.

## 6. The Current Changing Rate

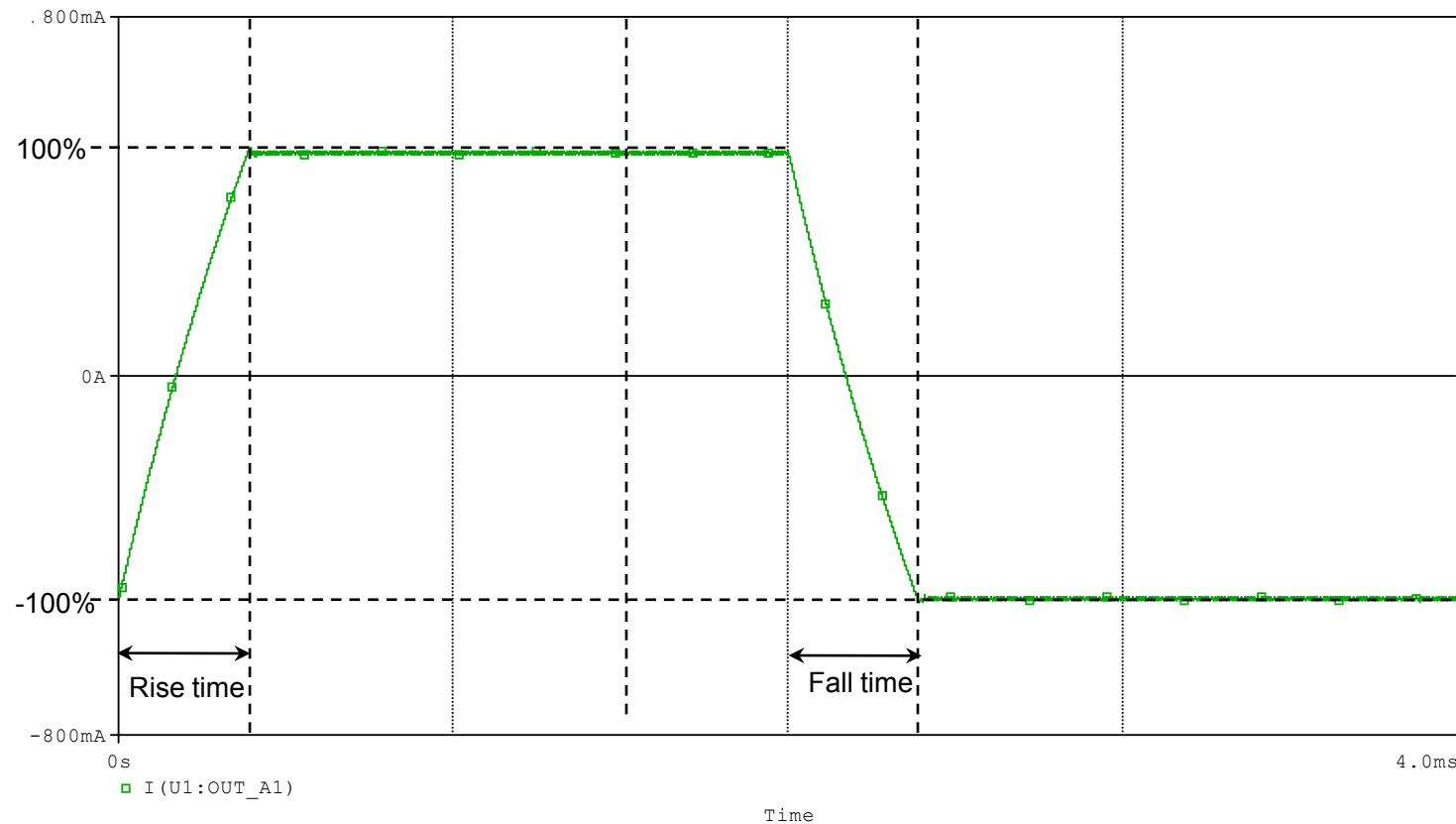


- This figure shows the current changing rate (rise and fall time) that is determined by the phase inductance value.
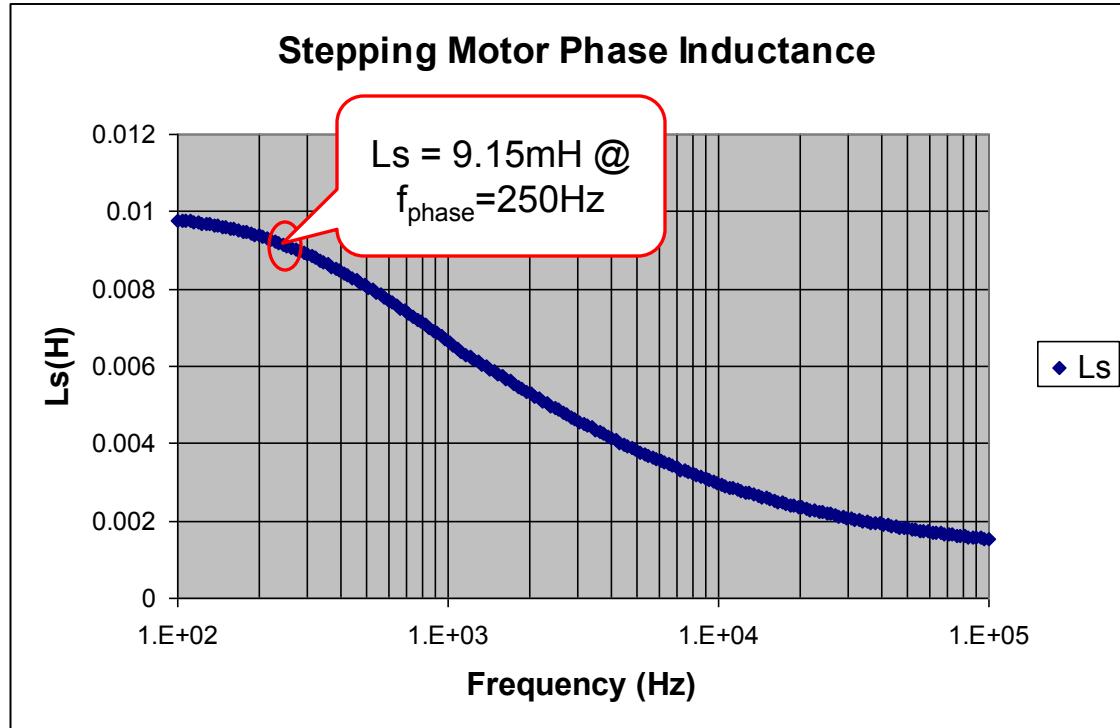
## 6.1 Stepping Motor Phase Inductance at The Phase Frequency





- $L_s(H)$  vs. Frequency(Hz) is shown in figure above.  $L_s$  value at the phase frequency (250 Hz) will be used as stepping motor phase inductance.

## 6.2 Current Changing Rate Simulation

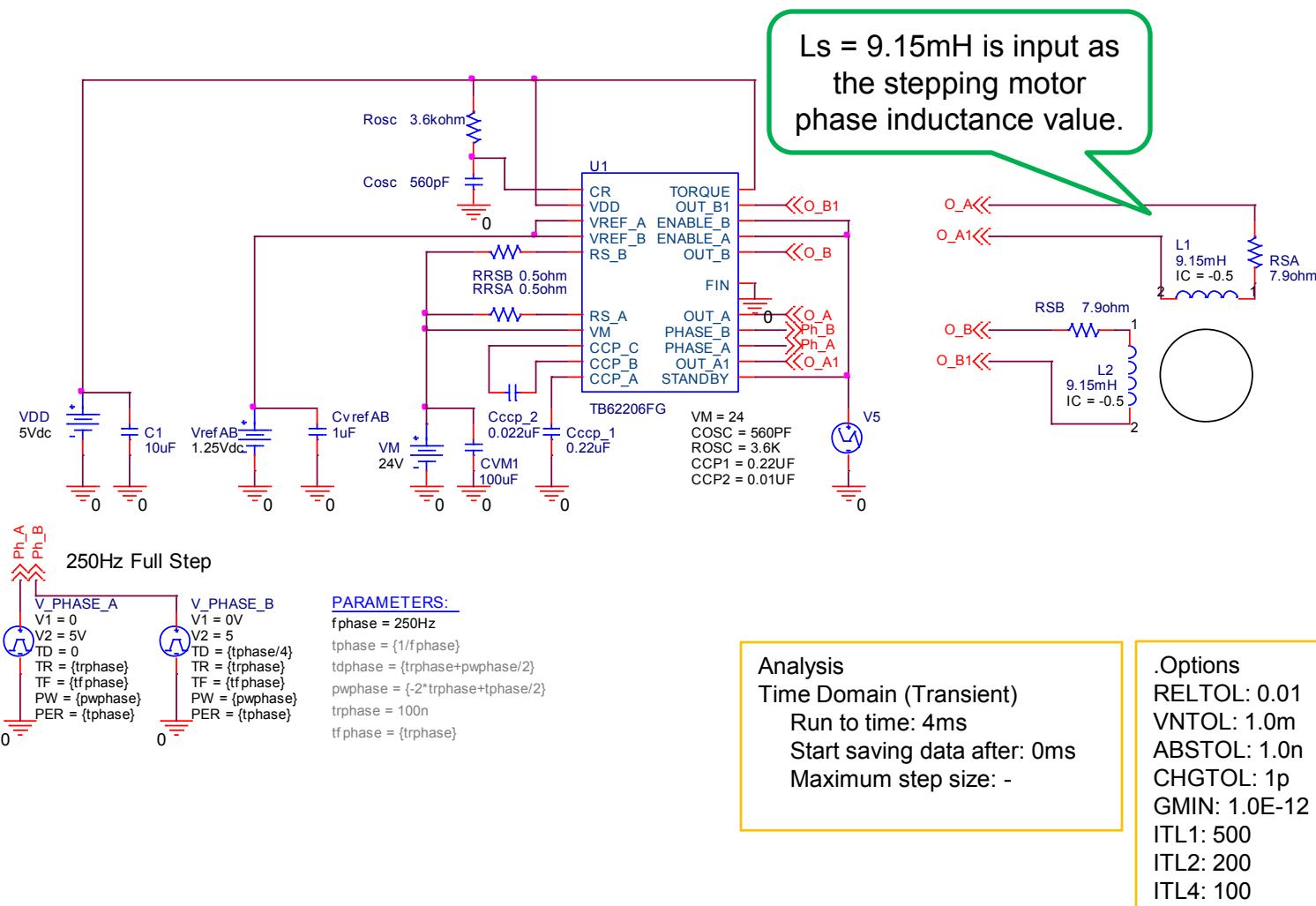


## 6.2 Current Changing Rate Simulation

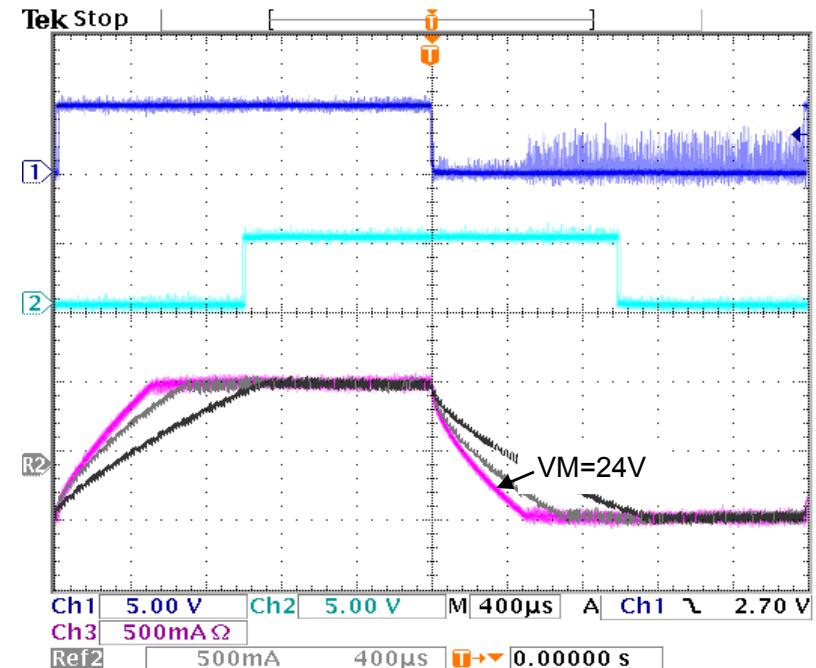
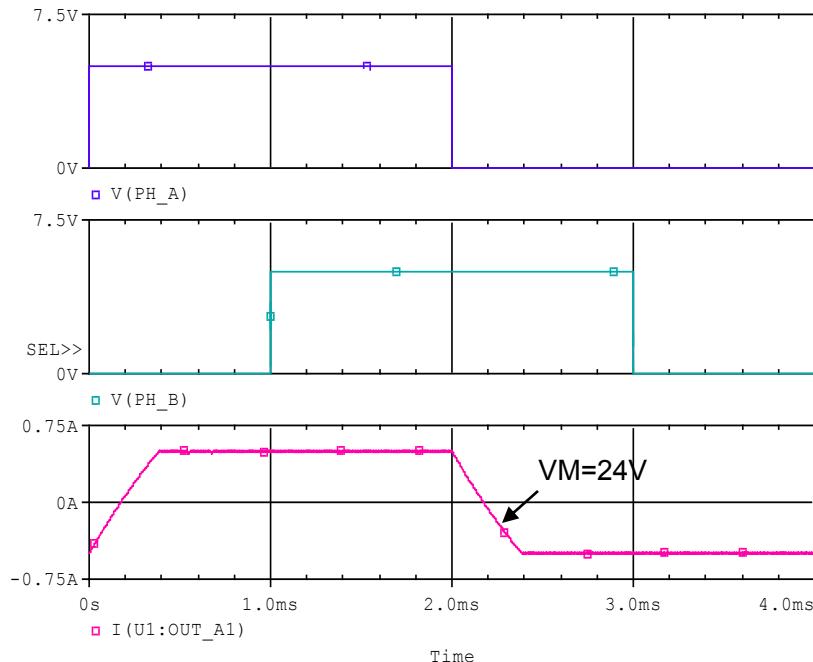


- The simulation result shows the current changing rate (rise and fall time) that agrees to the measurement data.
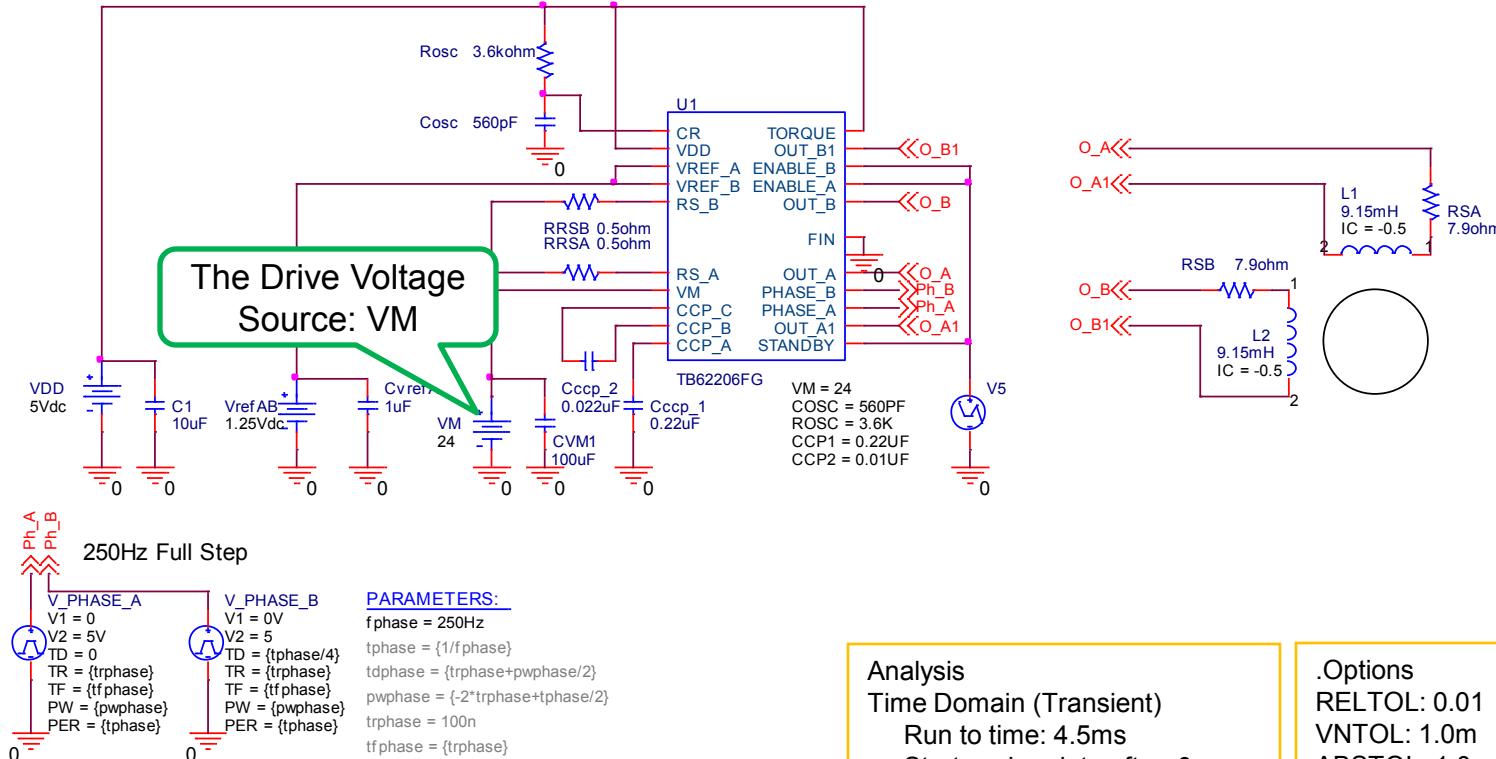
## 7. Optimization of The Drive Voltage VM


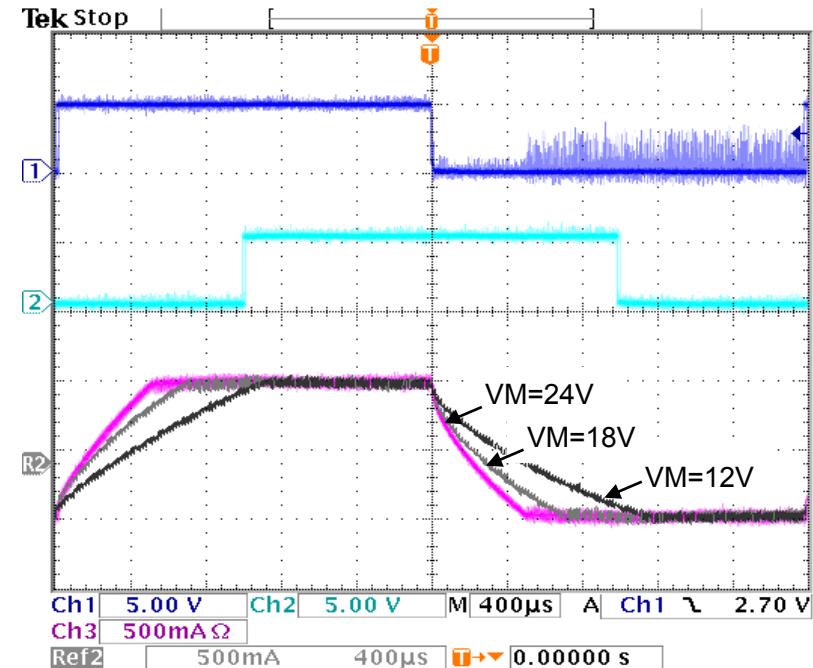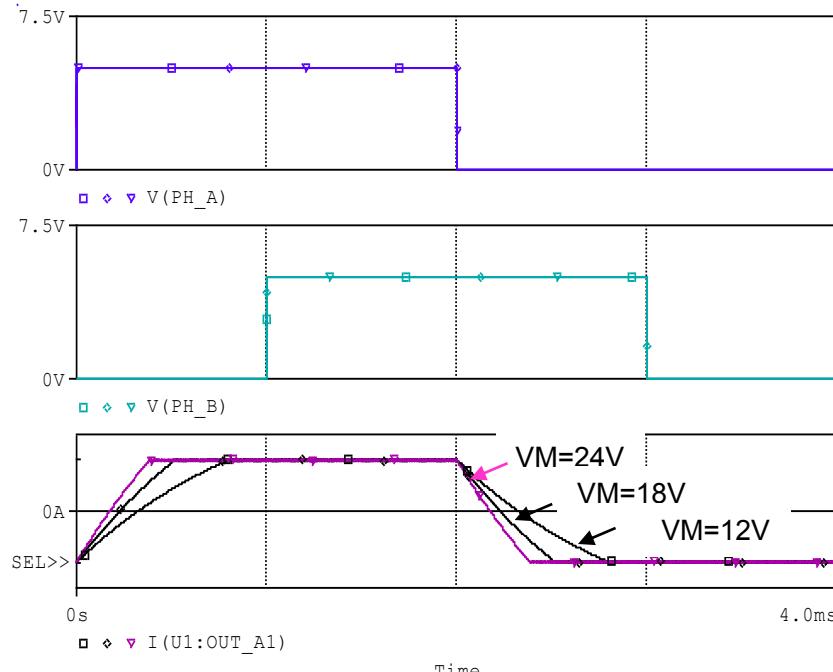
## 7. Optimization of The Drive Voltage VM



- These figures show that the current changing rates (rise and fall time) depend on the drive voltage (VM). The higher current changing rate means higher phase frequency is available.

# Simulations index

<b>Simulations</b>	<b>Folder name</b>
1. Full Step Switching Sequence.....	Full-Step
2. Half Step Switching Sequence.....	Half-Step
3. STANDBY.....	STANDBY
4. TORQUE.....	TORQUE
5. Phase A Over-current Protection.....	OCP_A
6. Phase B Over-current Protection.....	OCP_B
7. Ripple Current Simulation.....	RIPPLE
8. Current Changing Rate Simulation.....	I_Step
9. Optimization of The Drive Voltage VM.....	VM